

Chapter 2 - Circuit Elements.

IB
1

For now --
Voltage sources
Current sources
Resistance
Controlled sources


Also - conventions:
Direction of
current flow.

Terms: Nodes, Loops
"Connection is valid"

CH 2 -
Problems:
1-16
21, 23

"Validity" of a circuit ...
Voltage & current sources -

Some just don't work

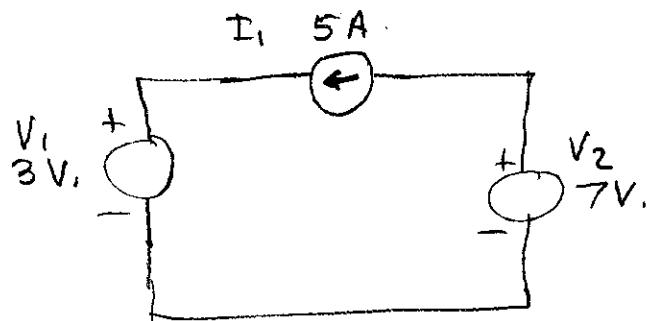


This one is valid ~

$$I(V_1) =$$


$$I(V_2) =$$

$$V(I_1) =$$

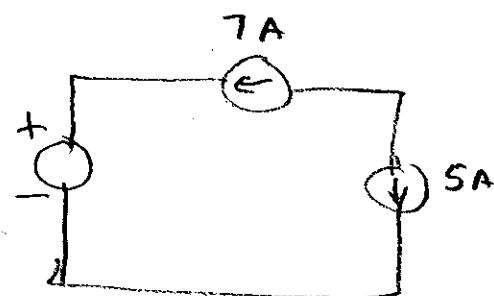

This one is not valid
 $I = ?$

"Cut set" of current sources.

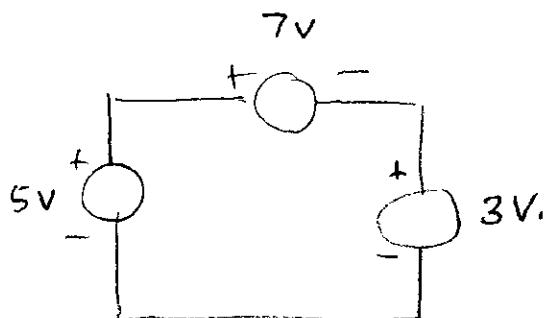


Not valid

$$V = ?$$

Loop of voltage sources

Is this circuit valid?

1B
2

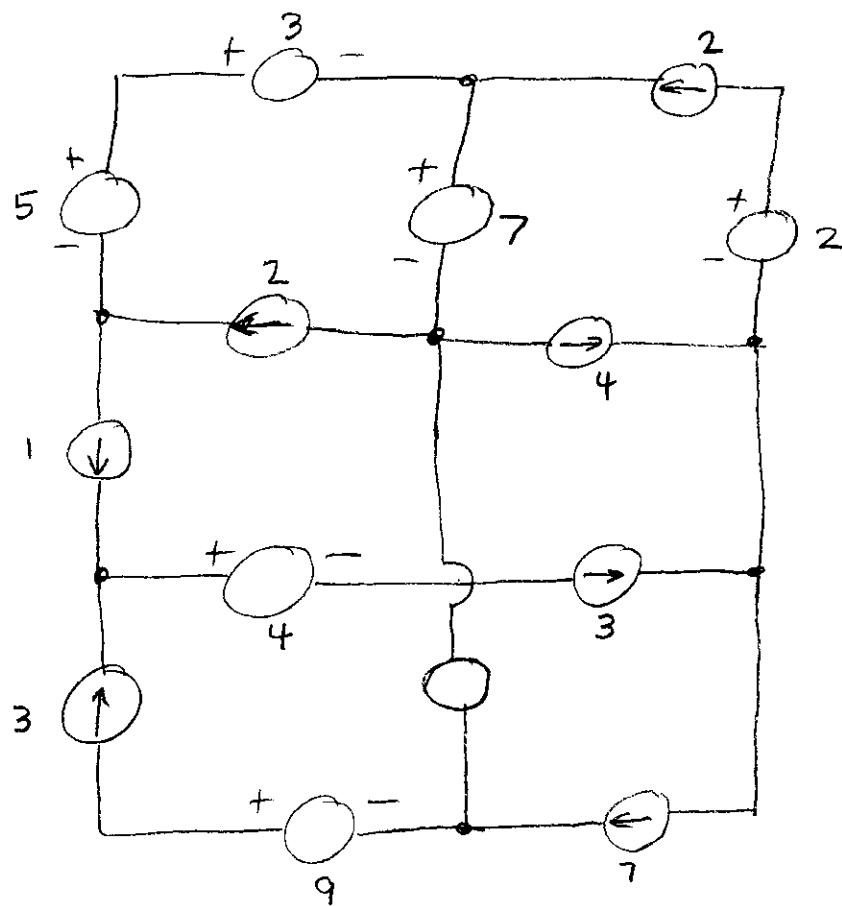


Kirchoff's laws ---

1B
3

"Sum of currents into a node = 0"
(out of)

"Sum of voltages around a loop = 0".

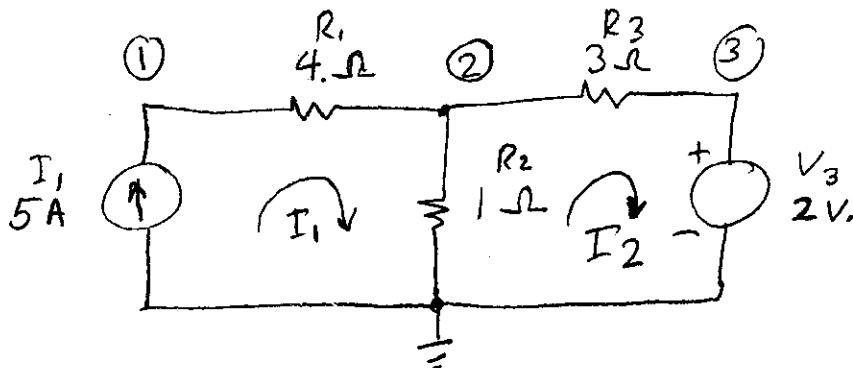

Node eq.:
(out-of)

$$\left\{ \begin{array}{l} -I_1 + \frac{V_1 - V_2}{R_1} = 0 \quad \text{Node } 1 \\ \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0 \quad \text{Node } 2 \\ V_3 = 2 \end{array} \right.$$

Current in voltage source
is arbitrary, so
don't write a node equation
for this node.


Loop eq.:

$$\left\{ \begin{array}{l} I_1 = 5 \\ R_2(I_2 - I_1) + R_3 I_2 + V_3 = 0 \end{array} \right.$$

Voltage across current source
is arbitrary, so don't
write loop equation
for this loop.

- Node eq. guides -
- Call one node ground, node 0, its voltage is 0.
 - First, write it in symbolic form.
 - Be careful of signs.

Info:

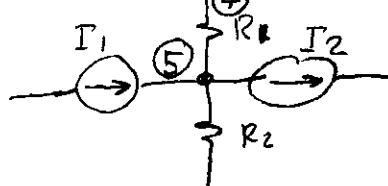

$$I_1 - I_2 + \frac{V_4 - V_5}{R_1} + \frac{-V_5}{R_2} = 0$$

Out-of

$$-I_1 + I_2 + \frac{V_5 - V_4}{R_1} + \frac{V_5}{R_2} = 0$$

→ Then simplify

→ Then substitute values.

Write a node equation for every node,

But not for nodes with grounded voltage source
and not for both ends of a floating
voltage source.

Write everything

Don't skip steps.

Finish solving the example --- (node equations)

IB
⑤

Group V terms, put terms not having a V on the right --

$$① \quad V_1\left(\frac{1}{R_1}\right) + V_2\left(-\frac{1}{R_1}\right) = I_1$$

$$② \quad V_1\left(-\frac{1}{R_1}\right) + V_2\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + V_3\left(-\frac{1}{R_3}\right) = 0$$

Solve by substitution:

$$① \quad V_1\left(\frac{1}{R_1}\right) = I_1 - V_2\left(-\frac{1}{R_1}\right)$$

$$V_1 = R_1 I_1 - V_2\left(-\frac{R_1}{R_1}\right)$$

$$V_1 = R_1 I_1 + V_2$$

Substitute V_1

$$② \quad (R_1 I_1 + V_2)\left(-\frac{1}{R_1}\right) + V_2\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + V_3\left(-\frac{1}{R_3}\right) = 0$$

simplify

$$-\frac{R_1 I_1}{R_1} + V_2\left(-\frac{1}{R_1}\right) + V_2\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + V_3\left(-\frac{1}{R_3}\right) = 0$$

$$-I_1 + V_2\left(\frac{1}{R_2} + \frac{1}{R_3}\right) + V_3\left(-\frac{1}{R_3}\right) = 0$$

Substitute values

$$-5 + V_2 \left(\frac{1}{1} + \frac{1}{3} \right) + 2 \left(-\frac{1}{3} \right) = 0$$

$$-15 + V_2 (3 + 1) - 2 = 0$$

$$-17 + V_2 (4) = 0$$

$$V_2 (4) = 17$$

$$\underline{V_2 = \frac{17}{4} = 4.25}$$

$$V_1 = R_1 I_1 + V_2$$

$$= (4)(5) + 4.25$$

$$= 20 + 4.25$$

$$= 24.25$$

→ I didn't apply any cleverness
here --

Just follow the rules!


Find currents by Ohms Law.

$$I_2 = \frac{V_{R3}}{R_3} = \frac{V_2 - V_3}{R_3} = \frac{4.25 - 2}{3} = \frac{2.25}{3} = 0.75 A$$

Then check ① Makes sense?
 ② by simulation

Loop equations

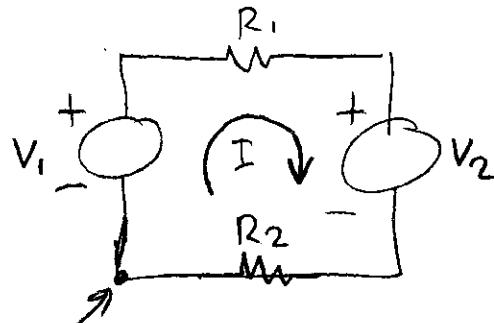
- Choose loops carefully -
 - Need to include all branches
 - It can be tricky to pick the loops
- Be careful of signs -




pick a starting point

If I is positive,
Voltage across R is positive.

So ---

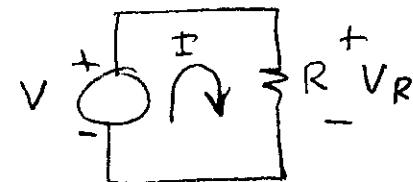
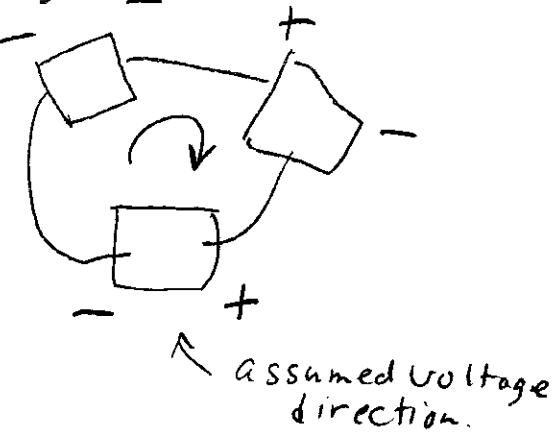
$$-V_1 + IR_1 + V_2 + IR_2 = 0 \text{ That means } -$$



When current goes through
an element



The "from" end has + voltage
the "to" end has - voltage

So a resistor has the same
sign for voltage & current.

Finish solving the example (P.3)

$$R_2(I_2 - I_1) + R_3(I_2) + V_3 = 0$$

Group I terms, put terms not having I on the right ..

$$I_1(-R_2) + I_2(R_2 + R_3) = -V_3$$

Substitute:

$$5(-1) + I_2(1+3) = -2$$

$$-5 + I_2(4) = -2$$

$$I_2(4) = 3$$

$$I_2 = \frac{3}{4} = 0.75$$

Find voltages by Ohm's Law.

$$V_{R_3} = I_{R_3} R_3 = \left(\frac{3}{4}\right)(3) = \frac{9}{4} = 2.25$$


$$V_{R_1} = I_{R_1} R_1 = (5)(4) = 20$$

$$V_{R_2} = I_{R_2} R_2 = (I_1 - I_2) R_2 = (5 - 0.75)(1) \\ = 4.25$$

Controlled sources

(This is how we make amplifiers)

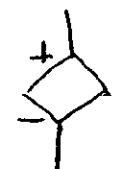E = VCVS = Voltage controlled voltage source



H = CCVS = Current controlled voltage source ("trans resistance")


G = VCCS = Voltage controlled current source ("trans conductance")




F = CCCS = Current controlled current source

Example:

VCVS

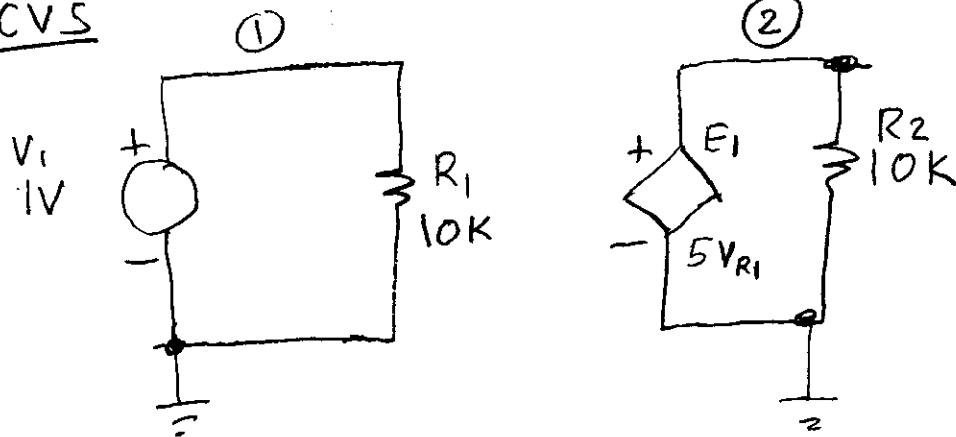


$$V_2 = 5 V_{R1} = 5$$

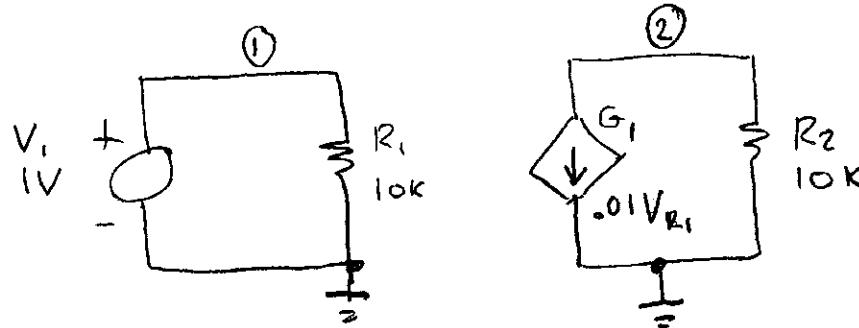

VCCS

1B
10

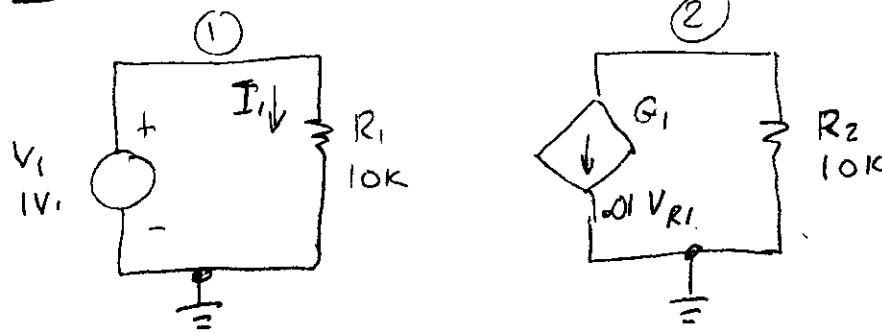


$$\text{Node } 2 : G_1 V_1 + \frac{V_2}{R_2} = 0$$

$$0.01(1) + \frac{V_2}{10k} = 0$$

$$\frac{V_2}{10k} = -0.01$$

$$V_2 = (-0.01)(10k) = \boxed{-100}$$

CCCS

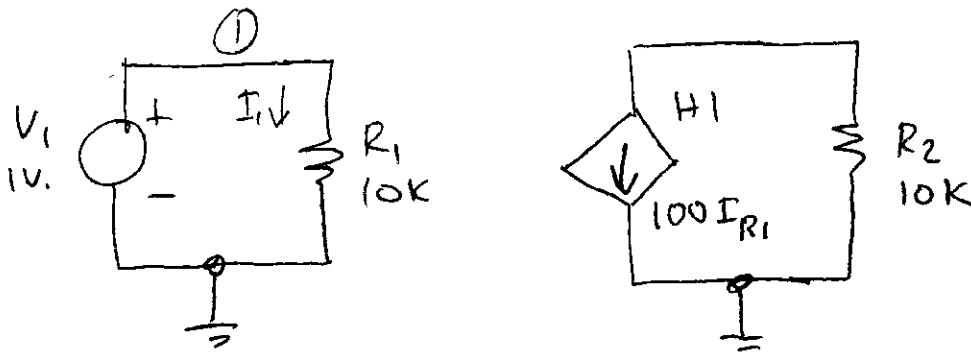

$$I_{R1} = \frac{V_1}{R_1}$$

BJT
amplifier.

$$H_1 I_{R1} + \frac{V_2}{R_2} = 0$$

$$H_1 \left(\frac{V_1}{R_1} \right) + \frac{V_2}{R_2} = 0$$

$$100 \left(\frac{1}{10k} \right) + \frac{V_2}{10k} = 0$$

$$100 + V_2 = 0$$

$$V_2 = -100$$