



Are these circuits valid?

If so -- show all node voltages and branch currents, on the schematic


If not -- why not? (which rule is violated)

and indicate at least one branch current

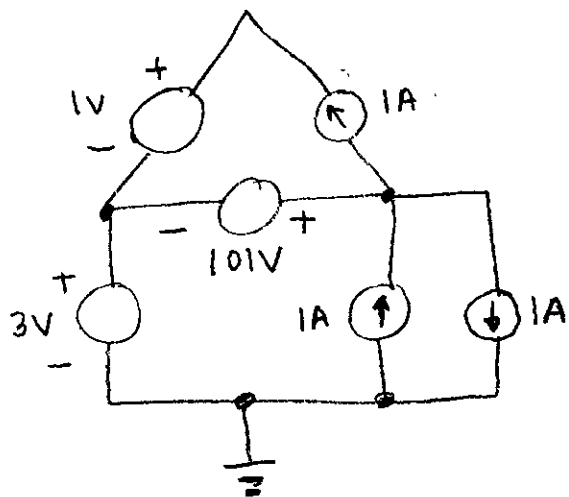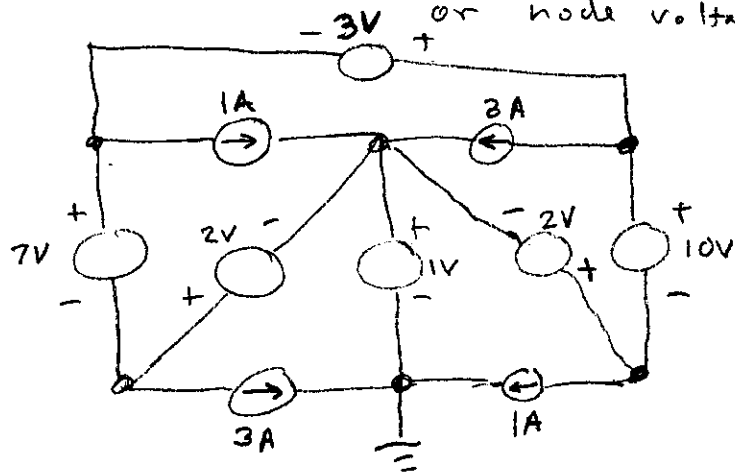-3V or node voltage that cannot be calculated.



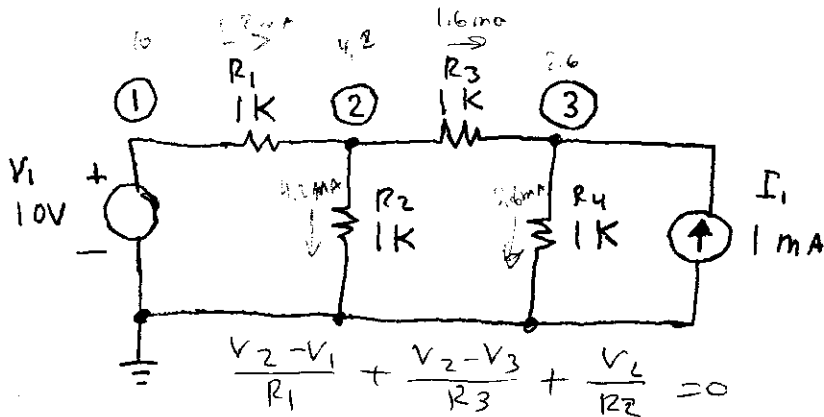Find the node equations,
and solve for all node voltages



$$\frac{V_2 - V_1}{1K} + \frac{V_2 - V_3}{1K} + \frac{V_2}{1K} = 0$$

$$10 \left(-\frac{1}{1K}\right) + V_2 \left(\frac{3}{1K}\right) + V_3 \left(-\frac{1}{1K}\right) = 0$$

$$-10 + 3V_2 - V_3 = 0$$

$$-10 + 3(1 + 2V_3) - V_3 = 0$$

$$-10 - 3 + 6V_3 - V_3 = 0$$

$$-13 + 5V_3 = 0$$

$$5V_3 = 13$$

$$V_3 = \frac{13}{5} = 2.6$$

$$\frac{V_3 - V_2}{R_3} + \frac{V_3}{R_4} - I_1 = 0$$

$$\frac{V_3 - V_2}{1K} + \frac{V_3}{1K} - 1mA = 0$$

$$V_2 \left(-\frac{1}{1K}\right) + V_3 \left(\frac{2}{1K}\right) - 1mA = 0$$

$$-V_2 + 2V_3 - 1 = 0$$

$$\Rightarrow V_2 = 1 - 2V_3$$

$$V_2 = 2V_3 - 1$$

~~$$V_2 = 1 - 2\left(\frac{13}{5}\right)$$~~

~~$$= 1 - \frac{26}{5}$$~~

$$V_2 = 2\left(\frac{13}{5}\right) - 1$$

$$= \frac{26}{5} - \frac{5}{5}$$

$$= \frac{21}{5} = 4.2$$

-0

-1 simple math error

-2 math error or didn't get answers.

-3 concept error, still nodal analysis.

-4

-5 - all wrong.