

Name _____

Find the Loop equations, using the loops indicated

Then find all
branch currents
and node voltages,
using your loop equations.

