

$$\textcircled{1} \quad I_1 = 1 \text{ mA}$$

$$\textcircled{2} \quad R_4(I_2 - I_1) + R_3(I_2) + R_2(I_2 - I_3) = 0$$

$$\textcircled{3} \quad R_2(I_3 - I_2) + R_1(I_3) + V_1 = 0$$

$$1K(I_2 - 1 \text{ mA}) + 1K(I_2) + 1K(I_2 - I_3) = 0$$

$$1K(I_3 - I_2) + 1K(I_3) + 10 = 0$$

$$I_2 - 1 \text{ mA} + I_2 + I_2 - I_3 = 0$$

$$I_3 - I_2 + I_3 + \frac{10}{1K} = 0$$


$$3I_2 - I_3 = 1 \text{ mA}$$

$$\rightarrow \begin{bmatrix} 3 & -1 & | & 1 \\ -1 & 2 & | & -10 \end{bmatrix}$$

$$-I_2 + 2I_3 = -10 \text{ mA}$$

$$\begin{bmatrix} 1 & -\frac{1}{3} & | & \frac{1}{3} \\ 0 & \frac{5}{3} & | & -\frac{29}{3} \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & | & \frac{-8}{5} \\ 0 & 1 & | & -\frac{29}{5} \end{bmatrix}$$

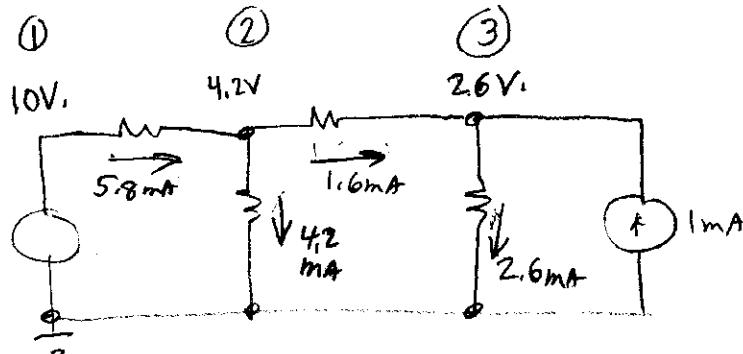

$$I_2 = -1.6 \text{ mA} = -\frac{8}{5} \text{ mA}$$

$$I_3 = -5.8 \text{ mA} = -\frac{29}{5} \text{ mA}$$

$$V_2 = (4.2 \text{ mA})(1K) = 4.2$$

$$V_3 = (2.6 \text{ mA})(1K) = 2.6$$

$$\textcircled{2} \quad I_1(-R_4) + I_2(R_2 + R_3 + R_4) + I_3(-R_2) = 0$$

$$\textcircled{3} \quad I_2(-R_2) + I_3(R_1 + R_2) + 10 = 0$$

$$1\text{mA}(-1\text{k}) + I_2(3\text{k}) + I_3(-1\text{k}) = 0$$

$$I_2(-1\text{k}) + I_3(2\text{k}) + 10 = 0$$

$$3I_2 - I_3 = 1\text{mA}$$

$$-I_2 + 2I_3 = -10\text{mA}$$

-0 1 correct

-1 4 simple math or sign error

-2 3 multiple errors, substitution, etc.

-4 5 loops have only own current

-6 2 Did sum of voltages, but nothing else, ~~just~~ just " $V_1 + V_2 + V_3 = 0$ "

-9 3  $\Sigma$  can't figure out,  
or completely wrong.