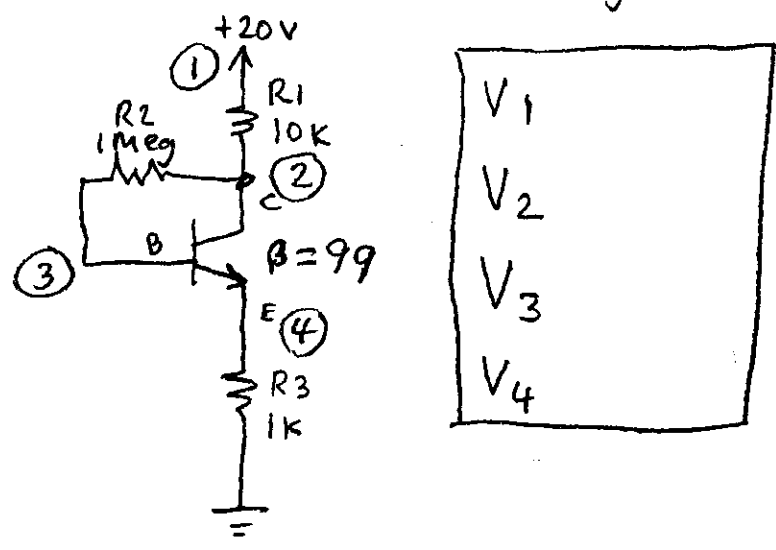



Name \_\_\_\_\_

Find all node voltages;






Did not collect.

The transistor model is:

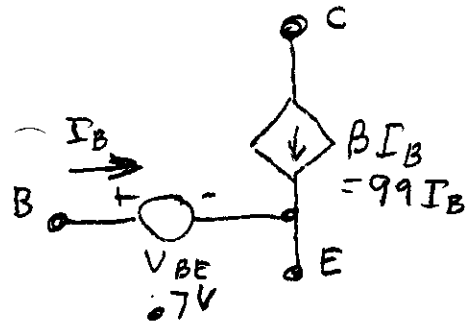

so the circuit with model is:

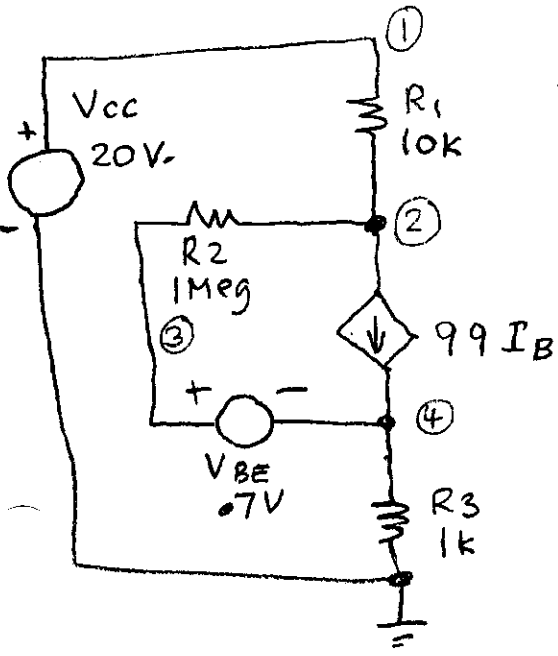

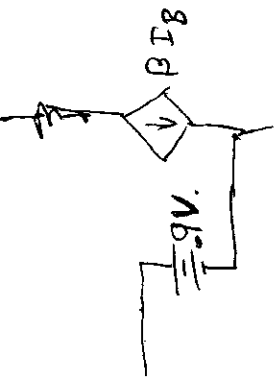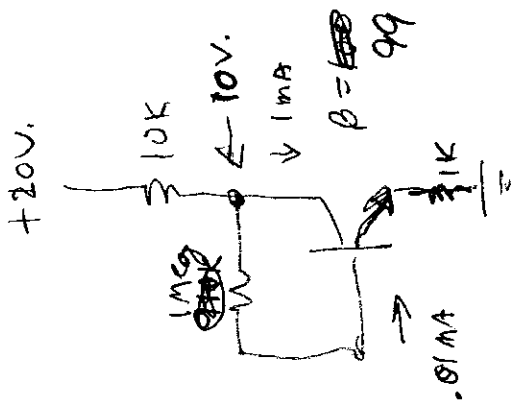


①  $V_1 = V_{cc}$

②  $\frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + \beta I_B = 0$

③  $\frac{V_3 - V_2}{R_2} + \frac{V_4}{R_3} - \beta I_B = 0$

$V_3 = V_4 + V_{BE} \rightarrow V_4 = V_3 - V_{BE}$

$I_B = \frac{V_2 - V_3}{R_2}$

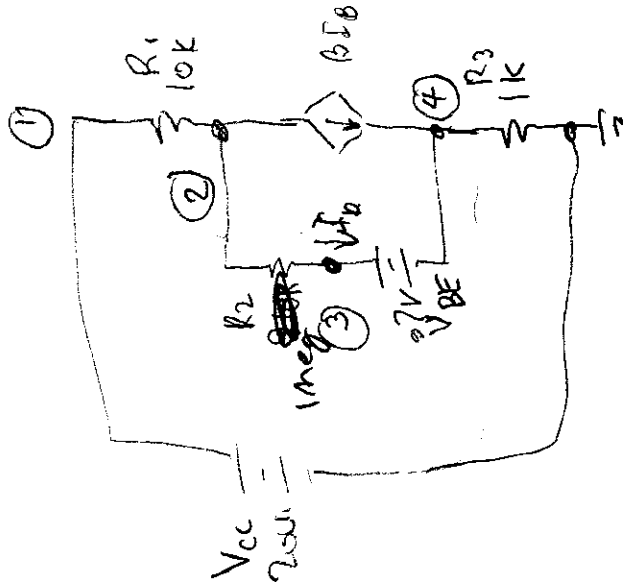

$$\textcircled{2} \frac{V_2 - 20}{10k} + \frac{V_2 - V_3}{1\text{meg}} + \frac{99}{100} \frac{V_2 - V_3}{1\text{Meg}} = 0$$

$$\textcircled{3} \frac{V_3 - V_2}{1\text{meg}} + \frac{V_3 - 0.7}{1k} - \frac{99}{100} \frac{V_3 - V_2}{1\text{meg}} = 0$$

$$\textcircled{2} \frac{V_2 - 20}{10k} + 100 \frac{V_2 - V_3}{1\text{meg}} = 0$$

$$\textcircled{3} 100 \frac{V_3 - V_2}{1\text{meg}} + \frac{V_3 - 0.7}{1k} = 0$$

$$\textcircled{2} \frac{V_2 - 20}{10k} + \frac{V_2 - V_3}{10k} = 0$$

$$\textcircled{3} \frac{V_3 - V_2}{10k} + \frac{V_3 - 0.7}{1k} = 0$$

$$\textcircled{2} V_2 - 20 + V_2 - V_3 = 0$$

$$\textcircled{3} V_3 - V_2 + 10V_3 - 7 = 0$$

$$\textcircled{2} 2V_2 = V_3 + 20$$

$$V_2 = \frac{V_3 + 20}{2} = \frac{V_3}{2} + 10$$

$$\textcircled{3} 11V_3 - V_2 - 7 = 0$$

$$11V_3 - \frac{V_3}{2} - 10 - 7 = 0$$

$$\rightarrow 10.5V_3 - 17 = 0$$

$$V_3 = \frac{17}{10.5} = 1.619$$

$$\rightarrow V_2 = \frac{1.619}{2} + 10$$

$$= 10.81$$

$$V_4 = 0.919$$