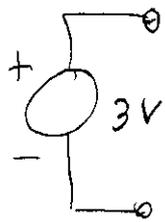



# Time varying voltages and currents

5A  
①

-- and superposition




3V


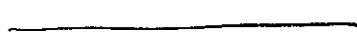


← always the same

0

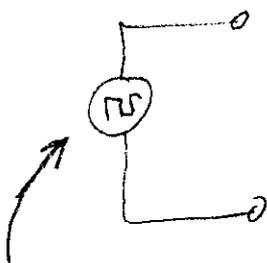

3V p-p  
100Hz  
Square wave!

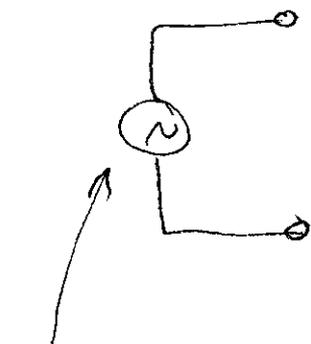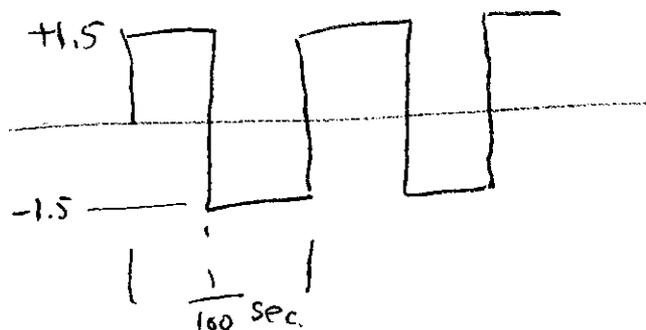

$2 \cos(2\pi 100 t)$

