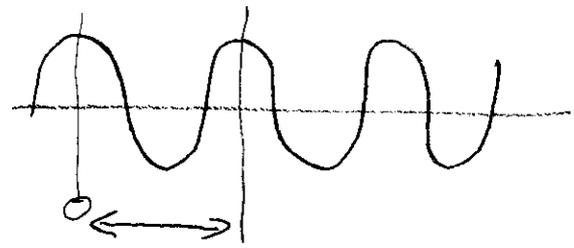


# Sinusoidal Steady State Analysis (Chapter 9)

7A  
①

Representation:  $\rightarrow$  

Frequency = "cycles per second"  
"F" (Hertz).

$$= \frac{1}{\text{period}}$$

Example: period = 0.001 second

Frequency = 1000 Hz.

HW: p. 465  
Ch. 9.  
1, 2, 3, 4,  
6, 7, 8

" $\omega$ " = radians per second  
(omega)  $= 2\pi f$

$$\omega = 2\pi 1000 \text{ Hz}$$

$$= 6283 \text{ rad/sec.}$$

Often we write it as " $2\pi f$ "  
and don't reduce it —  
so the example stays " $2\pi 1000$ ".


$$V(t) = \cos(2\pi f t)$$

$$= \cos(2\pi 1000 t) \quad \leftarrow \text{This example.}$$



Phase

A sinusoid may be shifted in time --

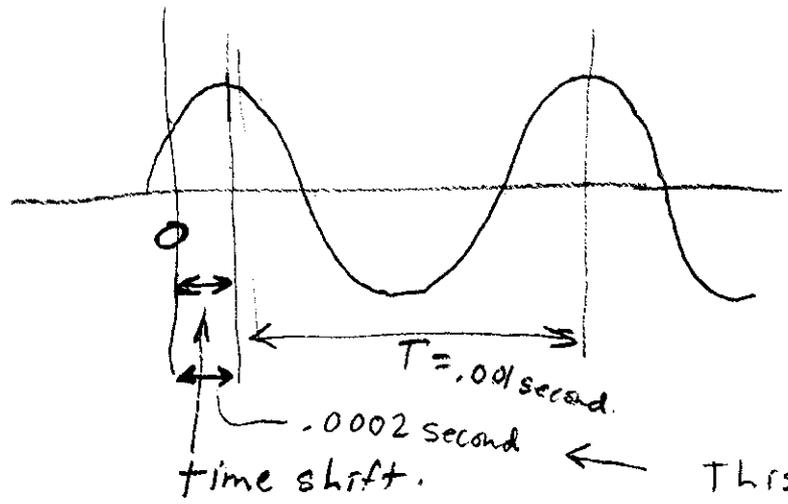

This cosine wave is delayed .0002 second.  
 $\Delta t = -.0002$  second.

Phase angle

Express the delay as an angle

in degrees:  $\frac{-.0002}{.001} = \frac{\phi}{360}$

$$\frac{\Delta t}{T} = \frac{\phi}{360}$$

$$\phi = 360 \left( \frac{-.0002}{.001} \right) = -72 \text{ degrees}$$

$$\phi = 360 \frac{\Delta t}{T}$$

$$\phi = -72 \text{ degrees}$$

$$= 360 f \Delta t$$

↑  
 negative = delayed  
 = shifted to right

positive = advanced  
 = shifted to left

in radians:  $\frac{-.0002}{.001} = \frac{\phi}{2\pi}$

$$\frac{\Delta t}{T} = \frac{\phi}{2\pi}$$

$$\phi = 2\pi \left( \frac{-.0002}{.001} \right) =$$

$$\phi = 2\pi \frac{\Delta t}{T} = 2\pi f \Delta t = \omega \Delta t$$

$$= -2\pi (.2) \text{ radians} = -1.25 \text{ radians}$$

← often we leave it like this.

Combined --

$$v(t) = V_m \cos(\omega t + \phi)$$

↑ radians.

Be consistent --

This example

$$v(t) = 10 \cos\left(\underbrace{2\pi 1000 t}_{\omega} + \underbrace{(2\pi 1000)(.0002)}_{\phi}\right)$$

Sometimes written:

$$v(t) = 10 \cos(2\pi 1000 (t + .0002))$$

$$v(t) = V_m \cos(\omega (t + \Delta t))$$

# "Phasor" notation

7A  
5

There are other ways to represent this -----

Math diversion ---

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Think of  $\cos$  as the real part  
 $\sin$  as imaginary part  
of the exponential.

$$\begin{aligned} V(t) &= V_m \cos(\omega t + \phi) \\ &= V_m \operatorname{Real}(e^{j(\omega t + \phi)}) \\ &= V_m \operatorname{Real}(e^{j\omega t} e^{j\phi}) \end{aligned}$$

$$= \operatorname{Real} \left( \underbrace{V_m}_{\text{Amplitude}} \underbrace{e^{j\phi}}_{\text{Phase}} \underbrace{e^{j\omega t}}_{\text{Frequency + time}} \right)$$

This term carries ---  
Frequency  
+ time

Phase

Amplitude

For AC steady state analysis —

We use one frequency

so don't include it in the analysis —

$$\begin{aligned}
 \text{big } V \rightarrow V &= V_m e^{j\phi} \\
 \text{means phasor representation} &= V_m (\cos \phi + j \sin \phi)
 \end{aligned}$$

Usually, we use a short form:

$$V_m \angle \phi$$

The example continued ---

$$v(t) = 10 \cos(2\pi 1000t - 1.25 \text{ rad})$$

$$V = 10 \angle -1.25 \text{ rad}$$

$$\text{or } 10 \angle -72^\circ$$

$$= 10 (\cos(-72^\circ) + j \sin(-72^\circ))$$

$$= 10 (0.309 - j 0.951)$$

To get  $v(t)$ , multiply by  $e^{j\omega t}$   
but we won't.

# Complex math, Phasor math

7A  
7

## Addition, subtraction -

use rectangular coordinates:

$$\begin{aligned} & 1 \angle 0^\circ + 2 \angle 45^\circ \\ & = (1 + j0) + (1.414 + j1.414) \\ & = 2.414 + j1.414 \\ & = 2.798 \angle 30.36^\circ \end{aligned}$$

## Multiplication

Multiply the amplitudes,

Add the angles.

then wrap angles to  $\pm 180^\circ$

$$1 \angle 0^\circ \times 2 \angle 45^\circ = 2 \angle 45^\circ$$

$$1 \angle 45^\circ \times 2 \angle 45^\circ = 2 \angle 90^\circ$$

$$3 \angle 70^\circ \times 2 \angle 45^\circ = 6 \angle 115^\circ$$

$$3 \angle 110^\circ \times 2 \angle 140^\circ = 6 \angle 250^\circ = 6 \angle -110^\circ$$

## Division

Divide the amplitudes, subtract the angles

then wrap to  $\pm 180^\circ$

$$\frac{5 \angle 70^\circ}{2 \angle 15^\circ} = \frac{5}{2} \angle 70^\circ - 15^\circ = 2.5 \angle 55^\circ$$

# The passive elements

## Resistors

voltage and current are in phase.

$$V = IR$$

↓

$$V = R (I_{max} \cos(\omega t + \phi_i))$$

$\phi_i =$  phase of current

No phase change

## Capacitor

$$i = C \frac{dv}{dt}$$

$$v = V_m \cos(\omega t + \phi_v)$$

phase of voltage

time domain → 
$$i = C \frac{d}{dt} V_m \cos(\omega t + \phi_v)$$

$$= C V_m \frac{d}{dt} \cos(\omega t + \phi_v)$$

$$= C V_m (-\omega \sin(\omega t + \phi_v))$$

$$= -\omega C V_m \underbrace{(-\sin(\omega t + \phi_v))}_{\substack{\uparrow \\ \text{"j"}}$$

AC phasor

↓ 
$$I = j\omega C V$$

$$V = \frac{1}{j\omega C} I$$

$$= \frac{I}{\omega C} \angle -90^\circ$$

↑ 
$$Z_C = \frac{1}{j\omega C}$$

voltage lags current by  $90^\circ$

Notation: It is common to use to represent  $j\omega$  --

"S"

$$Z_C = \frac{1}{sC}$$

current leads voltage by  $90^\circ$

Inductor

$$V = L \frac{di}{dt}$$

$$i = I_m \cos(\omega t + \phi_i)$$

$$V = L \frac{d}{dt} I_m \cos(\omega t + \phi_i)$$

$$V = L I_m \frac{d}{dt} \cos(\omega t + \phi_i)$$

$$= L I_m (-\omega \sin(\omega t + \phi_i))$$

$$= \omega L I_m \underbrace{(-\sin(\omega t + \phi_i))}_{"j"}$$

$$V = \underbrace{j\omega L I}_{Z_L = j\omega L} = \omega L I \angle 90^\circ$$

↑  
Voltage leads current  
by 90°  
(current lags voltage  
by 90°)

$$Z_L = j\omega L = sL$$

Impedance

$$Z = \frac{V}{I}$$

V and I are complex

Resistance

$$R = \text{Real}(Z)$$


Reactance

$$X = \text{Imag}(Z)$$

$$Z = R + jX$$

	Z Impedance	R Resistance	X Reactance
Resistor	R	R	0
Capacitor	$\frac{1}{j\omega C}$	0	$-\frac{1}{\omega C}$
Inductor	$j\omega L$	0	$\omega L$

# A simple circuit -- (voltage divider)

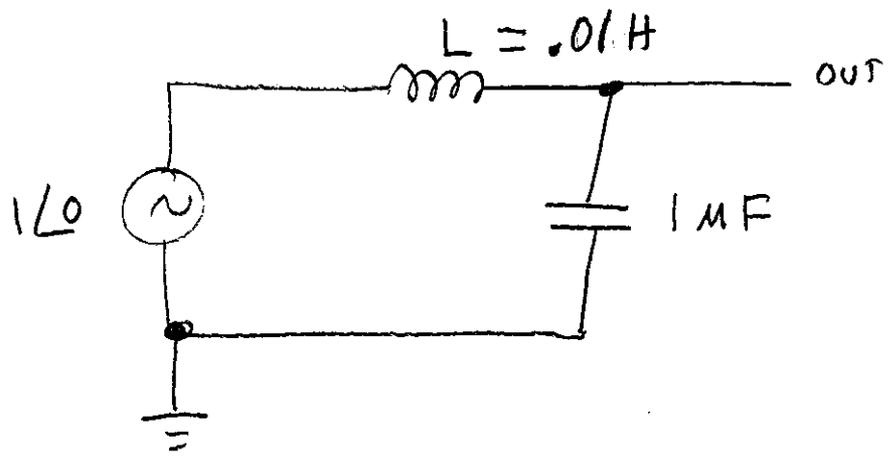


What is  $V_{out}$ ?

It depends on frequency --

$$V_{OUT} = V_{IN} \frac{Z_{shunt}}{Z_{series} + Z_{shunt}}$$
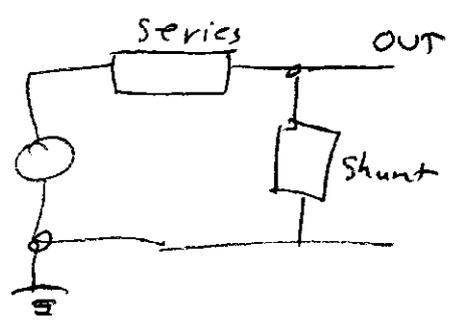
$$= V_{IN} \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$






$$= V_{IN} \frac{1}{j^2 \omega^2 LC + 1} = \frac{1}{-\omega^2 LC + 1}$$

Sub values --

$$V_{OUT} = \frac{1}{-\omega^2 (-01)(10^{-6}) + 1} = \frac{1}{-\omega^2 (10^{-8}) + 1}$$

$\omega$	$V_{OUT}$
0	1
$\infty$	0
$10^4$	$\frac{1}{0}$
$10^3$	$\frac{1}{-10^{-2} + 1}$
$10^5$	$\frac{1}{-10^2 + 1}$

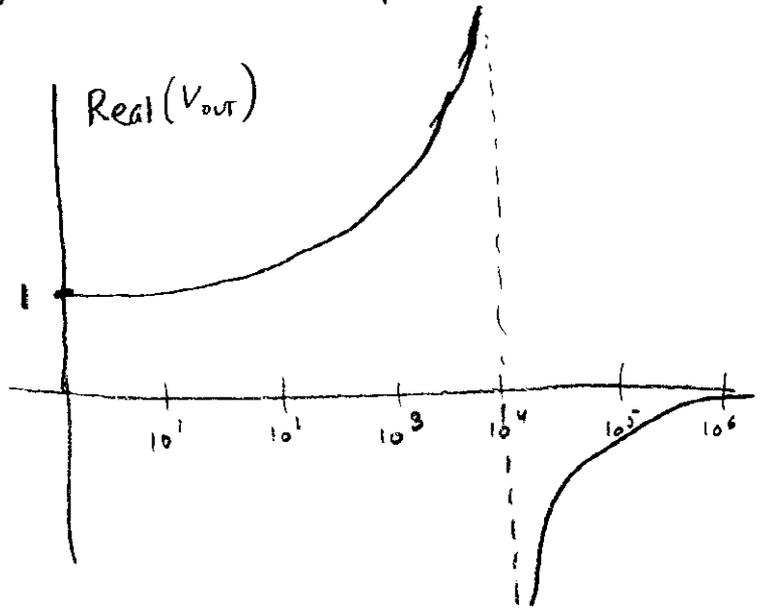

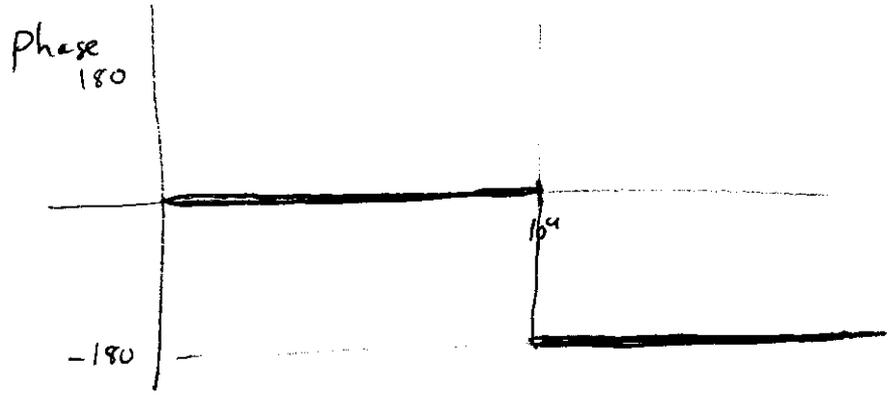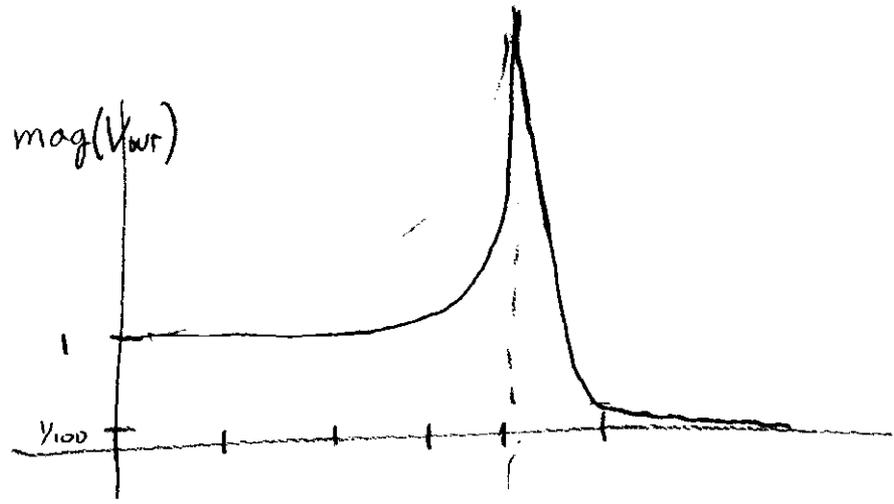

### AC simulation --

The netlist is the same

Commands:

print AC V(nodes) Vp(nodes)  
 ↑ voltage magnitude ↑ voltage phase

print AC I(R1) IP(R1)  
 ↑ current magnitude ↑ current phase

AC 60  
 ↑ Frequency, in Hz.

AC start stop step  
 AC 100 1000 100  
 100 Hz to 1000 Hz  
 in 100 Hz steps.