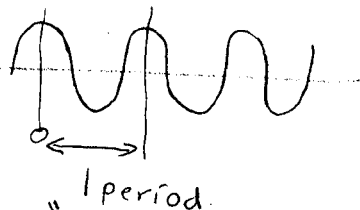


Sinusoidal Steady State Analysis (Chapter 9)

7A
①

Representation: →



Frequency = "cycles per second"
"F" (Hertz).

$$= \frac{1}{\text{period}}$$

Example: period = .001 second
Frequency = 1000 Hz.

" ω " = radians per second
(omega) = $2\pi f$

$$\omega = 2\pi 1000 \text{ Hz} \\ = 6283 \text{ rad/sec.}$$

Often we write it as " $2\pi f$ "
and don't reduce it —
so the example stays " $2\pi 1000$ ".


$$V(t) = \cos(2\pi f t) \\ = \cos(2\pi 1000 t) \quad \leftarrow \text{This example.}$$

Hw: p. 465
Ch. 9.
1, 2, 3, 4,
6, 7, 8

Amplitude:

$$V_m \cos(\omega t)$$

↑
peak amplitude

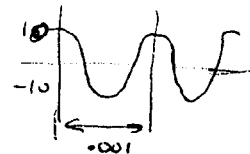

$$\leftarrow 10 \cos(2\pi 1000 t)$$

peak voltage = V_m

"peak-to-peak" = $2V_m$

"RMS" voltage — the "effective value"

"root mean square"

Used in computing power.

(Our 10 volt sine wave
contains less power than 10 volts DC.)

$$V_{RMS} = \sqrt{\underbrace{\frac{1}{T} \int_{t_0}^{t_0+T}}_{\text{Root Mean}} \underbrace{V_m^2 \cos^2(\omega t) dt}_{\text{Square}}}$$

$$= \frac{V_m}{\sqrt{2}}$$

$$V_m = 10$$


$$\Rightarrow V_{RMS} = 7.07$$

7A
②

Phase

A sinusoid may be shifted in time --

7A
③

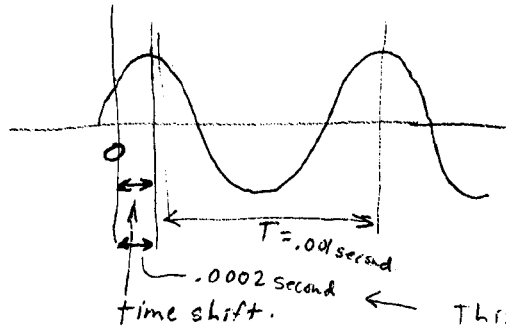

This cosine wave is
delayed .0002 second.
 $\Delta t = -.0002$ second

Phase angle

Express the delay as an angle

in degrees: $\frac{-.0002}{.001} = \frac{\phi}{360}$

$$\frac{\Delta t}{T} = \frac{\phi}{360}$$

$$\phi = 360 \frac{\Delta t}{T}$$

$$= 360 f \Delta t$$

$$\phi = 360 \left(\frac{-.0002}{.001} \right) = -72 \text{ degrees}$$

$$\phi = -72 \text{ degrees}$$



negative = delayed

= shifted to right

positive = advanced

= shifted to left

in radians: $\frac{-.0002}{.001} = \frac{\phi}{2\pi}$

$$\frac{\Delta t}{T} = \frac{\phi}{2\pi}$$

$$\phi = 2\pi \left(\frac{-.0002}{.001} \right) =$$

$$\phi = 2\pi \frac{\Delta t}{T} = 2\pi f \Delta t$$
$$= \omega \Delta t$$

$$= -2\pi (.2) \text{ radians} \leftarrow \text{often we leave it like this.}$$
$$= -1.25 \text{ radians}$$

Combined --

$$v(t) = V_m \cos(\omega t + \phi)$$

↑ radians

Be consistent --

This example

$$v(t) = 10 \cos \left(\underbrace{2\pi 1000 t}_{\omega} + \underbrace{(2\pi 1000)(-.0002)}_{\phi} \right)$$

Sometimes written:

$$v(t) = 10 \cos (2\pi 1000 (t + .0002))$$

$$v(t) = V_m \cos (\omega (t + \Delta t))$$

7A
④

"Phasor" notation

7A
⑤

There are other ways to represent this -----

Math diversion ---

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Think of \cos as the real part
 \sin as imaginary part
of the exponential.

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \phi) \\ &= V_m \operatorname{Real}(e^{j(\omega t + \phi)}) \\ &= V_m \operatorname{Real}(e^{j\omega t} e^{j\phi}) \end{aligned}$$

$$= \operatorname{Real}(\underbrace{V_m}_{\text{amplitude}} \underbrace{e^{j\phi}}_{\text{Phase}} \underbrace{e^{j\omega t}}_{\text{This term carries --- Frequency + time}})$$

For AC steady state analysis ---

7A
⑥

We use one frequency

so don't include it in the analysis ---

$$\begin{aligned} \rightarrow V &= V_m e^{j\phi} \\ &= V_m (\cos \phi + j \sin \phi) \end{aligned}$$

big V means phasor representation

Usually, we use a short form:

$$V_m \angle \phi$$

The example continued ---

$$v(t) = 10 \cos(2\pi 1000t - 1.25 \text{ rad})$$

$$V = 10 \angle -1.25 \text{ rad}$$

$$\text{or } 10 \angle -72^\circ$$

$$= 10 (\cos(-72^\circ) + j \sin(-72^\circ))$$

$$= 10 (0.309 - j 0.951)$$

To get $v(t)$, multiply by $e^{j\omega t}$
but we won't.

7A got this far.

7B ↓

Complex math, phasor math

Addition, subtraction -

use rectangular coordinates:

$$\begin{aligned}
& 1 \angle 0^\circ + 2 \angle 45^\circ \\
&= (1 + j0) + (1.414 + j1.414) \\
&= 2.414 + j1.414 \\
&= 2.798 \angle 30.36^\circ
\end{aligned}$$

Multiplication

Multiply the amplitudes, Add the angles, then wrap angles to $\pm 180^\circ$

$$\begin{aligned}
1 \angle 0^\circ \times 2 \angle 45^\circ &= 2 \angle 45^\circ \\
1 \angle 45^\circ \times 2 \angle 45^\circ &= 2 \angle 90^\circ \\
3 \angle 70^\circ \times 2 \angle 45^\circ &= 6 \angle 115^\circ \\
3 \angle 110^\circ \times 2 \angle 140^\circ &= 6 \angle 250^\circ = 6 \angle -110^\circ
\end{aligned}$$

Division

Divide the amplitudes, subtract the angles, then wrap to $\pm 180^\circ$

$$\frac{5 \angle 70^\circ}{2 \angle 15^\circ} = \frac{5}{2} \angle 70^\circ - 15^\circ = 2.5 \angle 55^\circ$$

7A
7

The passive elements

7A
8

Resistors

voltage and current are in phase.

$$\begin{aligned}
V &= IR \\
&\downarrow \\
V &= R(I_m \cos(\omega t + \phi_i))
\end{aligned}$$

$\phi_i = \text{phase of current}$

No phase change

Capacitor

$$\begin{aligned}
i &= C \frac{dv}{dt} \\
V &= V_m \cos(\omega t + \phi_v)
\end{aligned}$$

$\phi_v = \text{phase of voltage}$

time domain →

$$\begin{aligned}
i &\approx C \frac{d}{dt} V_m \cos(\omega t + \phi_v) \\
&= C V_m \frac{d}{dt} \cos(\omega t + \phi_v) \\
&= C V_m (-\omega \sin(\omega t + \phi_v)) \\
&= \omega C V_m \underbrace{(-\sin(\omega t + \phi_v))}_{\substack{\uparrow \\ \text{"j"}}}
\end{aligned}$$

AC phasor ↓

$$I = j\omega C V$$

$$\begin{aligned}
V &= \frac{1}{j\omega C} I \\
&\uparrow Z_C = \frac{1}{j\omega C} = \frac{I}{\omega C} \angle -90^\circ
\end{aligned}$$

Notation: It is common to use "s" to represent $j\omega$... $Z_C = \frac{1}{sC}$

↑ voltage lags current by 90°
current leads voltage by 90°

Inductor

$$v = L \frac{di}{dt}$$

7A
9

$$i = I_m \cos(\omega t + \phi_i)$$

$$v = L \frac{d}{dt} I_m \cos(\omega t + \phi_i)$$

$$v = L I_m \frac{d}{dt} \cos(\omega t + \phi_i)$$

$$= L I_m (-\omega \sin(\omega t + \phi_i))$$

$$= \omega L I_m \underbrace{(-\sin(\omega t + \phi_i))}_{"j"}$$

$$V = j\omega L I = \omega L I \angle 90^\circ$$

\uparrow
 $Z_L = j\omega L$
 $= sL$

\uparrow
 Voltage leads current by 90°
 (Current lags voltage by 90°)

Impedance $Z = \frac{V}{I}$ V and I are complex

Resistance $R = \text{Real}(Z)$


Reactance $X = \text{Imag}(Z)$

$$Z = R + jX$$

	Z Impedance	R Resistance	X Reactance
Resistor	R	R	0
Capacitor	$\frac{1}{j\omega C}$	0	$-\frac{1}{\omega C}$
Inductor	$j\omega L$	0	ωL

A simple circuit -- (voltage divider)

1A
10

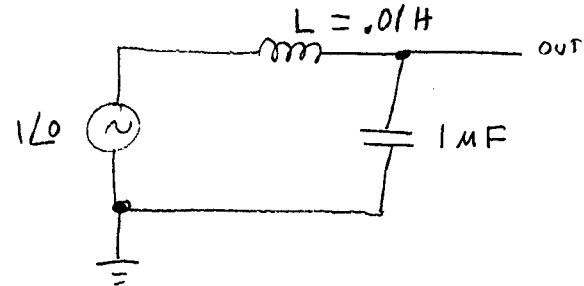


What is V_{out} ?

It depends on frequency --

$$V_{out} = V_{in} \frac{Z_{shunt}}{Z_{series} + Z_{shunt}}$$
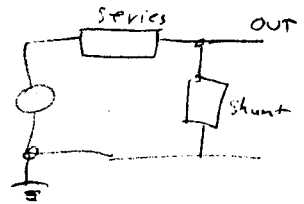
$$= V_{in} \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$




$$= V_{in} \frac{1}{j^2 \omega^2 LC + 1} = \frac{1}{-\omega^2 LC + 1}$$

Sub values -



$$V_{out} = \frac{1}{-\omega^2 (0.01)(10^{-6}) + 1} = \frac{1}{-\omega^2 (10^{-8}) + 1}$$

ω	V_{out}
0	1
∞	0
10^4	$\frac{1}{0}$
10^3	$\frac{1}{-10^{-2} + 1}$
10^5	$\frac{1}{-10^2 + 1}$

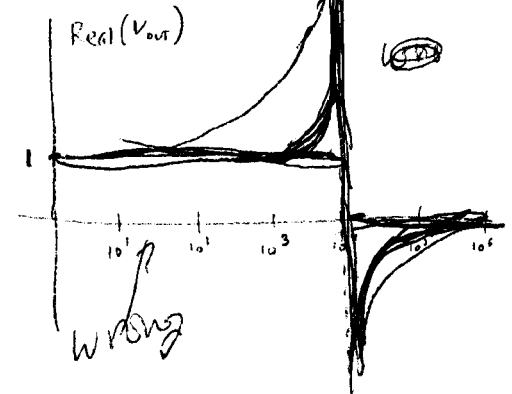

$\frac{1}{\omega C}$ is called "resonant frequency" (radians)

7a
⑪

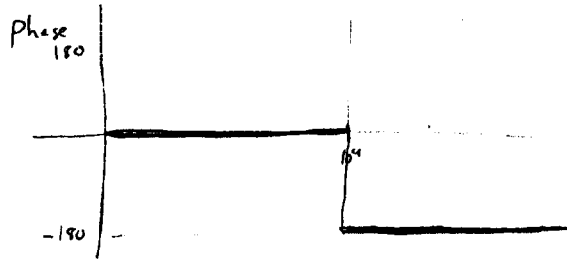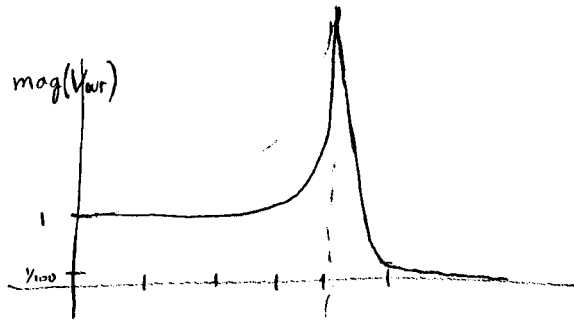

AC simulation --

The netlist is the same

Comments:

```

print AC V(nodes) VP(nodes)
         ↑      ↑
         voltage voltage
         magnitude phase
  
```

```

print AC I(R1) IP(R1)
         ↑      ↑
         current current
         magnitude phase
  
```

```

AC 60
  ↑
  Frequency, in Hz.
  
```

```

AC start stop step
AC 100 1000 100
  100 Hz to 1000 Hz
  in 100 Hz steps.
  
```

$V1$ (1 0) 5 ← DC value
 $V1$ (1 0) AC 1 ← AC value
 $V1$ (1 0) DC 5 AC 1
 both.

