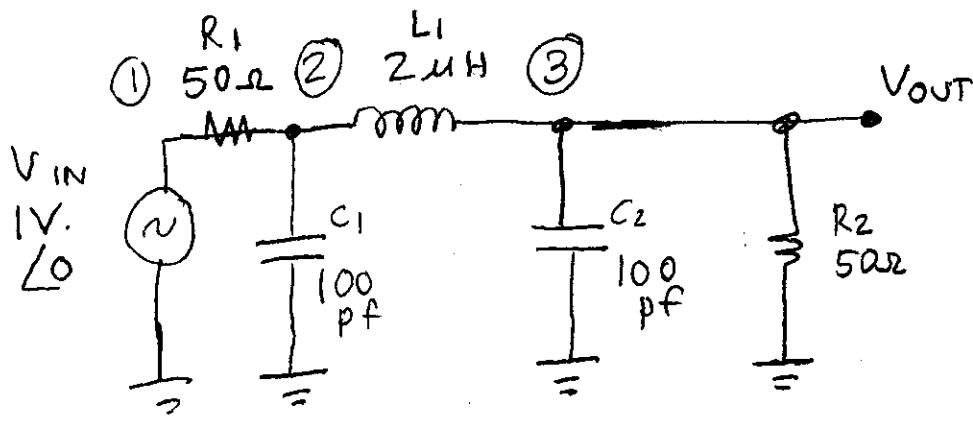


Nodal Analysis with inductors and capacitors

7C
①

It's just like resistors, except it is frequency dependent and the numbers are complex.



What is :

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} ?$$

$$\left(= \frac{V_3}{V_1} \right)$$

$$① \quad V_1 = V_{\text{IN}}$$

$$② \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{Z_{C_1}} + \frac{V_2 - V_3}{Z_{L_1}} = 0$$

$$③ \quad \frac{V_3 - V_2}{Z_{L_1}} + \frac{V_3}{Z_{C_2}} + \frac{V_3}{R_2} = 0$$

HW p. 469 ...
ch. 9
22, 23, 34
36, 38

$$② \quad \frac{V_2 - V_1}{R_1} + j\omega C_1 V_2 + \frac{V_2 - V_3}{j\omega L_1} = 0$$

$$③ \quad \frac{V_3 - V_2}{j\omega L_1} + j\omega C_2 V_3 + \frac{V_3}{R_2} = 0$$

Shorthand: Let "s" = $j\omega$

②

$$② \frac{V_2 - V_1}{R_1} + sC_1 V_2 + \frac{V_2 - V_3}{sL_1} = 0$$

$$③ \frac{V_3 - V_2}{sL_1} + sC_2 V_3 + \frac{V_3}{R_2} = 0$$

$$② V_1 \left(-\frac{1}{R_1} \right) + V_2 \left(\frac{1}{R_1} + sC_1 + \frac{1}{sL_1} \right) + V_3 \left(-\frac{1}{sL_1} \right) = 0$$

$$③ V_2 \left(-\frac{1}{sL_1} \right) + V_3 \left(\frac{1}{sL_1} + sC_2 + \frac{1}{R_2} \right) = 0$$

Solve ③ for V_2 :-

$$V_2 \left(\frac{1}{sL_1} \right) = V_3 \left(\frac{1}{sL_1} + sC_2 + \frac{1}{R_2} \right)$$

$$V_2 = V_3 (sL_1) \left(\frac{1}{sL_1} + sC_2 + \frac{1}{R_2} \right)$$

$$= V_3 \left(1 + s^2 L_1 C_2 + \frac{sL_1}{R_2} \right)$$

Sub in ②

$$V_1 \left(-\frac{1}{R_1} \right) + V_3 \left[\left(1 + s^2 L_1 C_2 + \frac{sL_1}{R_2} \right) \left(\frac{1}{R_1} + sC_1 + \frac{1}{sL_1} \right) - \frac{1}{sL_1} \right] = 0$$

$$V_1 \left(\frac{1}{R_1} \right) = V_3 \left[\left(\quad \quad \quad \right) \left(\quad \quad \quad \right) - \frac{1}{sL_1} \right]$$

$$\frac{V_3}{V_1} = \frac{\frac{1}{R_1}}{\left(1 + s^2 L_1 C_2 + \frac{sL_1}{R_2} \right) \left(\frac{1}{R_1} + sC_1 + \frac{1}{sL_1} \right) - \frac{1}{sL_1}}$$

We could plug in values, $s = j\omega$, here -..

7c
③

If you need only one frequency -..

Example: $\omega = 10^8$

$$R_1 = R_2 = 50$$

$$Z_{C1} = Z_{C2} = \frac{1}{j\omega C} = \frac{1}{j(10^8)(10^{-10})} = \frac{1}{j10^{-2}}$$

$$Z_L = j\omega L = j(10^8)(2 \times 10^{-6}) = j(2 \times 10^2) = j200$$

$$\textcircled{2} \quad \frac{V_2 - V_1}{50} + \frac{V_2}{\frac{1}{j10^{-2}}} + \frac{V_2 - V_3}{j200} = 0$$

$$\textcircled{3} \quad \frac{V_3 - V_2}{j200} + \frac{V_3}{\frac{1}{j10^{-2}}} + \frac{V_3}{50} = 0$$

$$\textcircled{2} \quad \frac{V_2 - V_1}{50} + \frac{V_2}{-j100} + \frac{V_2 - V_3}{j200} = 0$$

$$\textcircled{3} \quad \frac{V_3 - V_2}{j200} + \frac{V_3}{-j100} + \frac{V_3}{50} = 0$$

$$\textcircled{2} \quad 4(V_2 - V_1) + \frac{2V_2}{-j} + \frac{V_2 - V_3}{j} = 0$$

$$\textcircled{3} \quad \frac{V_3 - V_2}{j} + \frac{2V_3}{-j} + 4V_3 = 0$$

7C
④

$$\textcircled{2} \quad 4(V_2 - V_1) + j2V_2 - j(V_2 - V_3) = 0$$

$$\textcircled{3} \quad -j(V_3 - V_2) + j2V_3 + 4V_3 = 0$$

$$\textcircled{2} \quad V_1(-4) + V_2(4 + j2 - j) + V_3(j) = 0$$

$$\textcircled{3} \quad V_2(j) + V_3(-j + j2 + 4) = 0$$

$$\textcircled{2} \quad V_1(-4) + V_2(4 + j) + V_3(j) = 0$$

$$\textcircled{3} \quad V_2(j) + V_3(4 + j) = 0$$

solve ③ for V_2 : $V_2(-j) = V_3(4 + j)$

$$V_2 = V_3 \frac{4+j}{j}$$

$$= V_3(-j4 - j^2)$$

$$= V_3(1 - j4)$$

sub in ②

$$V_1(-4) + V_3(1 - j4)(4 + j) + V_3(j) = 0$$

$$V_1(-4) + V_3(4 + j - j16 - j^24 + j) = 0$$

$$V_1(-4) + V_3(4 + j - j16 + 4 + j) = 0$$

$$V_1(-4) + V_3(16 - j14) = 0$$

$$V_1(4) = V_3(16 - j14)$$

$$\frac{V_3}{V_1} = \frac{4}{16 - j14} = 14159 + j12389$$

$$= 18814 \angle 41.186^\circ$$