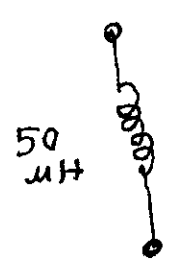
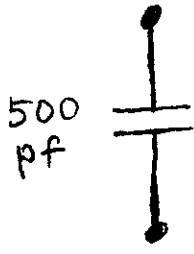
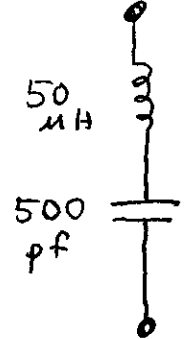
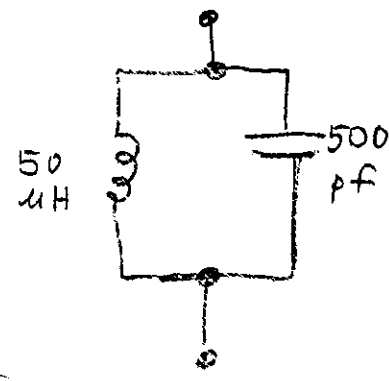


Name \_\_\_\_\_ Key \_\_\_\_\_

Fill in the chart: for  $f = 1 \text{ MHz}$  ( $10^6 \text{ Hz}$ )  
 $\omega = 6.28 \times 10^6$

	Resistance	Reactance	Impedance
 <p>50 <math>\mu\text{H}</math></p>	0	$\omega L$ $= 314$ $100\pi$	$j\omega L$ $j314$ $j100\pi$
 <p>500 pf</p>	0	$-\frac{1}{\omega C}$ $-318$ $\frac{-1}{2\pi f C} =$	$\frac{1}{j\omega C}$ $-j318$
 <p>50 <math>\mu\text{H}</math> 500 pf</p>	0	$X_L + X_C$ $-4$	$-j4$
 <p>50 <math>\mu\text{H}</math> 500 pf</p>	0	$\frac{1}{\frac{1}{X_L} + \frac{1}{X_C}}$ $25 \times 10^3$	$j25 \times 10^3$

all wrong -

almost attendance quiz

2nd time:  
-8 clueless

or  $\omega = f??$   
 -1 got concept pf =  $10^{-9}$ ?  
 -2  $Z$  not X, pf =  $10^{-9}$ ?  
 -4 mixed wrong, got something correct  
 -6 all wrong or bland