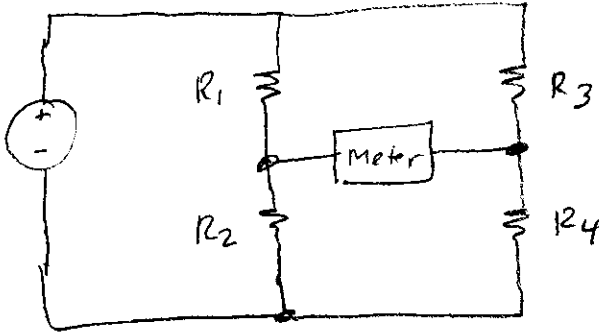


A practical circuit --

The Wheatstone bridge


Idea: Use a voltage source and two voltage dividers.
Measure between them.




HW -
P. 47, CH 9
45, 46, 49, 50, 51
56, 57

The meter reads zero
when $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

Example:

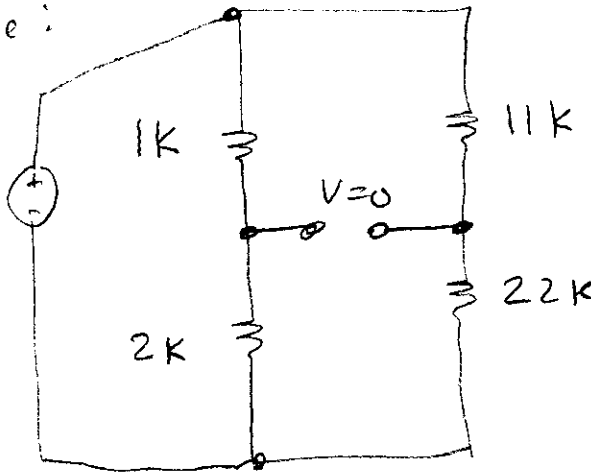


↑
in balance

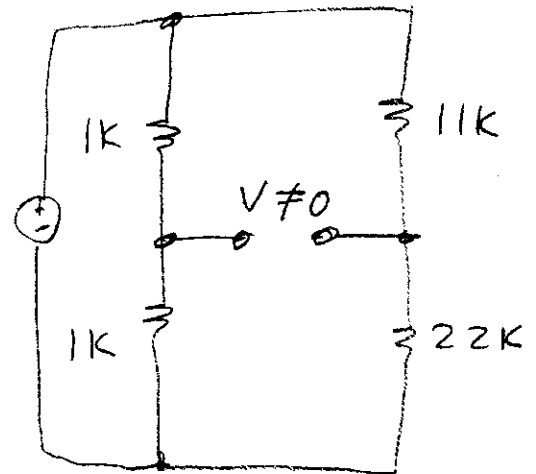

↑
not in balance

Using it to measure resistance

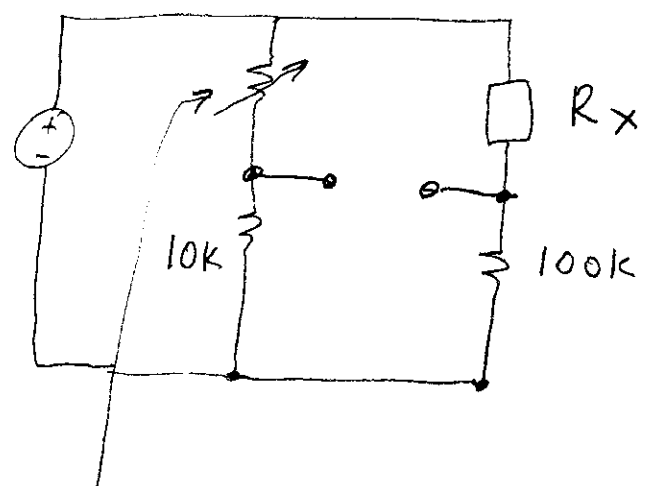


This variable resistor is calibrated - -

suppose it is 4.7k

What is the value of Rx?

To measure capacitance


Make one leg out of capacitors - -

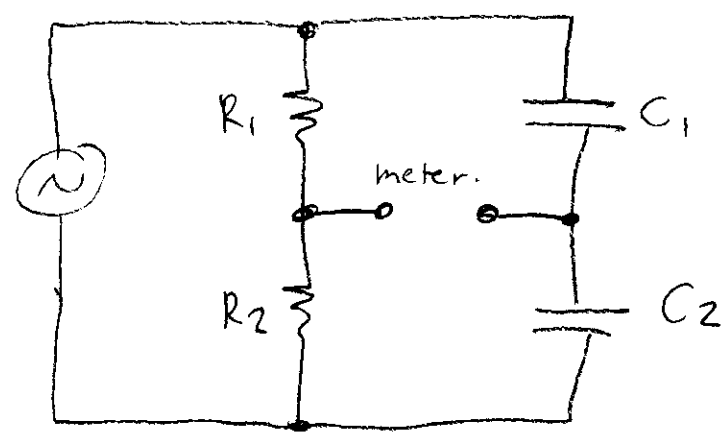

in balance when $\frac{R_1}{R_2} = \frac{C_2}{C_1}$


↑
note inversion.

Example:

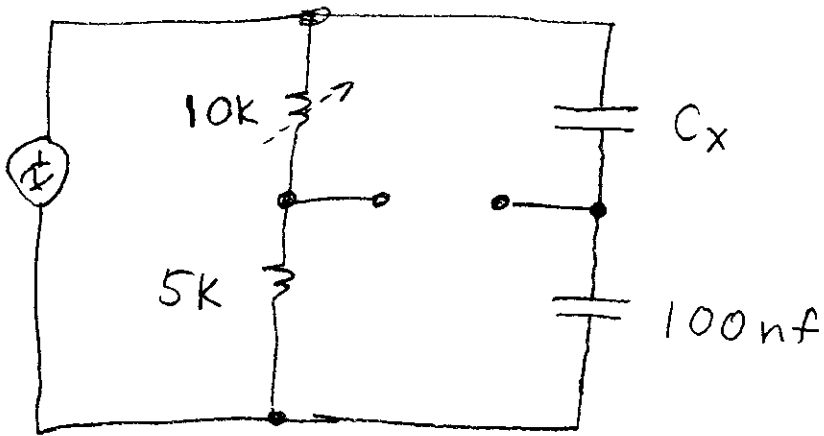


The bridge is in balance.
What is C_x ?

There are other configurations:

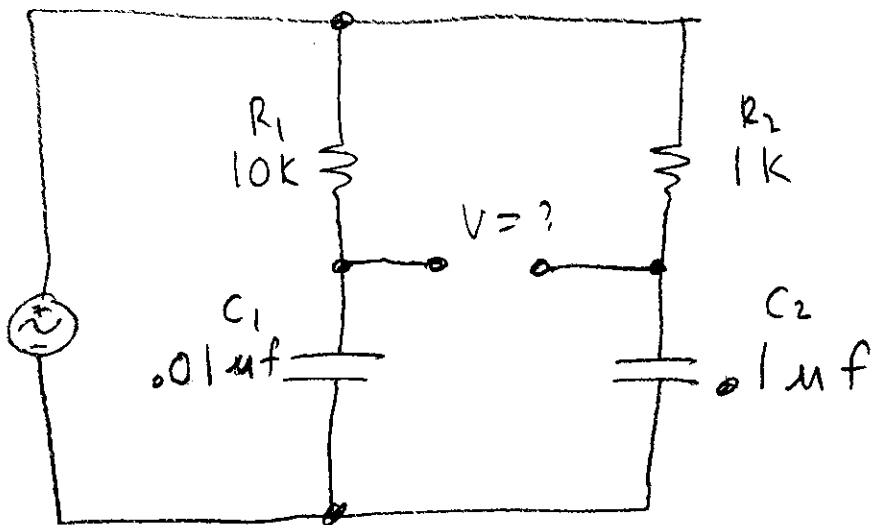

$$V = 0 \quad \text{when} \quad \frac{R_1}{C_1} = \frac{R_2}{C_2}$$

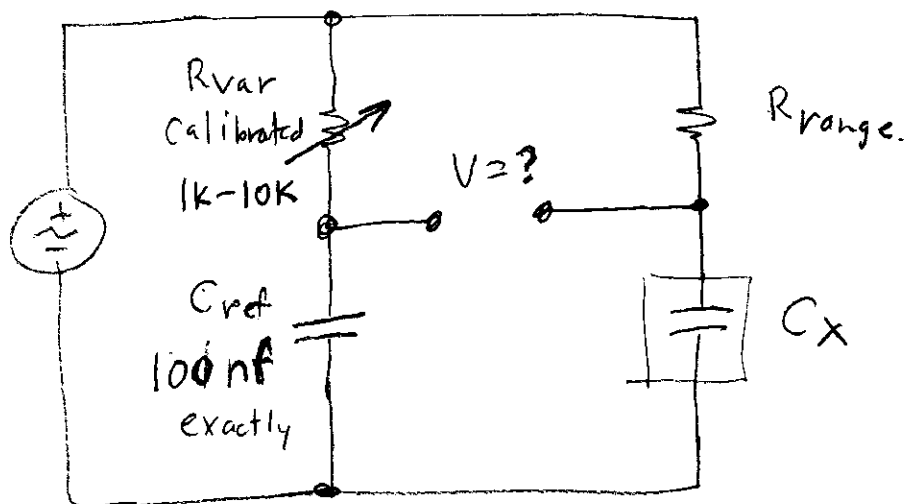→ can measure large range of capacitor with one precision capacitor




Set R_{range} to: 1Ω , 10Ω , 100Ω , 1K , 10K , 100K , 1Meg , 10Meg
(decades) exactly.

What is the value of C_x ?

R_{range}	R_{var}	C_x
10K	10K	100 nF
10K	1K	10 nF
10K	5K	50 nF
100K	5K	
1Meg	5K	
10Meg	5K	
1K	5K	
100 Ω	5K	
10 Ω	5K	
1 Ω	5K	

Measuring inductors

The obvious way --

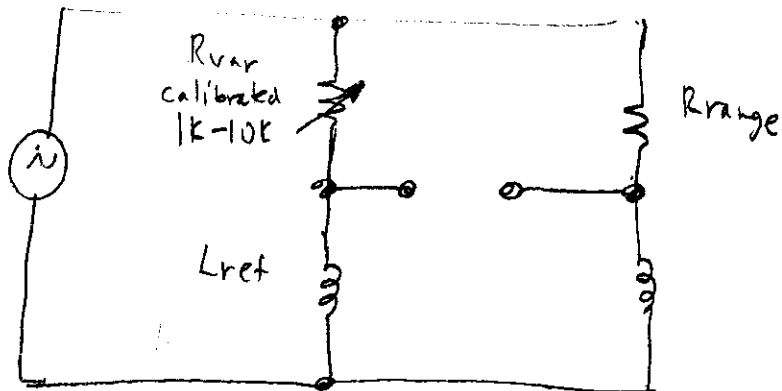

Using a capacitor --

