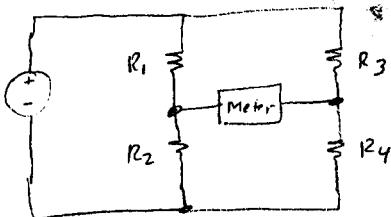


A practical circuit --

The Wheatstone bridge

Idea: Use a voltage source and two voltage dividers. Measure between them.




HW -
P. 478, CH9
45, 46, 49, 50, 51
56, 57


The meter reads zero

$$\text{when } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Example:

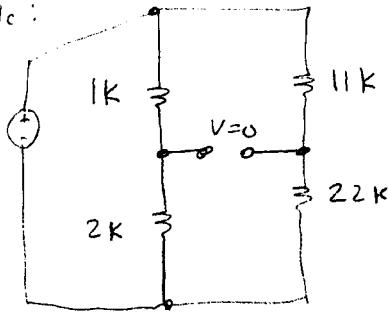

in balance

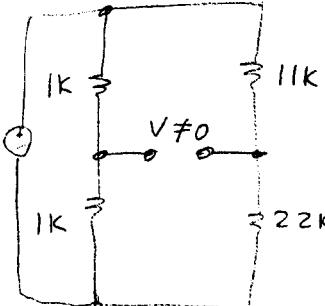


not in balance

84
①

Using it to measure resistance

84
②

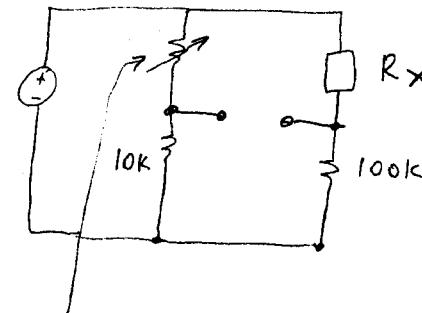


This variable resistor is calibrated --

Suppose it is 4.7 K

What is the value of R_x ?

To measure capacitance


Make one leg out of capacitors ..

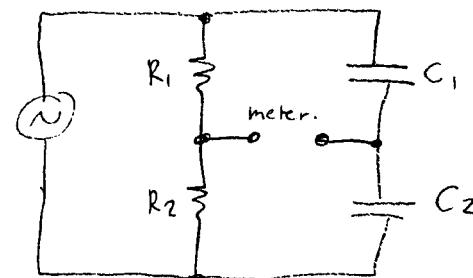

in balance when $\frac{R_1}{R_2} = \frac{C_2}{C_1}$

↑ note inversion.

Example:

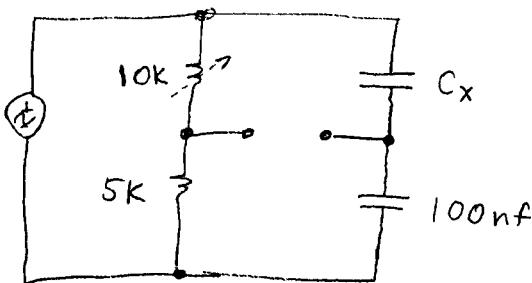


8A
③


The bridge is in balance.

What is C_x ?

There are other configurations:

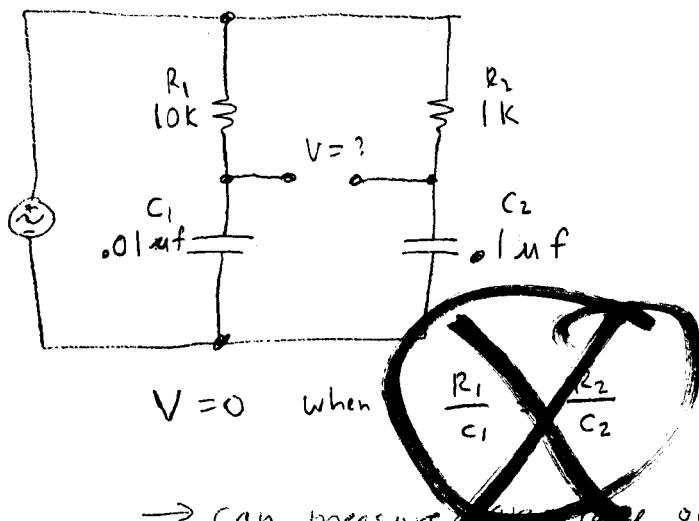

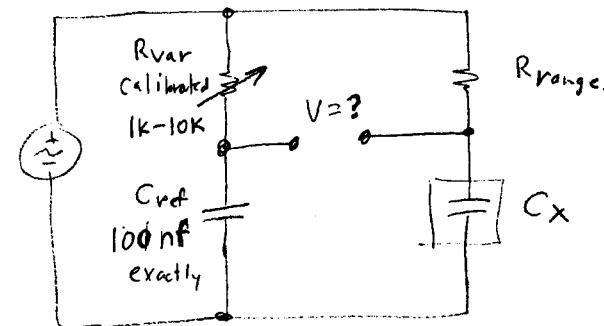→ Can measure ~~any range of~~ capacitor with one precision capacitor



8A
④

Set R_{range} to: 1 Ω , 10 Ω , 100 Ω , 1K, 10K, 1Meg, 10 Meg (decades) exactly.


What is the value of C_x ?

R_{range}	R_{var}	C_x
10 K	10K	100nF
10K	1K	10 nF
10K	5K	50 nF
100K	5K	
1Meg	5K	
10 Meg	5K	
1K	5K	
100 Ω	5K	
10 Ω	5K	
1 Ω	5K	

)
Measuring inductors

The obvious way --

8A
⑤

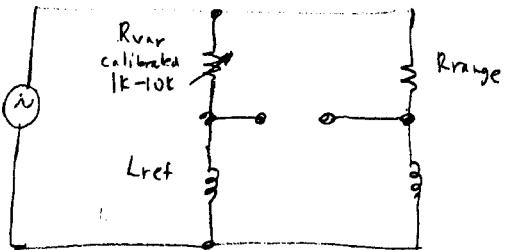

Using a capacitor --

