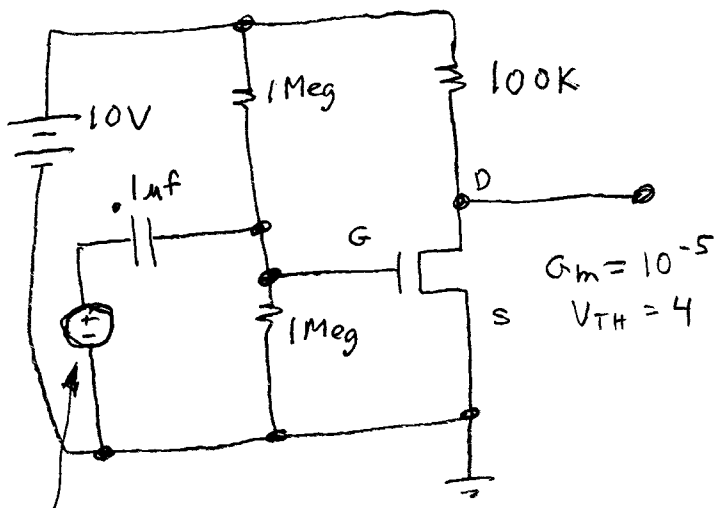


A sample circuit - using superposition -
AC and DC solution:


From a quiz ---



$.001 \cos(2\pi 1000t)$
 $.001 \cos(2\pi 10t)$

either of these

Equivalent circuit:

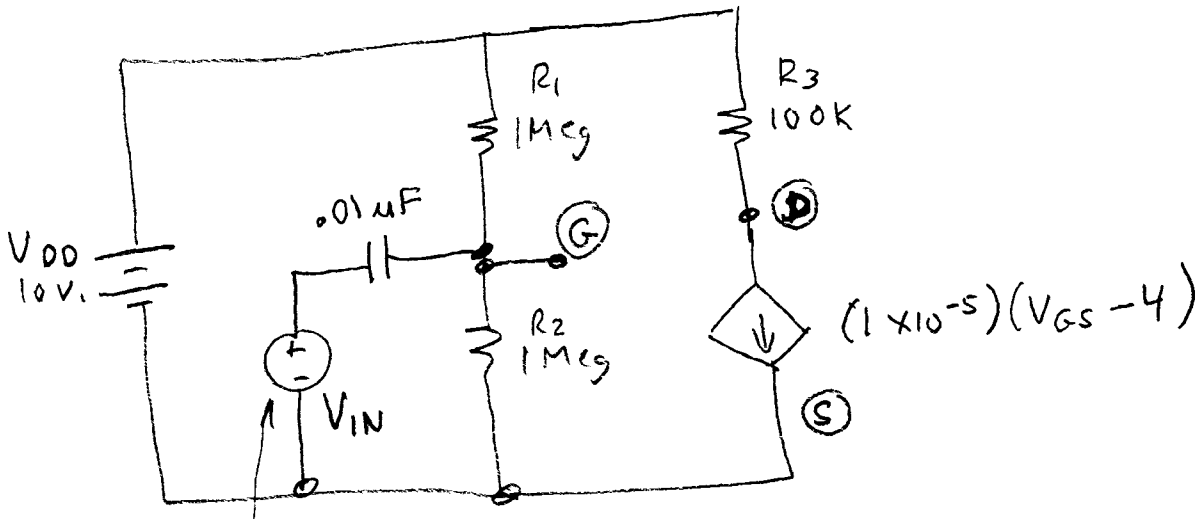


$.001 \cos(2\pi f t)$
 $f = \begin{cases} 1000 \text{ Hz} \\ 10 \text{ Hz} \end{cases}$
 Call it ".001 ∠0"

What is V_D ?
 What is $\frac{V_D}{V_{IN}}$?
 'AC component?

Idea: use superposition -

8B
2

First set AC sources to zero - solve.

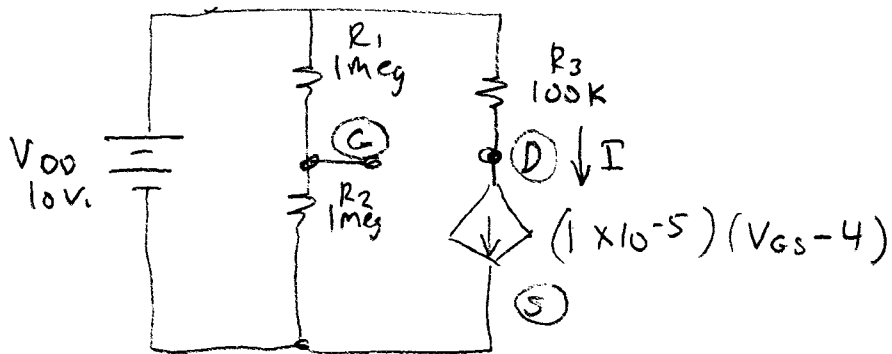

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{10^6}{10^6 + 10^6} 10 = 5$$

$$I = (10^{-5})(V_{GS} - 4) = (10^{-5})(5 - 4) = 10^{-5} \text{ A}$$


$$V_{R3} = I R = (10^{-5})(10^5) = 1$$

$$V_{DS} = V_{DD} - V_{R3} = 9$$



(repeat of a
quiz from a
few weeks ago)

Now, set the DC sources to zero, --
 leaving only the AC sources--.

8B
 3

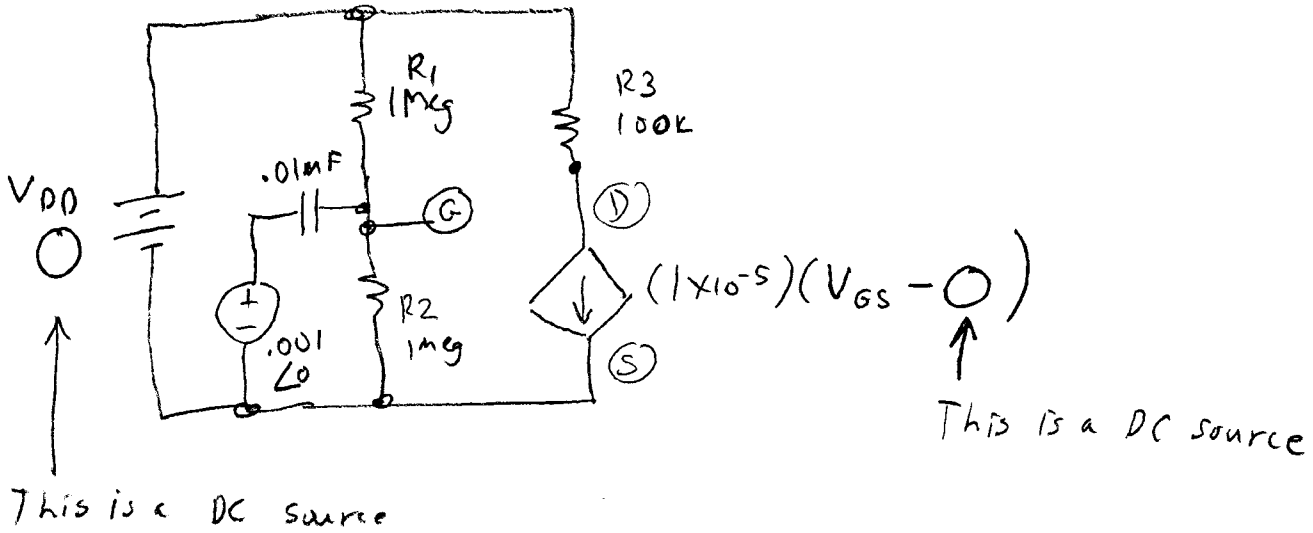

Leaving---

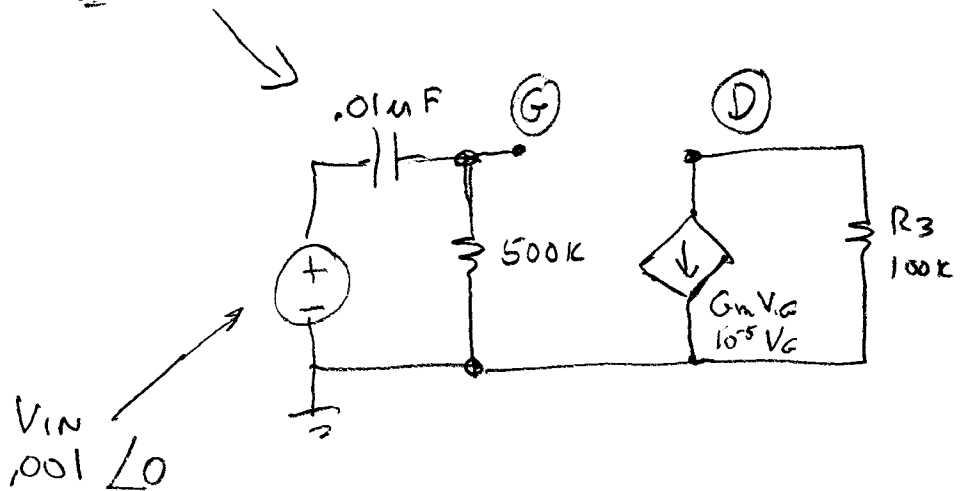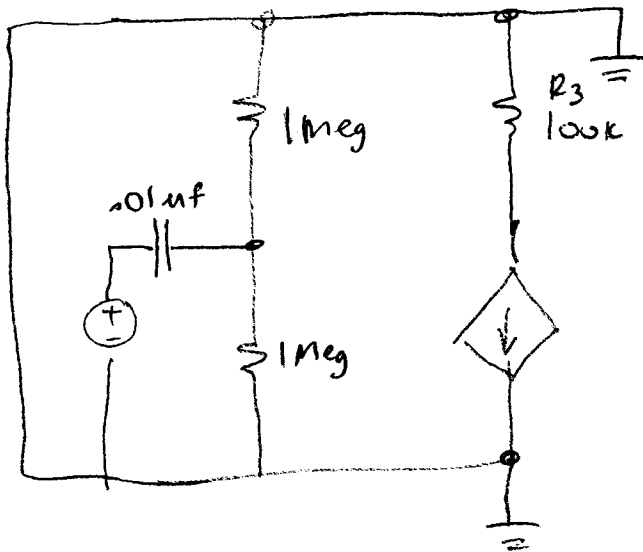

Node equations:

$$\textcircled{G} \quad \frac{V_G}{R} + \frac{V_G - V_{IN}}{\frac{1}{j\omega C}} = 0$$

Solve for $\frac{V_G}{V_{IN}}$

$$\frac{V_G}{R} + \frac{V_G}{\frac{1}{j\omega C}} - \frac{V_{IN}}{\frac{1}{j\omega C}} = 0$$

$$\frac{V_G}{R} + j\omega C V_G - j\omega C V_{IN} = 0$$

$$V_G \left(\frac{1}{R} + j\omega C \right) = V_{IN} (j\omega C)$$

$$\frac{V_G}{V_{IN}} = \frac{j\omega C}{\frac{1}{R} + j\omega C}$$

$$\frac{V_G}{V_{IN}} = \frac{j\omega C R}{1 + j\omega C R}$$

$$\textcircled{D} \quad G_m V_G + \frac{V_D}{R_3} = 0$$

solve for $\frac{V_D}{V_G}$

$$\frac{V_D}{R_3} = -G_m V_G$$

$$\frac{V_D}{V_G} = -G_m R_3$$

$$= -(10^5)(10^5)$$

$$\frac{V_D}{V_G} = -1$$



bad example --
this value is only
by chance

Combine ---

$$\frac{V_D}{V_{IN}} = \frac{V_D}{V_G} \cdot \frac{V_G}{V_{IN}} = - \frac{j\omega C R}{1 + j\omega C R}$$

$$\begin{aligned} \omega = 2\pi 1000: & \quad j\omega C R = j\omega (.01 \times 10^{-6})(5 \times 10^5) \\ & \quad \rightarrow = j5 \quad \frac{j5}{1+j5} = .961 + j.192 \\ & \quad \quad \quad = .98 \angle .197 \text{ rad} \\ \omega = 2\pi 10: & \quad \rightarrow = j.05 \quad = .98 \angle 110^\circ \end{aligned}$$

$$\begin{aligned} \frac{j.05}{1+j.05} &= .0024938 + j.0498753 \\ &= .0499 \angle 1.52 \text{ rad.} \\ &= .0499 \angle 87.138^\circ \end{aligned}$$