

Power — real and imaginary

Review — DC power --

$$\text{Volts} \times \text{Amps}$$



$$I = \frac{V}{R} = \frac{10}{2} = 5 \text{ A}$$

$$P_R = 10 \times 5 = 50 \text{ watts}$$

$$P_{\text{source}} = 10 \times (-5) = -50 \text{ watts}$$



$$I = \frac{V}{R} = \frac{-10}{2} = -5 \text{ A}$$

$$P_R = (-10) \times (-5) = 50 \text{ watts}$$

$$P_{\text{source}} = (-10) \times (5) = -50 \text{ watts.}$$

Conventions:

Component polarity — assume a direction —


one node is +, other is -

current flows into the + node.

power dissipated is positive

power sourced is negative

Power with time varying signals -

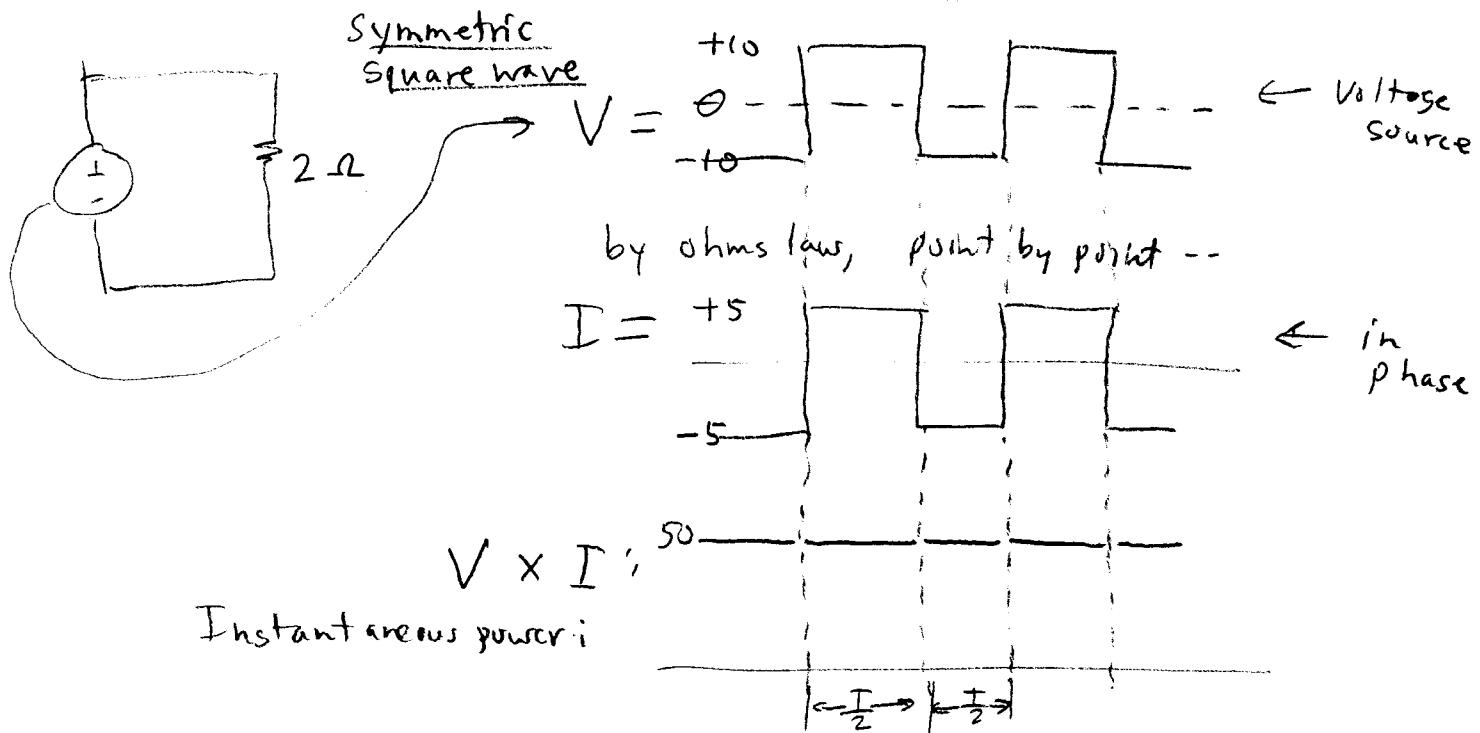


Instantaneous power:

$$\text{Average power} = \frac{1}{T} \int_{T_0}^{T_0+T} P_i dt = 50 \text{ watts}$$

over a cycle.

A symmetric square wave:

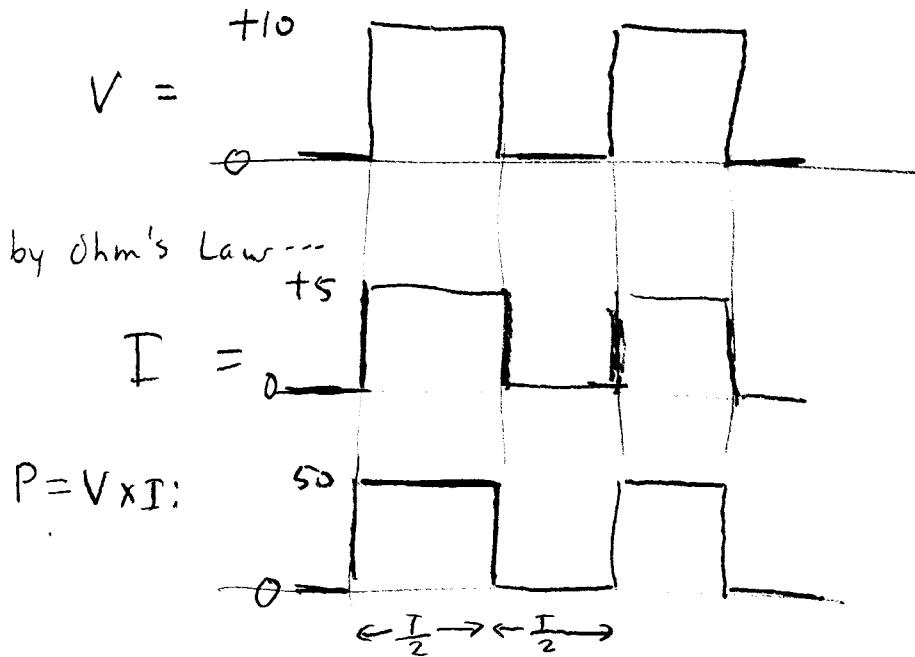


Average power =


$$P_{AV} = \frac{1}{T} \int_{T_0}^{T_0+T} P_i dt$$

$$\frac{1}{T} \left[ \int_0^{\frac{T}{2}} 5 dt + \int_{\frac{T}{2}}^T 0 dt \right] = 2.5 \text{ watts.}$$


For sine wave:

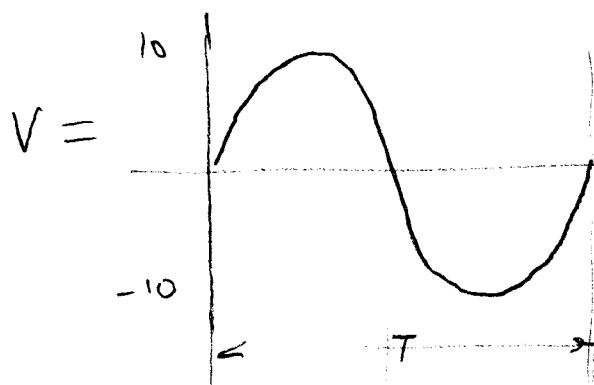
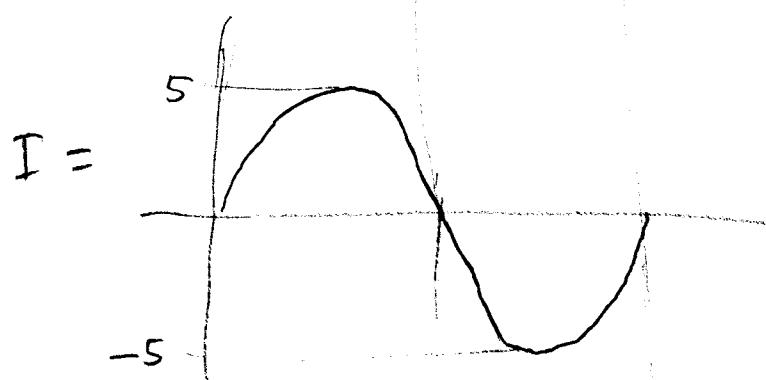
$$V = 10 \sin(\omega t) \\ = 10 \angle -90^\circ$$


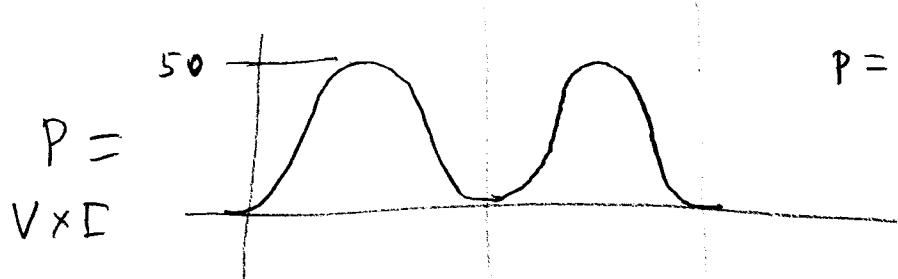
$$I = \frac{V}{R} \\ = \frac{10 \sin(\omega t)}{2} \\ = 5 \sin(\omega t) \\ = 5 \angle -90^\circ$$



$$P = 10 \sin(\omega t) \times 5 \sin(\omega t) \\ = 50 \sin^2(\omega t) \\ = 25 - 25 \cos(2\omega t)$$

$$P_{AV} = \frac{1}{T} \int_{T_0}^{T_0+T} P_i dt = \frac{1}{T} \int_{T_0}^{T_0+T} 25 - 25 \cos(2\omega t) dt \\ = \frac{1}{T} \left( \int 25 dt + \int -25 \cos(2\omega t) dt \right)$$

9C  
④

$$\begin{aligned}
 P_{Av} &= \frac{1}{T} \int_{T_0}^{T_0+T} p_i dt = \\
 &= \frac{1}{T} \int_{T_0}^{T_0+T} 25 + 25 \sin(2\omega t) dt \\
 &= \frac{1}{T} \left( \int_{T_0}^{T_0+T} 25 dt + \int_{T_0}^{T_0+T} 25 \sin(2\omega t) dt \right) \\
 &\quad \downarrow \\
 &= \frac{1}{T} \int_{T_0}^{T_0+T} 25 dt = 0 \\
 &= 25
 \end{aligned}$$

Rule: For sine wave:


$$P = \frac{V_{peak} \times I_{peak}}{2}$$

$$= \frac{V_{peak}}{\sqrt{2}} \times \frac{I_{peak}}{\sqrt{2}}$$

$$\frac{I_{peak}}{\sqrt{2}} = I_{rms}$$


$$\frac{V_{peak}}{\sqrt{2}} = V_{rms}$$

Capacitive load -- Sine wave

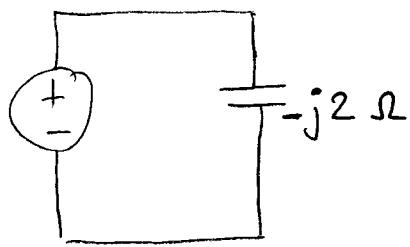


$$V = 10 \sin(\omega t)$$

$$= 10 \angle -90^\circ$$

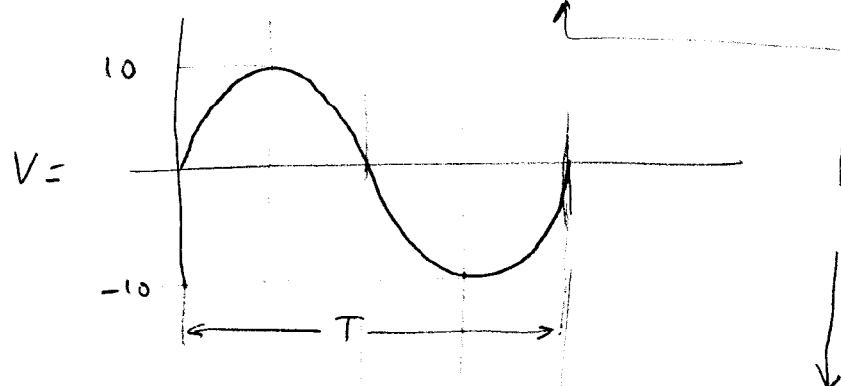

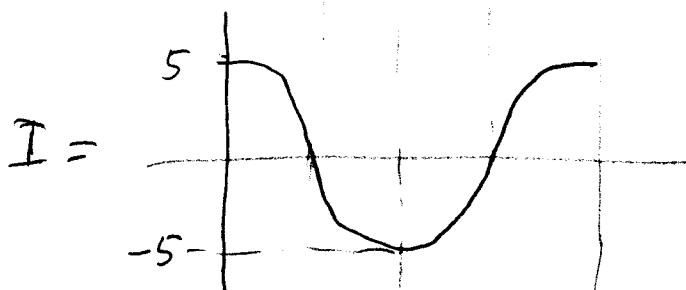
$$I = \frac{V}{Z} = \frac{10 \angle -90^\circ}{2 \angle -90^\circ} = 5 \angle 0^\circ$$



Current leads voltage by  $90^\circ$   
 $= 5 \cos(\omega t)$

$$P = V \times I$$

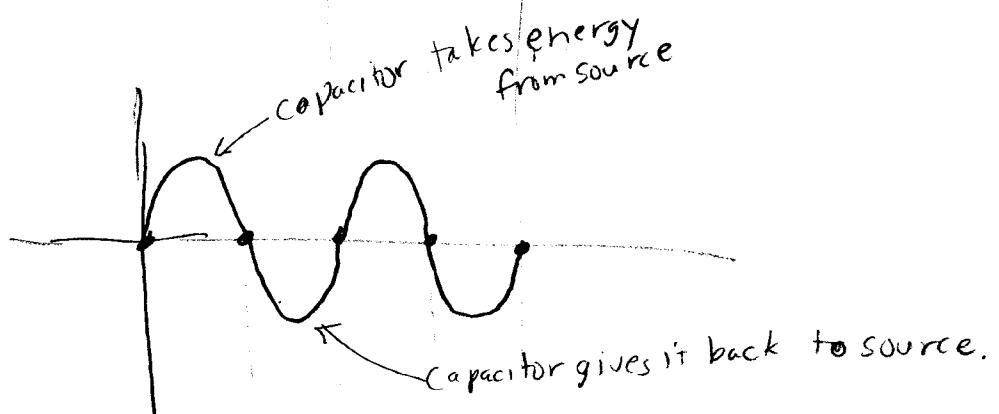

$$P = 10 \sin(\omega t) \times 5 \cos(\omega t)$$

$$= 50 (\sin(\omega t) \cos(\omega t))$$

$$= 50 \times \frac{1}{2} (\sin(2\omega t))$$


$$= 25 \sin(2\omega t)$$

$$P_{AV} = \frac{1}{T} \int_{T_0}^{T_0+T} 25 \sin(2\omega t) dt = 0 \leftarrow \text{real power} = 0$$

In general :

$$P = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta)$$

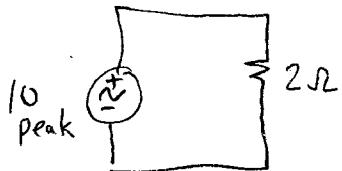↑  
phase angle between  
voltage and current



$$V = 10 \sin(\omega t)$$

$$V_{\text{RMS}} = 7.07$$

$$I = 5 \sin(\omega t)$$

$$I_{\text{RMS}} = 3.54$$

$$\theta = 90^\circ - 90^\circ = 0$$

$$P = (7.07)(3.54)(\cos(0))$$

$$= 25 \text{ watts.}$$



$$V = 10 \sin(\omega t)$$

$$V_{\text{RMS}} = 7.07$$

$$I = 5 \cos(\omega t)$$

$$I_{\text{RMS}} = 3.54$$

$$\theta = 0 - 90^\circ = -90^\circ$$

$$P = (7.07)(3.54)(\cos(-90^\circ))$$

$$= 0 \text{ watts.}$$

New terms:

$$\text{Power factor} = \cos(\theta)$$

↑  
angle between voltage  
and current

$$\text{Real power} = V_{\text{Rms}} I_{\text{Rms}} \cos(\theta)$$

The actual amount of power to do work.

Units: watts.

$$\text{Apparent power} = V_{\text{Rms}} I_{\text{Rms}}$$

→ Misleading number that you get  
if you ignore phase

Units: Volt-amps "VA"

$$\text{Imaginary power} = V_{\text{Rms}} I_{\text{Rms}} \sin(\theta)$$


→ You think it is power, but it isn't.

It can cause a lot of trouble.

Units: Voltamps reactive "VAR"

Try this one:

9C  
8

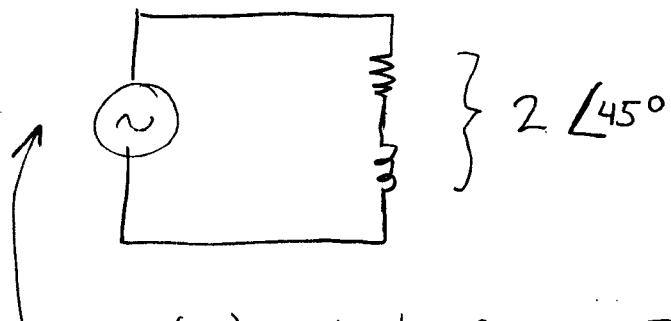

$$V = 10 \sin(\omega t) = 10 \angle -90^\circ \quad I = \frac{V}{Z} = \frac{10 \angle -90^\circ}{2 \angle 45^\circ} = 5 \angle -135^\circ$$

$$V_{RMS} = 7.07$$

$$I_{RMS} = 3.54$$

$$\theta = (-90) - (-135) = 45^\circ \quad \cos(\theta) = .707$$

Real power

$$P = VI \cos(\theta) = (7.07)(3.54)(.707)$$

$$= 17.67 \text{ watts} \leftarrow \begin{matrix} \text{only real power} \\ \text{is in watts.} \end{matrix}$$

$$\text{Apparent power} = VI = 25 \frac{\text{VA}}{\text{k}} \quad \begin{matrix} \text{volt-amps} \\ \text{Don't say} \\ \underline{\text{watts}} \end{matrix}$$

$$\text{Imaginary power} = VI \sin(\theta)$$

$$= (7.07)(3.54)(.707)$$

$$= 17.67 \frac{\text{VAR}}{\text{k}} \quad \begin{matrix} \text{volt-amps} \\ \text{reactive.} \\ \text{Don't say} \\ \underline{\text{watts}} \end{matrix}$$

$$\text{Power factor} = \cos(\theta) = .707$$