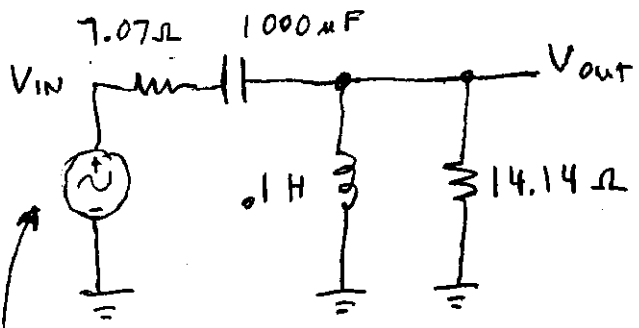


Find the phasor representation of the circuit,

and  $V_{in}$  and  $V_{out}$  in both phasor and time-domain representations.




$1 \cos(141.4t + \frac{\pi}{2})$

$\omega = 141.4$   
 $f = 22.5 \text{ Hz}$


Hint:  $\sqrt{2} = 1.414$        $\frac{1}{\sqrt{2}} = 0.707$

$Z_C = \frac{1}{j\omega C} = \frac{1}{j(141.4)(.001)} = -j7.07$

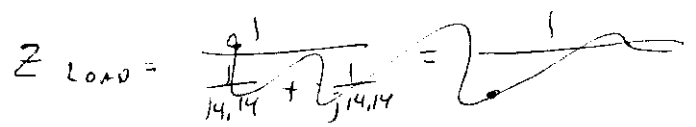$Z_L = j\omega L = j(141.4)(.1) = j14.14$



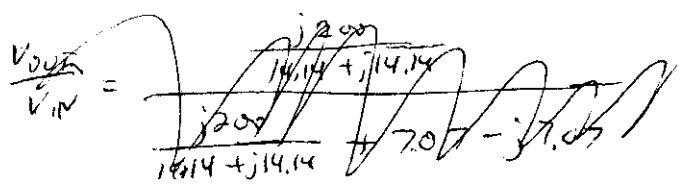$Z_{Load} = \frac{Z_L Z_R}{Z_L + Z_R} = \frac{(j14.14)(14.14)}{14.14 + j14.14} = \frac{j200}{14.14 + j14.14}$



$\frac{V_{OUT}}{V_{IN}} = \frac{7.07 + j7.07}{7.07 + j200 + 7.07 - j7.07} = \frac{7.07 + j7.07}{14.14} = \frac{10 \angle 45^\circ}{14.14 \angle 0} = 0.707 \angle 45^\circ$

$V_{OUT} = (0.707 \angle 45^\circ)(1 \angle 90^\circ) = 0.707 \angle 135^\circ$

Phasor representation of circuit

$V_{IN}(\text{time domain}) = 1 \cos(141.4t + \frac{\pi}{2})$   
 $V_{IN}(\text{phasor}) = 1 \angle \frac{\pi}{2}$   
 $V_{OUT}(\text{time domain}) = 0.707 \cos(141.4t + \frac{3\pi}{4})$   
 $V_{OUT}(\text{phasor}) = 0.707 \angle 135^\circ$

$\frac{200 \angle 90^\circ}{20 \angle 45^\circ} = 10 \angle 45^\circ = 7.07 + j7.07$

$$\textcircled{3} \quad \frac{V_{out}}{R_1} + \frac{V_{out}}{j\omega C} + \frac{V_{out} - V_2}{\frac{1}{j\omega C}} = 0$$

$$\textcircled{2} \quad \frac{V_2 - V_{out}}{\frac{1}{j\omega C}} + \frac{V_2 - V_{in}}{R_1} = 0$$

---

$$\textcircled{3} \quad V_{out} \left( \frac{1}{R_1} + \frac{1}{j\omega C} + j\omega C \right) - V_2 (j\omega C) = 0$$

$$\textcircled{2} \quad V_2 \left( j\omega C + \frac{1}{R_1} \right) - V_{out} (j\omega C) - V_{in} \left( \frac{1}{R_1} \right) = 0$$
$$V_2 = \frac{V_{out} (j\omega C) + V_{in} \left( \frac{1}{R_1} \right)}{j\omega C + \frac{1}{R_1}}$$

$V_{out} ($