

Power factor correction

Often, we need to fix it ---

just add a capacitor or inductor to tune it
to resonance --

Example:

You are setting up a radio transmitter at 1 MHz.
(AM broadcast),

The antenna is too short, so it has an
impedance of $5 - j500$

What voltage and current are necessary
to transmit 5000 Watts?


What is the power factor?

How can we fix it?

What voltage and current are required now?

Hw -
10.39

Equivalent circuit:

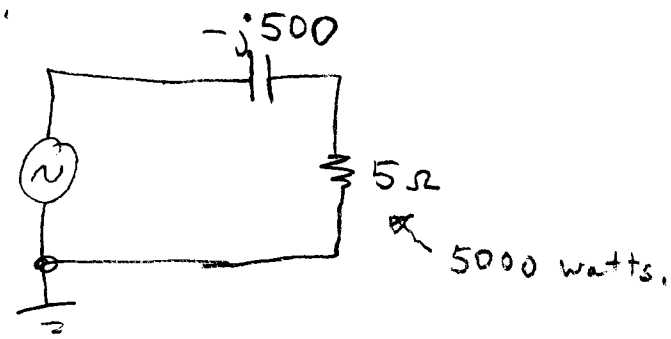

We need 5000 watts in the resistive part:

Find V:

$$P = \frac{V^2}{R} \rightarrow V^2 = PR \rightarrow V = \sqrt{PR}$$

$$V = \sqrt{(5000)(5)} = \sqrt{25000} = 158.1 \text{ volts}$$

Find I:

$$P = I^2 R \rightarrow I^2 = \frac{P}{R} \rightarrow I = \sqrt{\frac{P}{R}}$$

$$I = \sqrt{\frac{5000}{5}} = \sqrt{1000} = 31.62 \text{ Amps}$$

Check:

$$P = VI$$

$$(158.1)(31.62) = 5000 \checkmark$$

check:

$$R = \frac{V}{I}$$

$$\frac{158.1}{31.62} = 5 \checkmark$$

But this is not the answer.

It is only the resistive part.

Capacitor voltage ---

Current is 31.62 Amps (same as resistor)

$$V = I Z$$

$$= (31.62)(-j500)$$

$$V = -j15811 = 15.8 \text{ kV} \angle -90^\circ$$

So -- voltage out of generator =

$$= V_C + V_R = 15811 \angle -90^\circ + 158.1 \angle 0^\circ$$

$$V_{\text{generator}} = 15812 \angle -89.4^\circ$$


Real power = 5000 watts

Imaginary power = 500,000 VAR

Complex "power" \approx 500,000 VA

Generator must supply 15812 volts

at 31.62 Amps

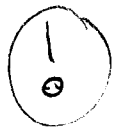


to put out only 5000 watts ---

$$\text{power factor} = \cos(\theta) = 0.01$$

To fix it --- put an inductor
either in series or parallel ---

Series:

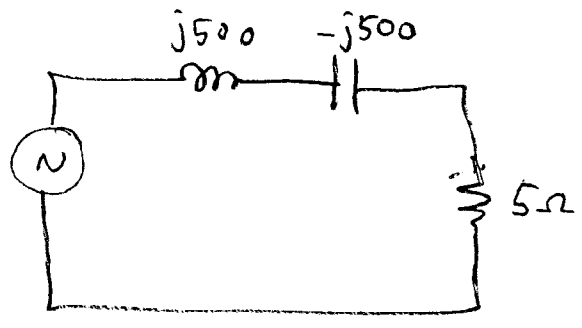

$Z_L = j500 \Omega$. — to cancel the $-j500$
of the capacitive part
of the load.

$$Z_L = j\omega L \rightarrow L = \frac{Z_L}{j\omega}$$

$$L = \frac{j500}{j(2\pi 10^6)} = \frac{500}{2\pi 10^6} = 79.58 \mu H.$$

Now, the generator only needs to supply
158.1 volts

so --- Real power = 5000 watts
Imaginary power = 0.