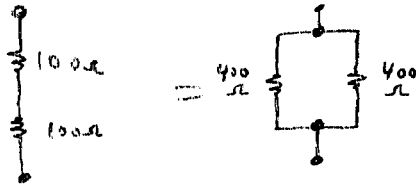



Series - parallel equivalent circuits--

10c
①


At any one frequency, For every series circuit there is an equivalent parallel circuit.



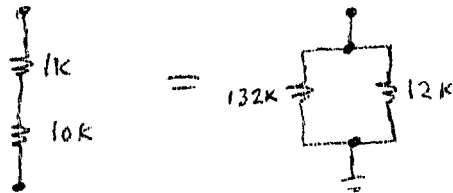
← Actually, there are many - anything that results in 200Ω



How about ---

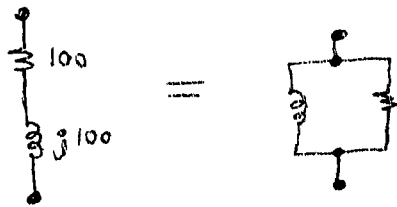

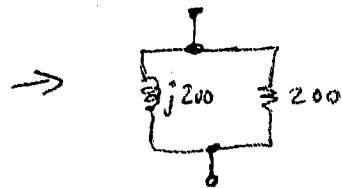
$$100 + j100 = \frac{1}{.005 - j.005} = \frac{1}{\frac{1}{200} + \frac{1}{j200}}$$




But it really is at only one frequency

10c
②


Suppose $\omega = 10$

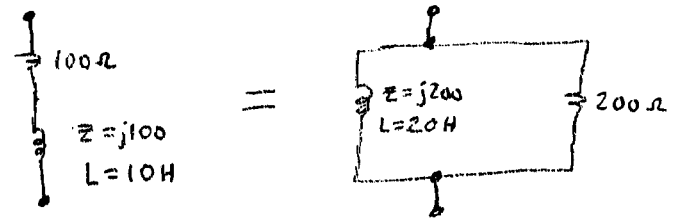

But when $\omega = 20$:

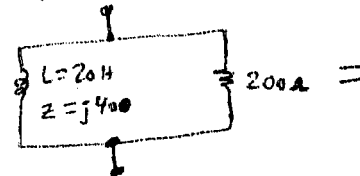

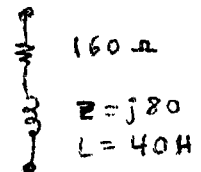
$$\frac{1}{\frac{1}{200} + \frac{1}{j400}} = \frac{1}{.005 - j.0025} = 160 + j80$$



Impedance matching

Suppose we have a power source that doesn't match the load ---
What can we do?

Example:

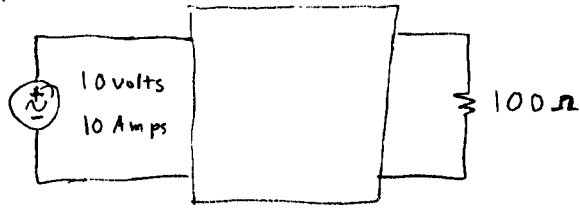

The source (10 Volts) can supply 10 Amps - (100 watts)

$$\text{The optimum load is } R = \frac{V}{I} = \frac{10V}{10A} = 1 \Omega$$

We want to deliver 100 watts to 100 Ω
That's 100 Volts at 1 Amp.

How? What goes in the box?

Two approaches:


① Transformer

② LC Matching network

10c
③

Approach #1 -- Transformer --

10c
④

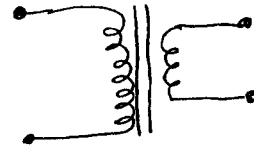

Two inductors wound on the same core ---
so they are coupled.

We refer to "turns ratio" ---

1:10 means there are 10 times as many turns in the primary as in the secondary

Example: 50 turns to 500 turns.

→ This will "transform" the voltage according to the turns ratio ---

10 Volts on primary gives you 100 Volts on secondary

and the current according to the inverse of the turns ratio

10 Amps on the secondary gives you 1 Amp on the primary

power ---

$$\text{primary: } P = VI = (10)(10) = 100 \text{ Watts}$$

$$\text{secondary: } P = VI = (100)(1) = 100 \text{ Watts}$$

$$\text{Impedance --- primary } Z = \frac{V}{I} = \frac{10}{10} = 1 \Omega$$


$$\text{Secondary } Z = \frac{V}{I} = \frac{100}{1} = 100 \Omega$$

→ impedance ratio is turns ratio squared.


Approach #2 -- LC network --

10c
⑤

Recall:  series $\rightarrow 0 \Omega$ at resonance
"Lo-Z"

 parallel $\rightarrow \infty \Omega$ at resonance.
"Hi-Z"

Consider these:

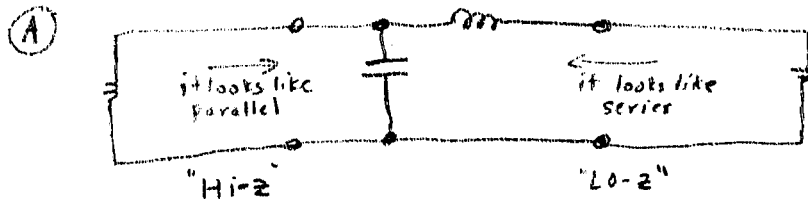

Idea: put this L-C between our generator and load.
Which way? Look at "Hi-Z" and "Lo-Z" ends.



Lo Z
(1 Ω)

Hi-Z
put cap on this end

Pick value of cap for $X = \sqrt{Z_1 Z_2}$

$$= \sqrt{(1)(100)}$$


$$= \sqrt{100}$$

$$= 10 \Omega$$

$$X_C = -j10 \Omega$$


Now pick L to tune it, but
the combination of series-parallel is hard to tune

10c
⑥

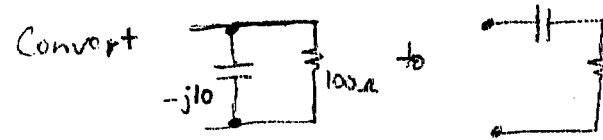


$$Z = \frac{1}{\frac{1}{100} + \frac{1}{-j10}}$$

$$= \frac{1}{.01 + j.1}$$
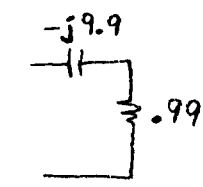
$$= .99 - j9.9 \rightarrow$$


So choose inductor $+j9.9$

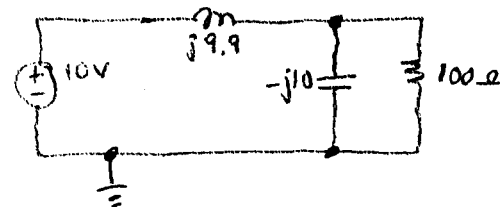

The 10V source sees
a 1Ω resistive load!

Try some real values --

suppose $F = 60 \text{ Hz}$ $\omega = 376.99$

$$X_L = j\omega L \rightarrow L = \frac{X_L}{j\omega} = \frac{j9.9}{j376.99} = .026261 \text{ H}$$

$$X_C = \frac{1}{j\omega C} \rightarrow C = \frac{1}{j\omega X_C} = \frac{1}{j(376.99)(-j10)} = .00026526 \text{ F}$$

$$= 265.26 \mu\text{F}$$