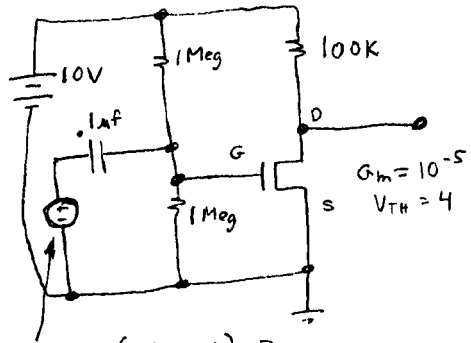


A sample circuit - using superposition --  
AC and DC solution:


8B  
①

From a quiz---



$.001 \cos(2\pi 1000t)$   
 $.001 \cos(2\pi 10t)$  } either of these

Equivalent circuit:

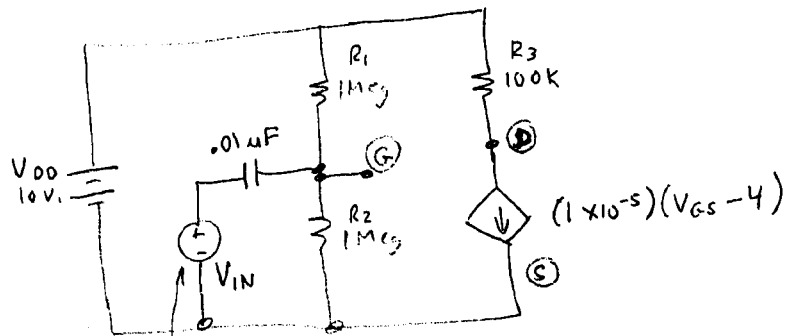

$.001 \cos(2\pi f t)$

$f = \begin{cases} 1000 \text{ Hz} \\ 10 \text{ Hz} \end{cases}$

call it ".001  $\angle \omega$ "

What is  $V_D$ ?


What is  $\frac{V_D}{V_{IN}}$

'AC component'

Idea: use superposition -

8B  
②

First set AC sources to zero - solve.

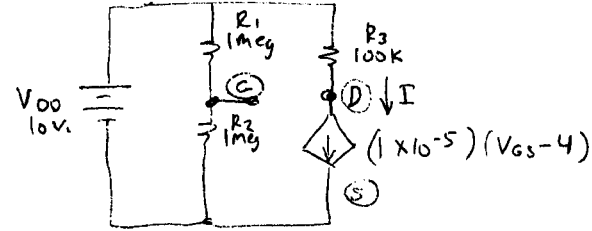

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{10^6}{10^6 + 10^6} 10 = 5$$

$$I = (10^{-5})(V_{GS} - 4) = (10^{-5})(5 - 4) = 10^{-5} \text{ A}$$


$$V_{R3} = I R = (10^{-5})(10^5) = 1$$

$$V_{DS} = V_{DD} - V_{R3} = 9$$



(repeat of a quiz from a few weeks ago)

Now, set the DC sources to zero, --  
leaving only the AC sources--

8B  
3

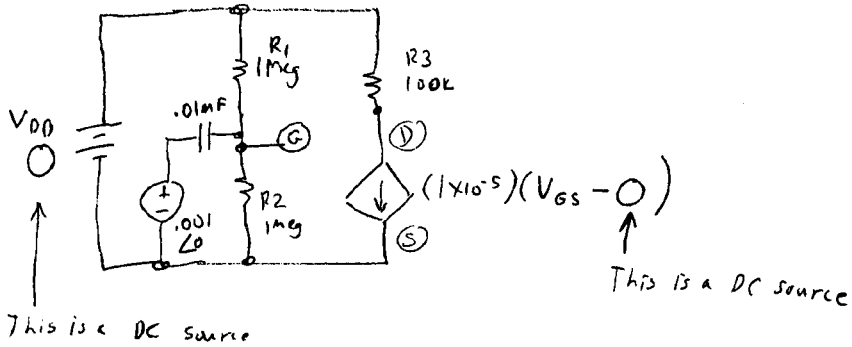

Leaving---

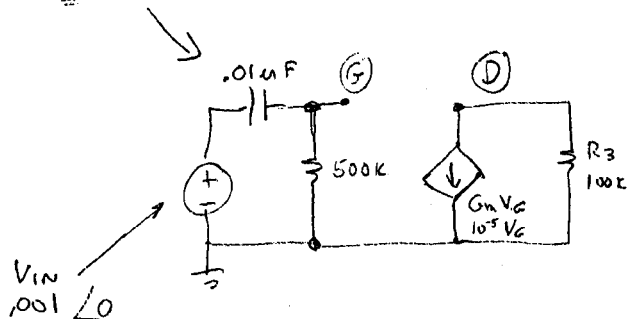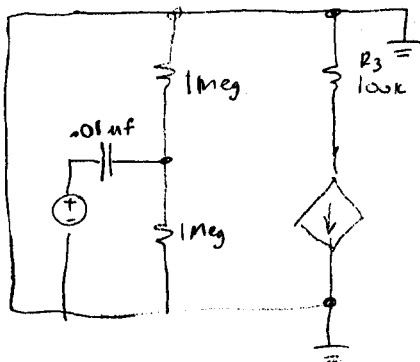

Node equations:

$$\textcircled{G} \quad \frac{V_G}{R} + \frac{V_G - V_{IN}}{\frac{1}{j\omega C}} = 0$$

Solve for  $\frac{V_G}{V_{IN}}$

$$\frac{V_G}{R} + \frac{V_G}{\frac{1}{j\omega C}} - \frac{V_{IN}}{\frac{1}{j\omega C}} = 0$$

$$\frac{V_G}{R} + j\omega C V_G - j\omega C V_{IN} = 0$$

$$V_G \left( \frac{1}{R} + j\omega C \right) = V_{IN} (j\omega C)$$

$$\frac{V_G}{V_{IN}} = \frac{j\omega C}{\frac{1}{R} + j\omega C}$$

$$\frac{V_G}{V_{IN}} = \frac{j\omega C R}{1 + j\omega C R}$$

Combine---

$$\frac{V_D}{V_{IN}} = \frac{V_D}{V_G} \cdot \frac{V_G}{V_{IN}} = - \frac{j\omega C R}{1 + j\omega C R}$$

$$\omega = 2\pi 1000: \quad j\omega C R = j\omega (.01 \times 10^{-6})(5 \times 10^5) = j5$$

$$\omega = 2\pi 10: \quad j\omega C R = j0.05$$

$$\frac{j5}{1+j5} = .961 + j.192 = .98 \angle 1.107 \text{ rad}$$

$$= .98 \angle 110^\circ$$

$$\frac{j.05}{1+j.05} = .0024938 + j.0498753 = .0499 \angle 1.52 \text{ rad}$$

$$= .0499 \angle 87.138^\circ$$

8B  
4

$$\textcircled{D} \quad G_m V_G + \frac{V_D}{R_3} = 0$$

solve for  $\frac{V_D}{V_G}$

$$\frac{V_D}{R_3} = -G_m V_G$$

$$\frac{V_D}{V_G} = -G_m R_3$$

$$= -(10^5)(10^5)$$

$$\frac{V_D}{V_G} = -1$$

↑  
bad example --  
this value is only  
by chance