

Summary so far --

2A
①

"small signal" "linear" applications
of op amp.

We assumed it is ideal.

Negative feedback

Virtual short-circuit applies.

Guru
OA-D
Sec. 11.18
only.

Today:

"Large signal" and "positive feedback"
applications of op-amp.


Not ideal.

Positive feedback

Can't use virtual-short-circuit (Nullor)
model,
(but still, $I_{in} = 0$)

Comparator

2A
②

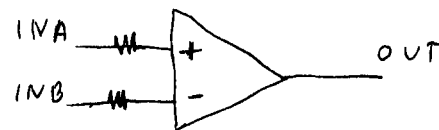

OUT is positive when $INA > INB$
negative when $INA < INB$
unknown when $INA \approx INB$

Uses: Analog to digital conversion
digital buffers
relay drivers.

Resistors limit current, $I=0$ should still apply,
but doesn't always
Typical value $\times 10K$ — not critical.


Schmitt Trigger

2A
③


We want a window, where it doesn't change.
"hysteresis".

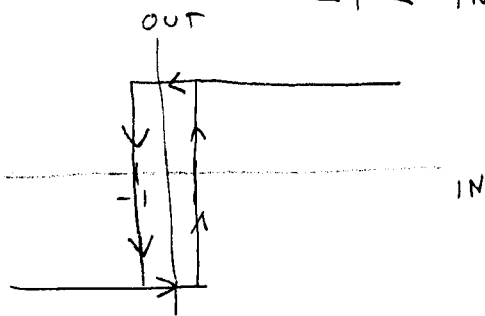Example: $IN > 1 \text{ volt} \rightarrow \text{HIGH}$
 $IN < -1 \text{ volt} \rightarrow \text{LOW}$


$-1 < IN < 1 \rightarrow \text{maintain state.}$
 initially unknown



How? — Positive feedback

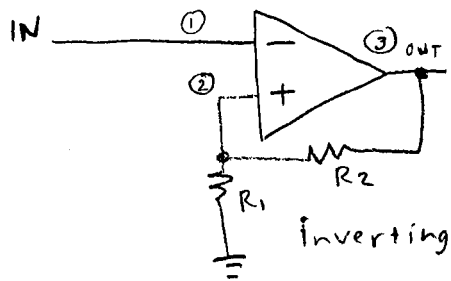

or...

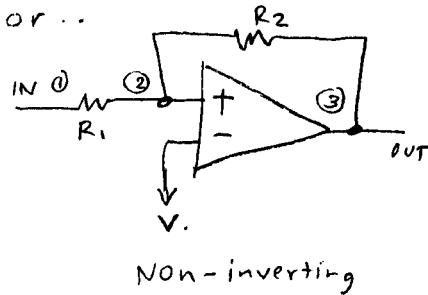

Analysis of schmitt trigger

2A
④

Inverting: $V_3 = \begin{cases} +14 & \text{in high state} \\ -14 & \text{in low state} \end{cases}$
 ↑
 depends on power supply

Assume $V_3 \dots$

$$\text{then } V_2 = V_3 \frac{R_1}{R_1 + R_2}$$

When output is high ...

when $V_1 < V_2$ — will remain high
 $V_1 > V_2$ — will change state.
 (go low)

When output is low ...

when $V_1 > V_2$ — will remain low
 $V_1 < V_2$ — will change state
 (go high)

— almost like comparator —
 but V_2 changes.

Example

Suppose $R_1 = R_2 = 10K$ 2A
5

$$V_{power} = \pm 15$$

$$V_3 = \begin{cases} +14 & \text{in high state} \\ -14 & \text{in low state} \end{cases}$$

Must analyze in each state:

High state: $V_3 = 14 \Rightarrow V_2 = 7$

When $V_1 < 7$ — output remains high

$V_1 > 7$ — changes state
(becomes low)

Low state: $V_3 = -14 \Rightarrow V_2 = -7$

When $V_1 > -7$ — output remains low

$V_1 < -7$ — changes state
(becomes high).

So ---

IN	OUT
> 7	Low
\rightarrow to \rightarrow	hold state.
< -7	HIGH

Designing it —

we want threshold $\pm 1V$.

$$V_{power} = \pm 12V$$

$$V_{out} = \pm 11V$$

$$V_2 = V_3 \frac{R_1}{R_1 + R_2}$$

$$1 = 11 \frac{R_1}{R_1 + R_2}$$

$$\frac{R_1}{R_1 + R_2} = \frac{1}{11} \Rightarrow \frac{10K}{110K}$$

$$R_1 = 10K \\ R_2 = 100K$$

IN	OUT
> 1	Low
-1 to 1	hold.
< -1	HIGH


2A
6

Waveform generation

2A
7

By adding an R-C network to the Schmitt trigger, we can make an oscillator.


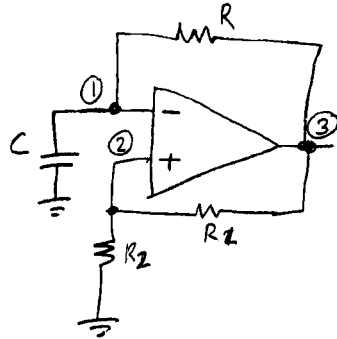
This one is called "relaxation oscillator"



Positive feedback
(3) to (2)
makes it change state quickly, and hold it.

Negative feedback
(3) to (1)
determines timing.

Recall... RC Network

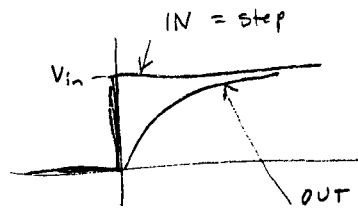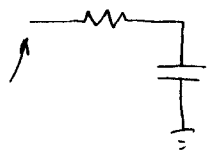

$$out = V_{in} (1 - e^{-\frac{t}{RC}})$$

t	OUT (for Vin=1)
0	0
RC	.632
2RC	.864

$$T = 2RC \ln \left(1 + 2 \frac{R_2}{R_1} \right)$$

Example: Let $R_2 = R_1$


$$\text{then } \ln \left(1 + 2 \frac{R_2}{R_1} \right) = \ln(3) \approx 1.1$$

$$T = 2.2 RC$$


For 100 Hz, $T = .01$

Choose $C = 100 \text{ nF}$
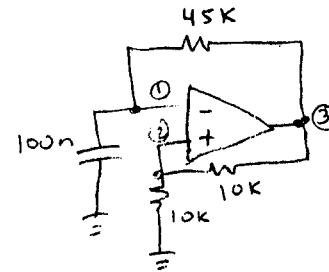
$$\begin{aligned} \text{Then } .01 &= (2.2)(10^{-7})(R) \\ R &= 4.5 \times 10^4 \\ &= 45 \text{ K} \end{aligned}$$



Waveforms:

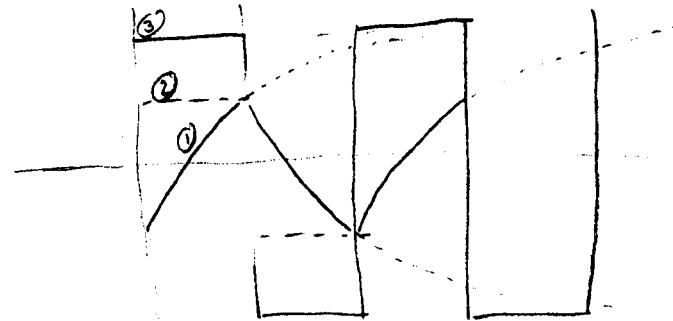

2A
8