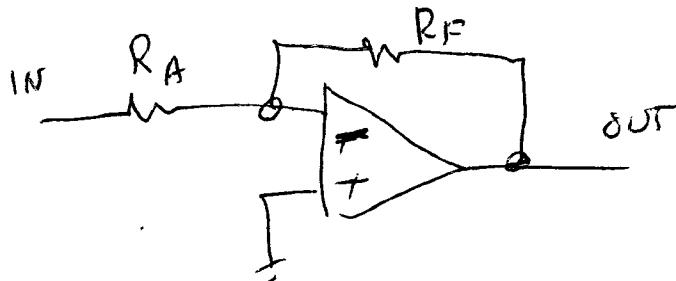


Name \_\_\_\_\_

## Key

1. Draw the circuit diagram of the basic inverting amplifier configuration.



-0	1
-1	9
-2	2
-3	6
-5	2
-7	1
-8	1

- Give an expression for the voltage gain of the circuit in terms of the resistors, assuming an ideal op-amp.

$$- \frac{R_F}{R_A}$$

-0	13
-1	4
-2	4
-3	1


- Give an expression for the input impedance of the circuit.

$$R_A$$

- Give the resistor values for a voltage gain of -20 and input impedance of 20k.

$$R_A = 20\text{ k} \quad R_F = 400\text{ k}$$

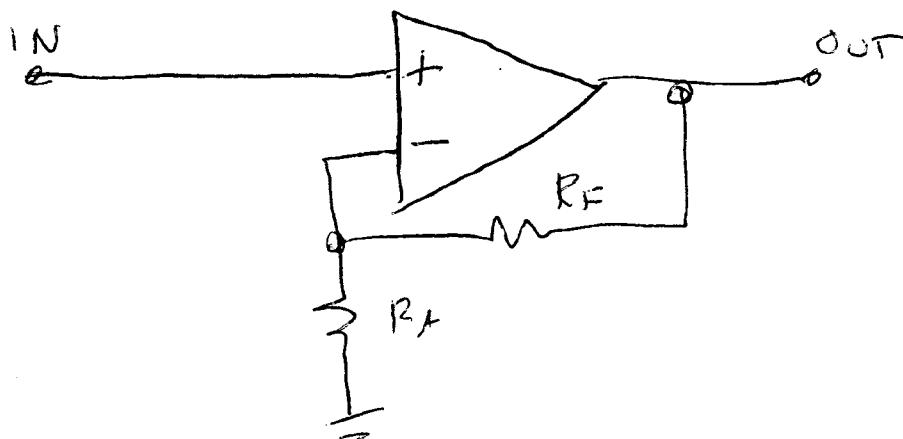2. Draw the circuit diagram of the basic non-inverting amplifier configuration.



-6	2
-1	10
-2	3
-3	5
-5	2

Give an expression for the voltage gain of the circuit in terms of the resistors, assuming an ideal op-amp.

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{R_A}$$

Give an expression for the input impedance of the circuit.

$\infty$

Give the resistor values for a voltage gain of 20 and input impedance of 20k. You may use resistor values only 1k and higher.

$$R_A = 1\text{K}$$

$$R_F = 19\text{K}$$

+1  
for doing this

Add a resistor:  
 $= 20\text{K}$

