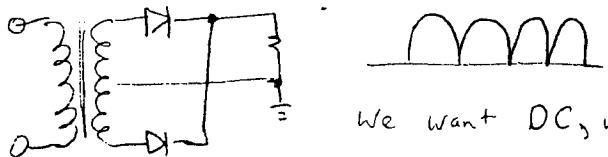


Power supply filters (2.1.3)

3A
1


Recall ...

A rectifier puts out something like this!




We want DC, without ripple.

Ideal: Add a capacitor

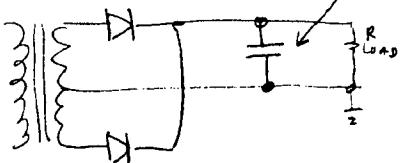

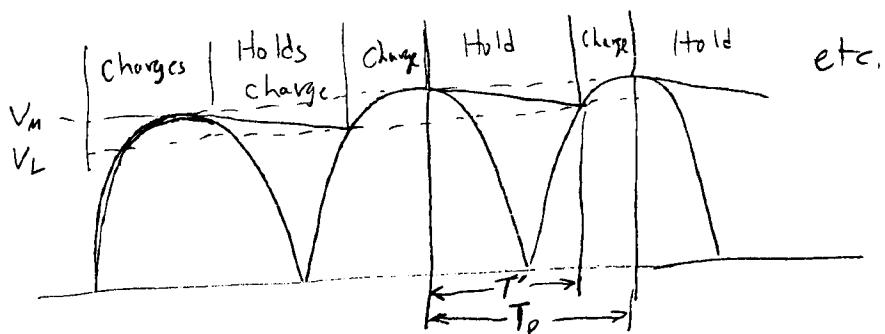It charges when the diode is on, then holds the charge.



The capacitor holds the voltage to nearly the peak voltage.


The diode is only on for a short period at the peak (marked "charge" here).

The output has a small (?) ripple.


Recall ... The formula for a capacitor voltage decaying ...

$$V_o(t) = V_m e^{-\frac{t}{T}}$$
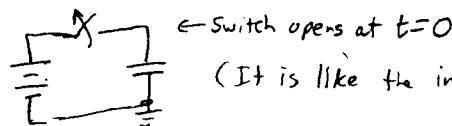
$$\begin{aligned} t &= \text{time since} \\ T &= \text{time constant} \\ &= RC \end{aligned}$$



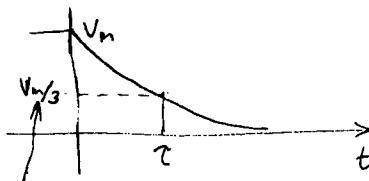(It is like the input dropping so the diode turns off)



approximately.

$$\text{Actually} \dots 368V_m$$

$$368 = e^{-1} \approx \frac{1}{3}$$

The smallest output voltage is when the diode turns back on -- after time T'

$$V_L = V_m e^{-\frac{T'}{T}}$$

Ripple voltage is the difference ..

$$V_r = V_m - V_L = V_m \left(1 - e^{-\frac{T'}{T}}\right)$$

Simpler analysis --

We need to supply a current \underline{I} .

We can tolerate some ripple $\underline{V_R}$.

Recall --- $I = C \frac{dV}{dt}$ $Q = CV$

Basic capacitor equations ..

$$I = \frac{dQ}{dt} \leftarrow \text{definition of current}$$

For half wave -- $dt = \frac{1}{f}$

full wave -- $dt = \frac{1}{2f}$

so $I = C \frac{dV}{dt}$

DC Load current

Capacitor needed

Ripple voltage - peak-to-peak

Time between peaks.

$$I = C V_R f$$

Rearrange:

$$C = \frac{I}{V_R f}$$

Replace
③

Example

Replace
④

A power supply must deliver 100 Volts at 100 mA with less than 10 Volts (peak-to-peak) ripple. What is C?

Power frequency = 60 Hz

Solution: (half wave)

$$C = \frac{I}{V_R f} = \frac{0.1 \text{ A}}{(10 \text{ Volts})(60 \text{ Hz})} = 166.7 \times 10^{-6} \text{ Farad}$$
$$= 166.7 \mu\text{F}$$

Full wave -- $f = \underline{\underline{120 \text{ Hz}}}$

$$C = \frac{I}{V_R f} = \frac{0.1}{(10)(120)} = 83.3 \mu\text{F}$$

Variants of the formula ...

$$C = \frac{V_m}{V_r} \frac{T_p}{R}$$

with current ... $V_m = IR$

$$C = \frac{IR}{V_r} \frac{T_p}{R} = \frac{I T_p}{V_r}$$

Usually, this is
the easiest form
to use.

$$\text{or } C = \frac{I}{V_r f}$$

Half wave : $C = \frac{-1}{(10)(60)} = 16.7 \mu\text{F}$

Full wave : $C = \frac{-1}{(10)(120)} = 83.3 \mu\text{F}$

(3A)
5


Diode current and Capacitor current

(3A)
6

Diode current flows only in a small part of the cycle, yet load current flows continuously.

It comes from the capacitor.

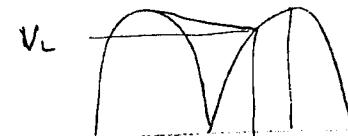Peak current is much higher than average current.



Δt_k
conducts
only here

To calculate Δt ...

$$V_L = V_m \cos(\omega \Delta t)$$

Taking the first 2 terms of the Taylor series -

$$\cos(x) \approx 1 - \frac{1}{2} x^2$$


$$V_L = V_m \left(1 - \frac{1}{2} (\omega \Delta t)^2\right)$$

$$V_m - V_r = V_m \left(1 - \frac{1}{2} (\omega \Delta t)^2\right)$$

$$V_m - V_r = V_m - \frac{V_m}{2} (\omega \Delta t)^2$$

$$V_r = \frac{V_m}{2} (\omega \Delta t)^2$$
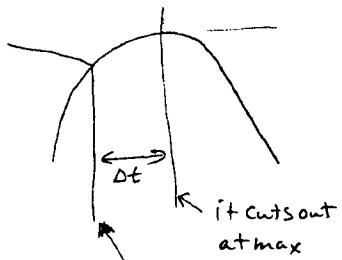
$$\frac{2V_r}{V_m} = (\omega \Delta t)^2$$



in here --
at min

example:

$$\sqrt{\frac{2(10)}{100}} = 44^\circ \text{ rad.}$$

$$= 25^\circ \text{ deg.}$$

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_m}}$$

$$\Delta t = \sqrt{\frac{2V_r}{V_m}} / \omega$$

Example:

$$\Delta t = \sqrt{\frac{2(10)}{100}} / \frac{2\pi 60}{} = 1.18 \times 10^{-3}$$

Charge lost by capacitor to load:

$$Q = CV_r \quad \text{also} \quad Q = IT_p \quad (q = \frac{di}{dt})$$

This charge must be restored when the diode is on..

$$Q = i_{cap.} \Delta t$$

↑ Charge time
avg. Current during charge.

$$i_{cap} = \frac{Q}{\Delta t}$$


Diode current = cap current + load current

$$i_{diode} = i_{cap} + i_{load}$$


$$\begin{aligned} i_{cap} &= \frac{1.67 \times 10^{-3}}{1.18 \times 10^{-3}} \\ &= 1.415 \text{ Amp.} \\ i_D &= 1.415 + .1 \\ &= 1.515 \end{aligned}$$

But that assumes it is uniform.

I+ isn't.

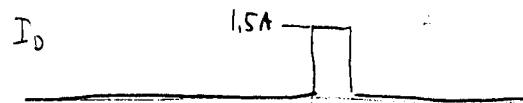

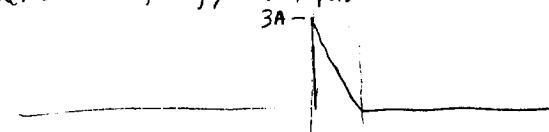Actual is higher at the beginning, then tapers off.



It is roughly triangular,

so the peak is about twice the average.

(3A for this example.)

(3A)

Exercises:

(Not to hand in)

P
61 #
1

62-63 2,3,4,5
87 4,8,11

To hand in:

P. 95 D 2.53

It doesn't come out exact.

Get as close as you can.

Assume $V_D = .7$


What is peak diode current?
Peak inverse diode voltage?

(3A)
8

Reverse voltage across diodes - with filter

3B
1

Here's a circuit

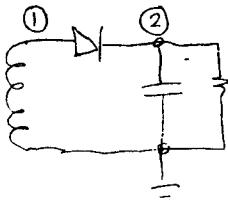


Recall ...

The output voltage is: (node 2)



The voltage at node 1 is:

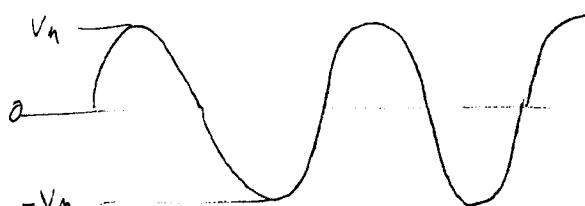

The voltage across the diode is:
 $(V(2) - V(1))$

The peak voltage across the diode is twice the max delivered voltage.

Twice what it was with no capacitor.


What about full wave?

bridge?

Designing a power supply

3B
2

① Pick a topology

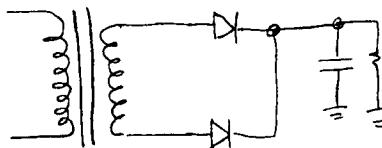

② Determine V_M , V_L from specs.

③ Take V_M .

Add voltage lost in diodes.

④ Add transformer loss.
(like a resistance)

→ This is peak secondary voltage

⑤ Convert to RMS if needed.
(depends on specs)

⑥ Calculate turns ratio

$$\frac{V_{sec}}{V_{pri}} \text{ or } \frac{V_{pri}}{V_{sec}}$$

Express as $n:1$ (step _{down})
or $1:n$ (step up)

⑦ Determine capacitor value

⑧ Determine voltage, power, current ratings of components.

Example

You are designing a power supply for the high voltage on a cathode ray tube.

Your power source is 7 volts AC (10 volts peak)
20 kHz

The supply must deliver 20-25 KV.
(25 KV max, 20 KV min, 5 KV max ripple)

With a load current of 1mA.

Assume a 10 volt drop in the diode.
(It is really 16 diodes in series.)

Choose a topology.

Then find: Turns ratio (pri:sec)

Capacitor

Voltage rating of diode


Peak diode current

Average primary current

Power delivered to load

(3B
3)

Topology: halfwave.

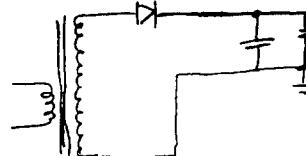(3B
4)

Ignore 10 volt diode loss.

$$V_m = 25 \text{ KV}$$

$$V_L = 20 \text{ KV}$$

$$V_r = 5 \text{ KV.}$$

Ignore transformer resistance

$$\text{Turns ratio} = \frac{25000}{10} = 2500$$

$$1 : 2500$$

Capacitor:

$$C = \frac{I}{V_r f}$$

$$= \frac{1 \times 10^{-3}}{(5 \times 10^3)(2 \times 10^4)}$$

$$= 10 \times 10^{-12}$$

$$= 10 \text{ pf}$$

Power delivered to load:

$$(25 \text{ KV})(1 \text{ mA})$$

$$= 25 \text{ watts}$$

Average primary current

$$(1 \text{ mA})(2500) = 2.5 \text{ A.}$$

Peak diode current:

$$Q = CV = (10^{-11})(5 \times 10^3)$$

$$= 50 \times 10^{-9}$$

$$= IT_p = (10^{-3})(50 \times 10^{-6})$$

$$= 50 \times 10^{-9}$$

$$\Delta t = \sqrt{\frac{2V_r}{V_m}} = \sqrt{\frac{(2)(5)}{25}}$$

$$= \frac{1}{2\pi(20 \text{ K})}$$

$$= \frac{\sqrt{\frac{10}{25}}}{126 \times 10^3} = \frac{.632}{126 \times 10^3}$$

$$= 5 \times 10^{-6} = 5 \mu\text{s}$$

$$i_{cap} = \frac{Q}{\Delta t} = \frac{50 \times 10^{-9}}{5 \times 10^{-6}} =$$

$$= 10 \text{ mA (avg when on)}$$

$$i_{cap} \approx 20 \text{ mA.}$$

Voltage rating of diode:
50 KV.

(10 5 KV diodes)