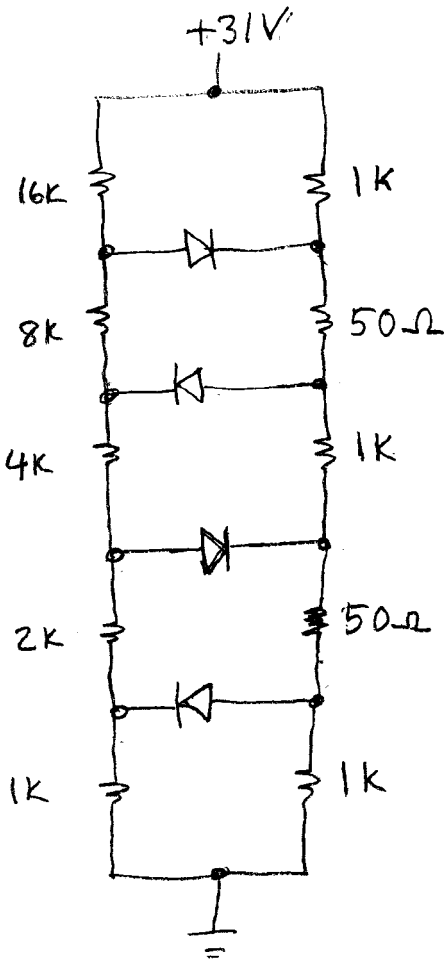


Name _____



Find node voltages and diode states

Name _____

Find node voltages
and diode states

