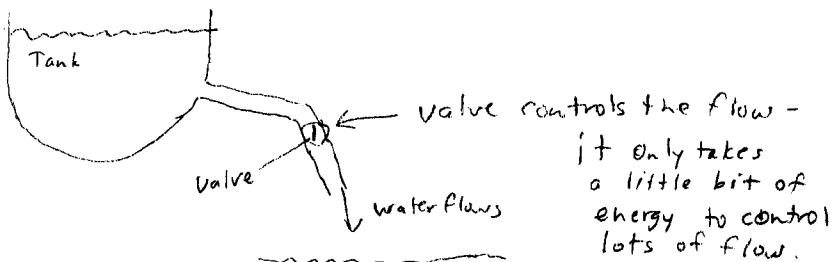


Introduction to amplifiers


Or--- how do we get "gain"?

Idea--- think of a fluid system:




Back to electronics --

Two kinds of devices:

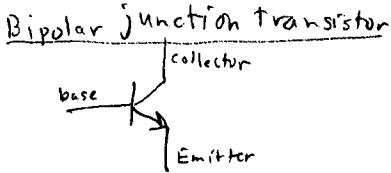


Current flows from collector to emitter controlled by the base (actually by base current)

Simple model:

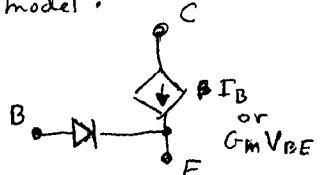


Field effect transistor

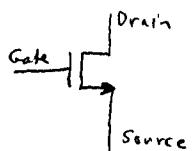

current flows from drain to source controlled by the gate (actually by gate to source voltage)

Simple model =

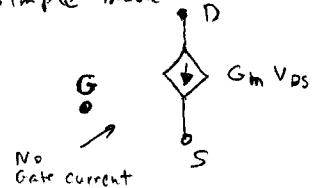

①


Both types only work when current is flowing in the indicated direction.

GB
②

They only sink current
absorb power.


They cannot generate power.

Simple "Common source" amplifier:

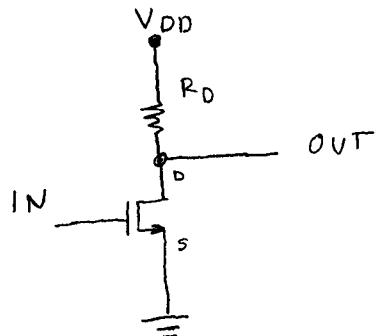


Using "Linear" model for now.
Not very accurate!

Substitute the model:

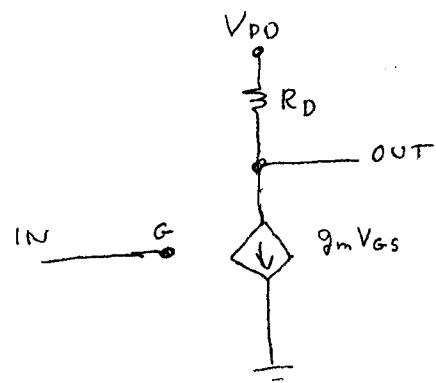

Try it with some values ---

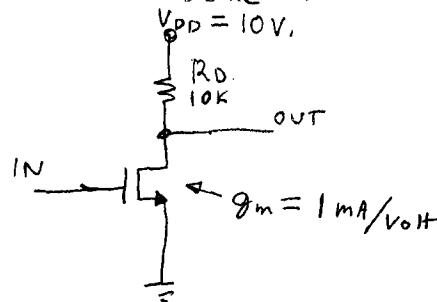


6B
③

Observations:

① Model is only valid in Active region.

Substitute the model :

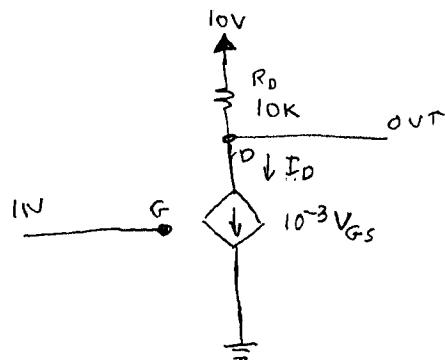

V _{GS}	I _D	V _{RD}	V _{GS}
0	0	0	10
.1	.1 mA	.1	9
.2	.2 mA	2	8
.5	.5 mA	5	5
.9	.9 mA	9	1
1.0	1 mA	10	0
1.1	1.1 mA	11	-1 ← model not valid (saturation)
-0.1	-0.1 mA	-1	11 ← model not valid (cutoff)

"Active" region

.1 Volt change in input produces 1 volt change in output

$\text{Gain} = \frac{\Delta \text{out}}{\Delta \text{in}} = -10$

This model is only valid for $V_{DS} > 0$
and $I_D > 0$

6B
④

How do we amplify AC?


How do we amplify DC that is both positive and negative?

Are there other configurations?

To amplify AC ---

→ Add "bias" to preset the device to the middle of the active region.

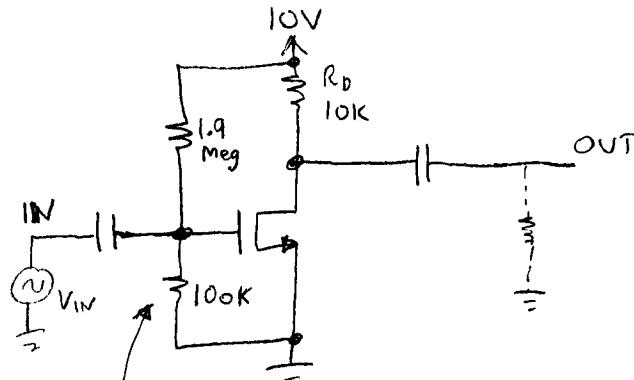→ Use capacitors to couple the signal in and out:



Select resistors to put drain at the midpoint of active region
 $= 5V$.

Make $V_{GS} = .5V$ Make them high.
(There's no gate current.)


Analysis:

You must do it twice -

(1) DC

(2) AC

DC - Find the "operating point"

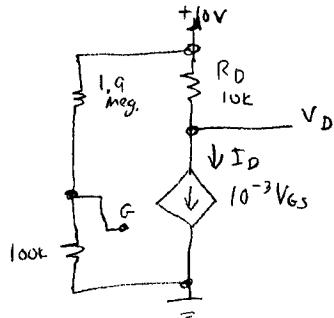

$$V_G = (10) \frac{100\text{k}}{100\text{k} + 1.9\text{meg}} = 0.5\text{V}$$

$$I_D = 10^{-3} V_{GS} \\ = (10^{-3})(0.5) \\ = 0.5 \times 10^{-3} = 0.5\text{mA}$$

$$V_{RD} = IR \\ = (0.5\text{mA})(10\text{k}) \\ = 5\text{ Volts}$$



$$V_{DS} = V_{DD} - V_{RD} \\ = 10 - 5 \\ = 5$$

Stop here if the operating point is not reasonable.

This one is OK.

(5)

AC - by superposition

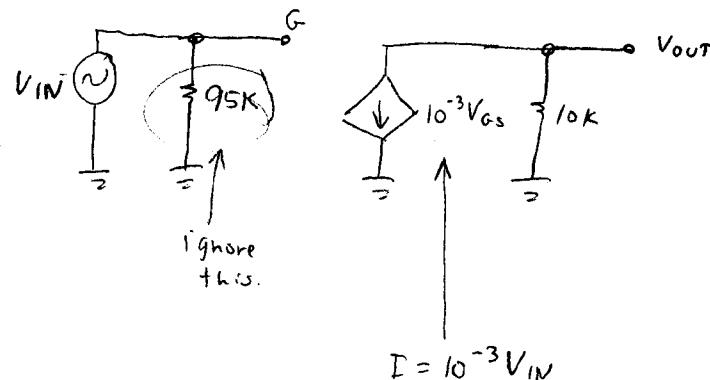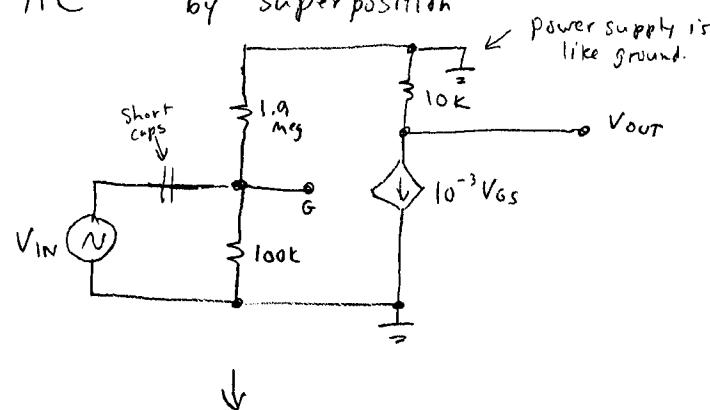

KCL ---

$$10^{-3} V_{IN} + \frac{V_{OUT}}{10\text{k} \parallel 10^4} = 0$$

$$\frac{V_{OUT}}{V_{IN}} = -(10^{-3})(10^4) \\ = -10$$

Only when it stays in the active region.


(6)

Homework

6B
7

Use the linear model of the MOSFET---

①

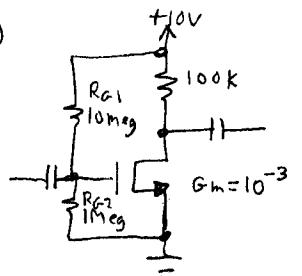


- a. Find operating point (node voltages)
- b. Determine if it is in the Active region
- c. if so, Find the AC gain.

② Determine the value for R_{G1} to make $V_{DS} = 5$ v.

then Find the AC gain


③

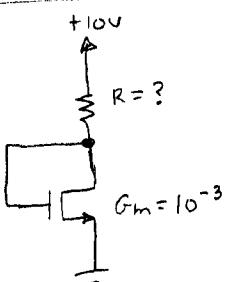

Find the value of R
for $V_{DS} = 5$

④

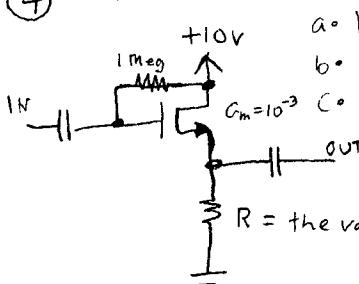Here's another circuit -- ("source follower")



- a. Find operating point
- b. Determine if in active region
- c. Find the AC gain

$R =$ the value from #3