
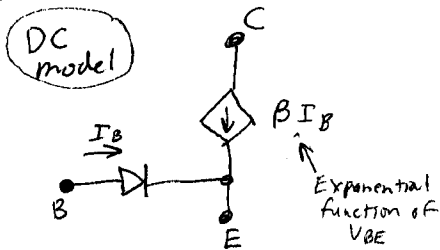


Real devices

1B
①

- There is resistance in parallel with the current source. (We will still ignore this for now).
- There may be something between the input (Gate or base) to the source (or emitter) which may load the input.
- The controlled source is nonlinear
 g_m is a function of current.

Bipolar Junction transistors

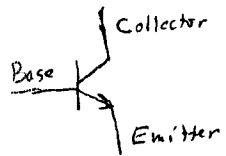

$$I_B = I_S \left(e^{\frac{V_{BE}}{nV_T}} - 1 \right)$$

Solve for V_{BE} ---

$$\log I_B \approx \log I_S + \frac{V_{BE}}{nV_T}$$


$$\frac{V_{BE}}{nV_T} = \log I_B - \log I_S$$

$$V_{BE} = nV_T (\log I_B - \log I_S)$$

\uparrow 10^{-6} \uparrow 10^{-15}

$$\approx 0.6 \text{ V.}$$

"Small signal" model

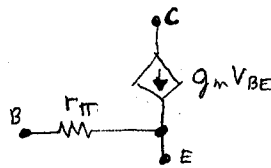


$$r_{\pi} = \frac{0.026}{I_B}$$

$$g_m = \frac{I_C}{0.026}$$


Field Effect Transistors

7B
②

DC model:

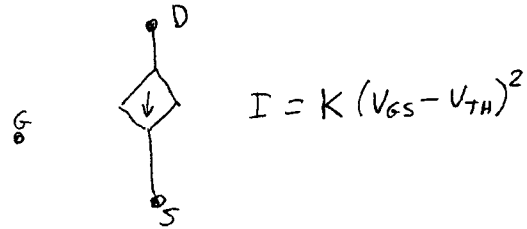

"Small signal" model

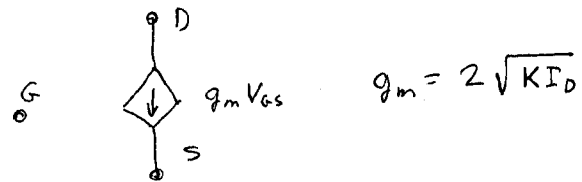

$K =$ "process transconductance" $\frac{\text{amps}}{\text{volts}^2}$

$V_{TH} =$ "Threshold voltage" - determined by process

K - determined by size and process

$$K = \frac{1}{2} K' \frac{W}{L}$$

K' is determined by process
(actually by the thickness of the insulator)