
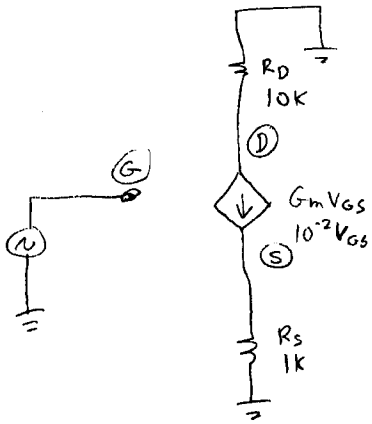


Analysis of the amplifier with source resistor -- τ (1)
 Another approach --

Use the same model --

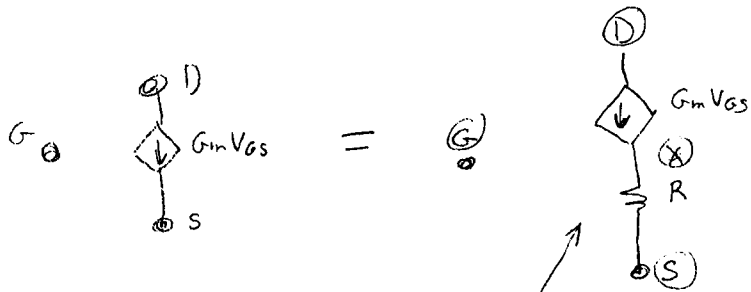

You can put a resistor in series with a current source without changing the result.




choose the resistor so $V_x = V_G$


$$I = G_m V_{GS} \quad V = V_{GS}$$

$$R = \frac{V}{I} = \frac{V_{GS}}{G_m V_{GS}} = \frac{1}{G_m}$$

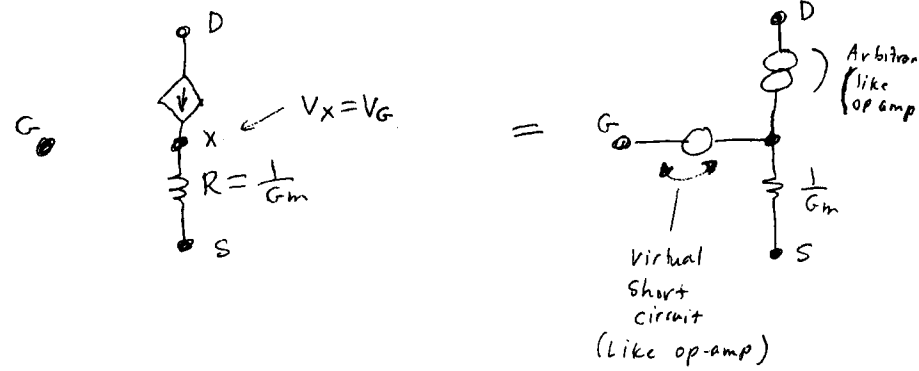SO -- You can use this model for a MOSFET -- τ (2)



plug in --

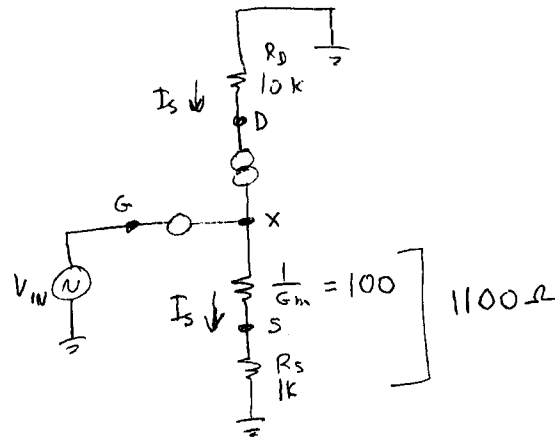

Analysis: $V_x = V_G$ $I_S = \frac{V_S}{R_S} = \frac{V_x}{R_S + \frac{1}{G_m}} = \frac{V_G}{R_S + \frac{1}{G_m}}$ $V_G = I_S (R_S + \frac{1}{G_m})$

$$V_D = -I_S R_D$$


$$\frac{V_D}{V_G} = \frac{-I_S R_D}{I_S (R_S + \frac{1}{G_m})} = \frac{-R_D}{R_S + \frac{1}{G_m}}$$

$$= \frac{-10K}{1K + 100} = \frac{-10K}{1.1K} = -9.09$$

```

gnucap> b
>q1 c b 0 nn
>.model nn npn is=1p
>
gnucap> list

```

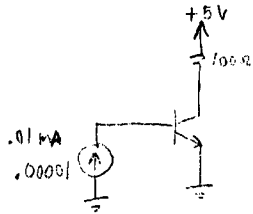

```

Q1 ( c b 0 ) nn area= 1.
.model nn npn (level=1 kf= 0. af= 1. bf= 100. br= 1. / is= 1.p] nf= 1. nr= 1. isc= 0. c
4= 0. nc= 2. ise= 0. c2= 0. ne= 1.5 rb= 0. rbm= 0. re= 0. rc= 0. cjc= 0. cje= 0. cjs=
0. fc= 0.5 mjc= 0.33 mje= 0.33 mjs= 0. vjc= 0.75 vje= 0.75 vjs= 0.75 xcjc= 1. itf= 0.
ptf= 0. tf= 0. tx= 0. xtf= 0. xtb= 0. xti= 3. eg= 1.11)
'+()

```

```

gnucap> b
>rc cc c 100
>vcc cc 0 5
>iin 0 b .00001
>

```

```

gnucap> pr op v *
gnucap> op


```

#	v(b)	v(c)	v(cc)	v(Q1)	v(nn)	v(Rc)	v(Vcc)	v(Iin)
300.15	0.53599	4.9	5.	??	??	0.1	5.	-0.53599

```

gnucap> b
>diode d 0 dd
>.model dd d is=1p
>idiode 0 d .001
>

```

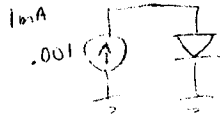

⇒ "is" is
"scale current"

$$I_c = I_s \left(e^{\frac{V_{BE}}{nV_T}} - 1 \right)$$

Transistor.

```

gnucap> pr op v nodes
gnucap> op

```

#	v(b)	v(c)	v(cc)	v(d)
300.15	0.53599	4.9	5.	0.53599

```

gnucap> EOF on stdin

```

↑ matches.