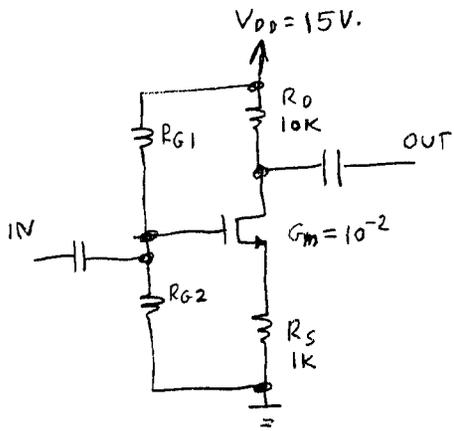


# The "Four resistor" bias circuit

7A  
①

We want → more control of gain and bias  
→ better consistency of performance.



We want to set the bias point for maximum possible voltage swing at the drain.

Target:  
Half of the voltage in the resistors  
Half of the voltage in the transistor.

To solve it ----

If  $V_{DD} = 15$ , we want 7.5 in resistors  
7.5 in transistor.

$$I = \frac{V}{R} = \frac{V_{DD}/2}{R_D + R_S} = \frac{7.5}{10k + 1k} = \frac{7.5}{11k} = 682 \mu A$$

$$\text{This makes: } V_{RD} = (682 \mu A)(10k) = 6.82 V.$$

$$V_{RS} = (682 \mu A)(1k) = 0.682 V.$$

Homework: ① Find the bias point for  $G_m = 10^{-3}, 10^{-1}$

② Find the gain for  $G_m = 10^{-3}, 10^{-1}$  for both bypassed and unbypassed.

We need to determine the gate voltage

②

Device characteristics:  $I_D = G_m V_{GS}$  (Properties of this type device)

rearrange formula:  $V_{GS} = \frac{I_D}{G_m}$

substitute:  $V_{GS} = \frac{682 \mu A}{10^{-2}}$

$$V_{GS} = 68.2 \text{ mV}$$

(.0682 V.) ← These small voltages are typical.


We can think of it as "zero"

$$V_G = V_S + V_{GS}$$

$$= 0.682 + 0.0682$$

$$= 0.75 V.$$

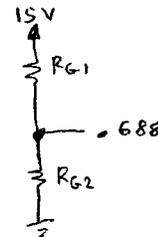Now choose  $R_{G1}$  and  $R_{G2}$  for 0.75 V



Voltage divider --


$$V_{RG2} = 0.75$$

$$V_{RG1} = 15 - 0.75 = 14.25$$

$$\frac{R_{G1}}{R_{G2}} = \frac{14.25}{0.75} \leftarrow \text{Any resistors in this ratio will work - choose high}$$

$$= \frac{19}{1}$$
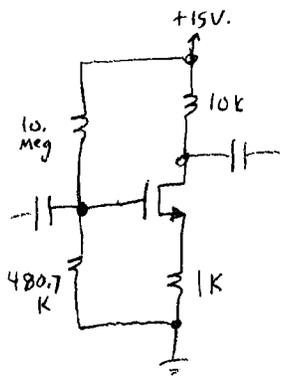
$$\frac{R_{G1}}{R_{G2}} = \frac{10 \text{ Meg}}{52.63 \text{ K}} \leftarrow \text{a possible pair of values.}$$




- ③
- ① What is the gain?
  - ② What happens when components are a little different?

② first ---

Components are a little different

$R_{G2} = 470K$  (standard value)

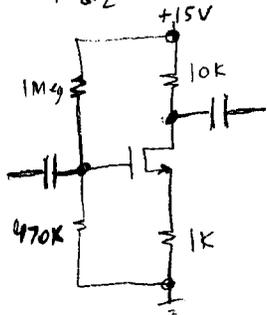


What is the real bias point?

First: Find  $V_G$

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$= 15 \frac{470K}{10M + 470K}$$

$$= .6734 V.$$

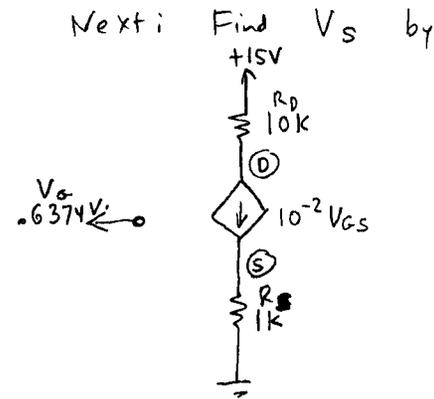

KCL at node (S)

$$\frac{V_S}{R_S} - G_m V_{GS} = 0$$

$$\frac{V_S}{1K} - 10^{-2} (.6374 - V_S) = 0$$

$$10^{-3} V_S - 6.374 \times 10^{-3} + 10 \times 10^{-3} V_S = 0$$

$$V_S - 6.374 + 10 V_S = 0$$

$$11 V_S = 6.374$$

$$V_S = \frac{6.374}{11}$$

$$V_S = .580$$

$$I_S = 580 \mu A$$

↑ we wanted 680  $\mu A$   
Does it matter?

$$V_{RD} = I R$$

$$= (580 \mu A)(10K)$$

$$= 5.8 V.$$

(wanted 6.82)

$$V_{Transistor} = 15 - 5.8 - .58$$


$$= 8.62$$

(wanted 7.5)


→ The bias point has moved by  $\approx 1$  volt.  
Probably it is still close enough!

Finding the gain:

Two variations:

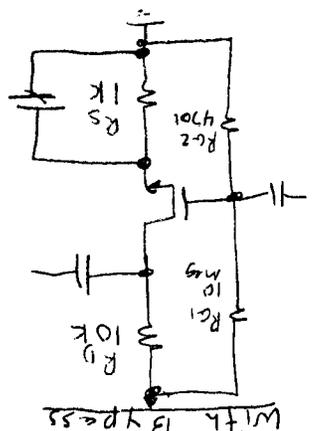


High gain

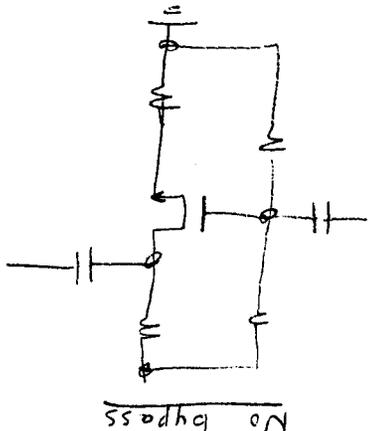

Low gain

First --- With bypass - high gain  
 → Bypassing the source resistor makes gain the same as if  $R_S$  was not there, but we keep the benefit in getting better bias.

⑤

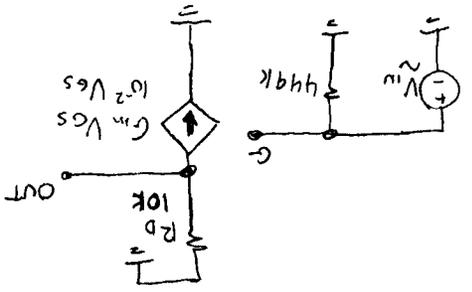

Gain =  $-G_m R_L$   
 $= -(10^{-2})(10^5)$   
 $= -100$

(by formula - You could do KCL at ①)

Substrate model: use AC equivalent circuit

⑥

7A got this far.


No bypass - lower gain

The hard way:

KCL at ①  $V_D + G_m V_{gs} = 0$   
 ⑤  $V_S - G_m V_{gs} = 0$   
 $V_{gs} = V_G - V_S$

④  $V_D + G_m (V_G - V_S) = 0$   
 ⑤  $V_S - G_m (V_G - V_S) = 0$

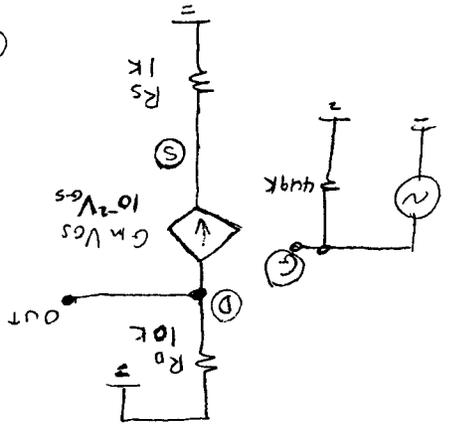2 equations, 2 unknowns  $V_S, V_D$   
 $R_D, R_S, G_m, V_G$  are known.



Solve ⑤ first - it has no  $V_D$

$$\frac{V_S}{R_S} - G_m V_G + G_m V_S = 0$$

$$V_S \left( \frac{1}{R_S} + G_m \right) - V_G (G_m) = 0$$

$$V_S \left( \frac{1}{R_S} + G_m \right) = V_G G_m$$

$$\frac{V_G}{V_S} = \frac{G_m}{\frac{1}{R_S} + G_m}$$

$$V_S = \left( \frac{\frac{1}{R_S} + G_m}{G_m} \right) V_G$$

Solve ④

[note that:  $\frac{V_S}{R_S} = G_m V_G$ ]

substitute ...

$$\frac{V_D}{R_D} + G_m V_G = 0$$

$$\frac{V_D}{R_D} + \frac{V_S}{R_S} = 0$$

$$\frac{V_D}{V_S} = -\frac{R_D}{R_S}$$

$$\frac{V_D}{V_S} = -\frac{R_D}{R_S} = -\frac{10k}{10k} = -10$$

$$\frac{V_D}{V_S} = \frac{V_D}{V_S} \frac{V_S}{V_S} = (-10)(-0.91) = -9.1$$

Voltage divider

⑦  
2A

$$\frac{V_D}{V_S} = \left( -\frac{R_D}{R_S} \right) \left( \frac{\frac{1}{G_m} + R_S}{R_S} \right)$$

$$= \frac{-R_D}{\frac{1}{G_m} + R_S} = \frac{10k}{\frac{1}{100} + 1k} = -9.1$$

$$\frac{\frac{1}{G_m}}{R_S + G_m} = \frac{\frac{1}{G_m}}{R_S} \downarrow$$

$$\frac{R_1}{R_1 + R_2} = \frac{\frac{1}{R_2} + \frac{1}{R_1}}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2}} = \frac{G_2}{G_2 + G_1}$$