
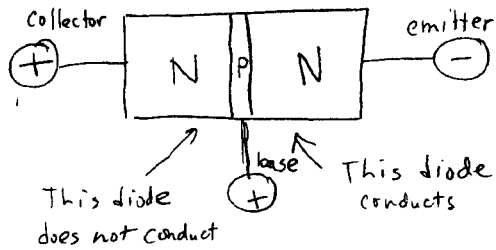


Bipolar Junction Transistors

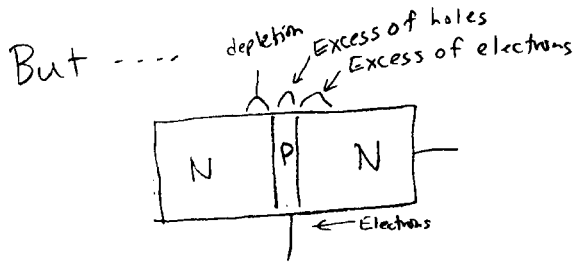

(Very crude explanation)



The excess of holes in the P region is sufficient to overcome the depletion region, making it conduct.

Electrons sweep through the base into the collector.

This conduction is controlled by the base current


→ more base current = more conduction.

6C
1
13A
3

Amplification

Remember diode V/I characteristic
Small change in voltage produces large change in current.
with no collector connection:
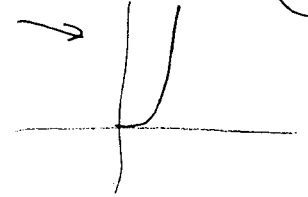
$$I_B = I_E = \text{same as a diode} \\ = I_{ES} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$



I_{ES} = emitter saturation current
= $10^{-12} - 10^{-17}$

$V_T \approx 26 \text{ mV}$

With positive voltage on collector

$I_B = \text{same as before,}$

$$I_E = I_C + I_B$$

$I_C = \text{big compared with } I_B$


$$I_C = \beta I_B$$

"beta" is a parameter that describes this.

$$\beta = \frac{I_C}{I_B}$$

$10 < \beta < 1000$ (usually)

Typical = 100

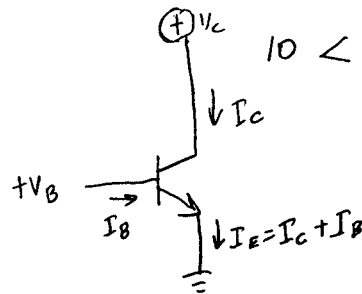

6C
2
13A
4

Other transistor parameters

$$\alpha = \frac{I_c}{I_E} = \frac{I_c}{I_c + I_B} = \frac{\beta I_B}{(\beta + 1)I_B} = \frac{\beta}{\beta + 1}$$

(really says the same as β , but looks different)

$0.9 < \alpha < 0.999$ Typical = 0.99

or ---

$$\alpha = \frac{\beta}{\beta + 1}$$

$$(\beta + 1)\alpha = \beta$$

$$\alpha\beta + \alpha = \beta$$

$$\alpha\beta - \beta = -\alpha$$

$$(\alpha - 1)\beta = -\alpha$$

$$\beta = \frac{-\alpha}{\alpha - 1} = \frac{\alpha}{1 - \alpha}$$

$$I_B = I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1)$$

$$I_C = \beta I_B$$


$$= \beta I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1)$$

$$\approx \beta I_{ES} e^{\frac{V_{BE}}{V_T}}$$

$$\approx I_S (e^{\frac{V_{BE}}{V_T}})$$

↑ "scale current"

Here's a circuit:

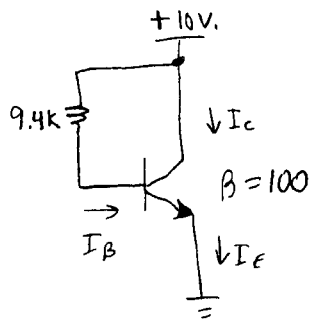

What is I_C, I_B, I_E .

Assume $V_{BE} = -6V$.

$$I_B = \frac{V}{R} = \frac{9.4}{9.4k} = 1 \text{ ma}$$

$$I_C = \beta I_B = 100 \text{ ma}$$

$$I_E = I_C + I_B = 101 \text{ ma}$$


6C
3
13A
5

Example 2: (more detail)

Transistor parameters: $\beta = 100 = 10^2$

$$I_{ES} = 10^{-14}$$

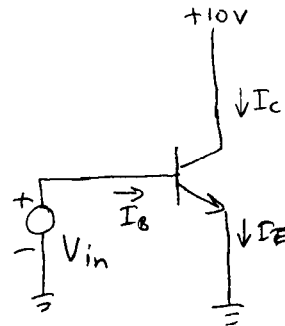Calculate: $I_S = 10^{-12} = \beta I_{ES}$




$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$= 10^{-12} e^{\frac{V_{BE}}{V_T}}$$

V_{BE}	I_C
0	10^{-12}
.1	4.7×10^{-11}
.2	2.1×10^{-9}
.3	1×10^{-7}
.4	4.8×10^{-6}
.5	2.2×10^{-4}
.6	1×10^{-2}
.7	5×10^{-1}
.8	2.3×10^1
.9	1.7×10^3
1.0	5.0×10^4

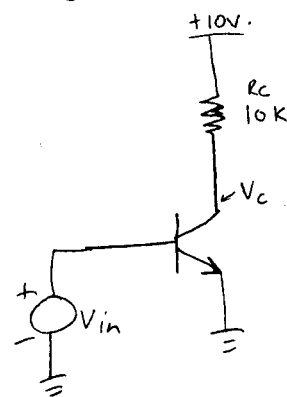Now, put a resistor in series with the collector:



Note Large current change →

Assume it doesn't change I_C .

What is V_C ?

V_{BE}	V_C
0	1×10^{-8}
.1	4.7×10^{-7}
.2	2.1×10^{-5}
.3	1.0×10^{-3}
.4	4.8×10^{-2}
.5	$2.4 \times 10^0 = 2.4$
.6	$1.0 \times 10^2 = 100$
.7	10^3
.8	10^5
.9	
1.0	

} ≈ 0
} > 10

So, for $V_{BE} = .5, V_C = 2.4$.

"saturated"

What if $R = 1k$?

6C
4
13A
6

More detail near .5

V_{BE}	I_c	$V_{RC} = I_c R_c$	Gain = $\frac{\Delta V_{RC}}{\Delta V_{BE}}$
.45	3.2×10^{-5}	.32	$\frac{.16}{-.1} = 1.6$
.46	4.8	.48	
.47	7.0	.7	$\frac{.49}{-.1} = 4.9$
.48	1.04×10^{-4}	1.04	
.49	1.53	1.53	7.1
.5	2.24×10^{-4}	2.24	
.51	3.30	3.30	10.6
.52	4.85	4.85	
.53	7.12	7.12	15.5
.54	1.04×10^{-3}	10.4	
.55	1.53	15.3 Saturated	22.7

With $R_c = 100k$

V_{BE}	V_{RC}
.45	3.2
.46	4.8
.47	7.0
.48	10.4

→ Higher Load resistance
→ Higher voltage gain.

Saturated

6C
5

13A
7

$$n = 0.10$$

$$v_{be} = n / 10$$

$$v_t = .026$$

$$i_c = \exp(v_{be}/v_t) \times 10^{-12}$$


$$V_{RC} = i_c \times 1000$$

← Octave program to calculate tables

6C
B

13A
8

How to use this amplifier:

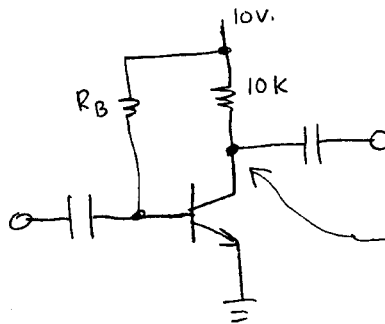

set this voltage to half of the supply (5V).

$$\text{So, } 5V \quad I_c = \frac{5V}{10k} = 5 \times 10^{-4}$$


$$V_{BE} \approx .52 \text{ (from table)}$$

$$\text{So, } V_{RB} = 10 - .52 \approx 9.5$$


$$R_B = \frac{V_{RB}}{I_B} = \frac{V_{RB}}{I_c/\beta} = \frac{9.5}{(5 \times 10^{-4})/100}$$

$$= \frac{9.5}{5 \times 10^{-6}} = 1.9 \text{ Meg.}$$

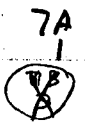Coupling (DC Block) capacitors allow AC signal to pass, maintaining transistor DC Bias.




Transistor characteristic curves.

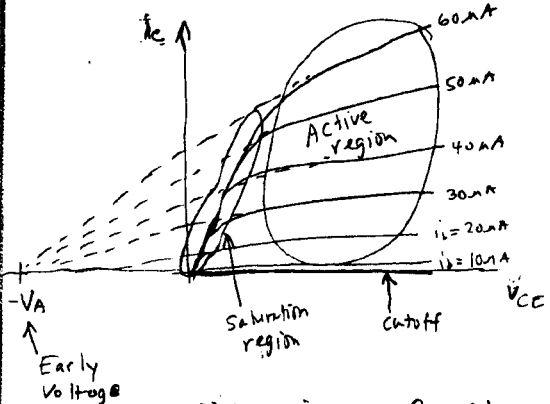

3 regions - Active
Saturation
cutoff.

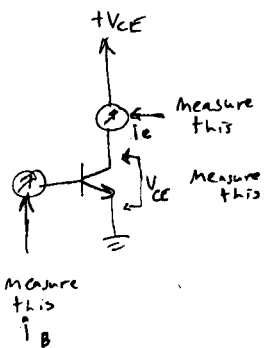
This is a family of curves.
"Common emitter characteristics" -
One curve for each sample V_{BE} .



Hold i_B constant -
sweep V_C
Measure i_C


Examples

①

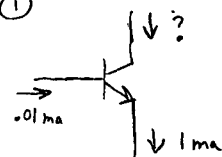

What is β ?
 α ?
 I_C ?

②

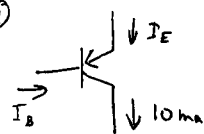

$\beta = 100$
What is I_B ?
 I_E ?

Breakdown - (3.1.6)

Like a zener diode -

When the voltage is too high, it breaks down -
non-destructive, but current can be destructive.