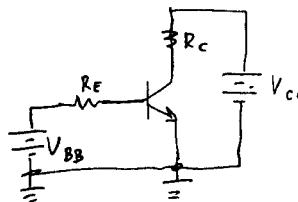



3.2 DC Analysis of Transistor Circuits

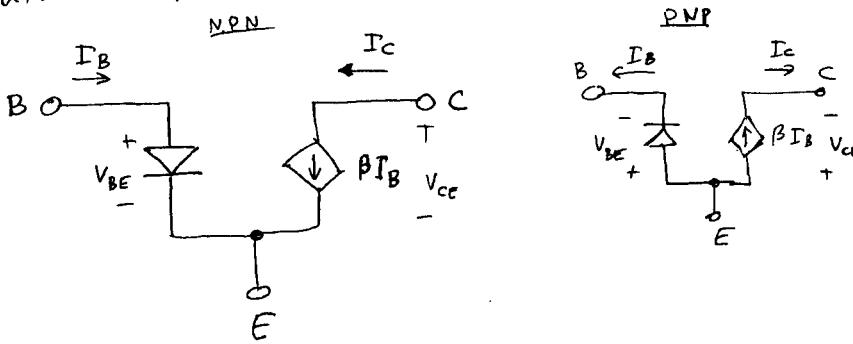3.2.1 Common Emitter Circuit.




What are voltages and currents?

Equivalent circuit of transistor: (Model)




Substitute the model for the transistor, and analyze.

Example:

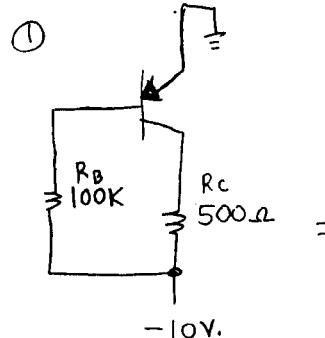

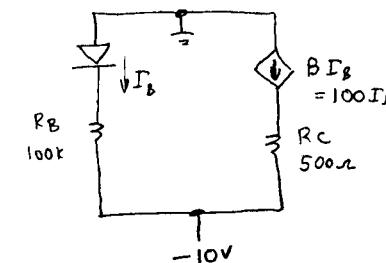Transistor parameters:
 $V_{BE} = .6$ $\beta = 100$




$$V_{RB} = 9.4 \quad I_B = \frac{9.4}{100k} = .094 \text{ mA}$$

$$I_C = \beta I_B = 9.4 \text{ mA}$$

$$V_{RC} = I_C R = (9.4 \text{ mA})(500) = 4.7$$
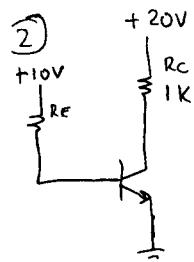
$$V_{CE} = (-10) - (-4.7) = -5.3 \text{ V}$$




$$V_{BE} = .6 \quad \beta = 100$$

What is R_E for $V_{CE} = 10$?


HW:
 Do again
 for
 $\beta = 50, 200, 500$

Load line analysis of transistor circuit

Like a diode

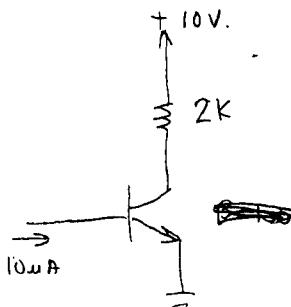

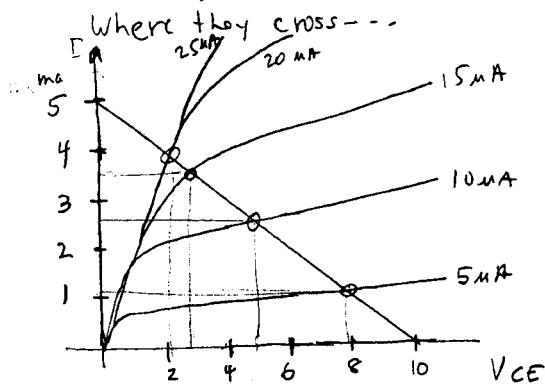Plot transistor curve
and load line on
same graph -



Transistor: I_C vs. V_{CE}

Resistor I vs. $V_{CE} \leftarrow V_{CE} + V_R = 10$

$$\text{so } V_{CE} = 10 - V_R$$

Resistor:		V_R	I	V_{CE}
0	0	0	10	
10	5mA	5	0	


From graph:

I_B	V_{CE}	I_C
10mA	4.9	2.6
5mA	1.1	7.9
15mA	2.8	3.6
20mA	2.1	4.0
25mA	2.1	4.0

] saturation.

Real saturation voltage ≈ 2

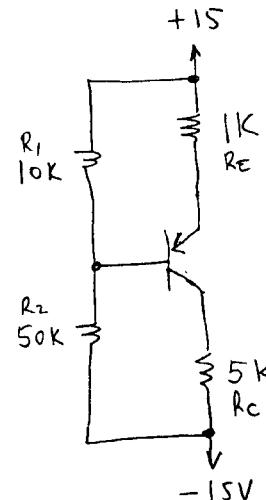Another circuit — Biasing a transistor amplifier



Find operating point.

$$\beta = 50 \quad V_{BE} = -0.6$$

Make Thevenin equivalent of
base circuit.


$$\frac{R_1}{R_1 + R_2} = \frac{V_{R1}}{V_{total}}$$

$$\frac{10k}{60k} = \frac{V_{R1}}{30}$$

$$V_{R1} = \frac{10k}{60k} \times 30 = \frac{30}{6} = 5$$


$$V_{R2} = 2.5$$

$$V_B = 10$$

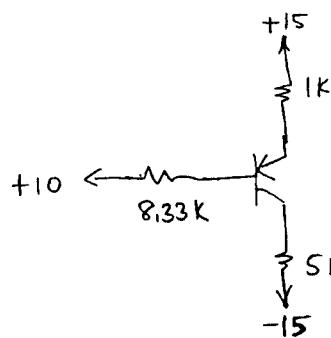


$$\begin{aligned} R &= R_1 \parallel R_2 = \frac{(10k)(50k)}{10k + 50k} \\ &= \frac{500 \text{ Meg}}{60k} \\ &= \frac{50}{6} \text{ k} \\ &= 8.33 \text{ k} \end{aligned}$$

Substitute the model.

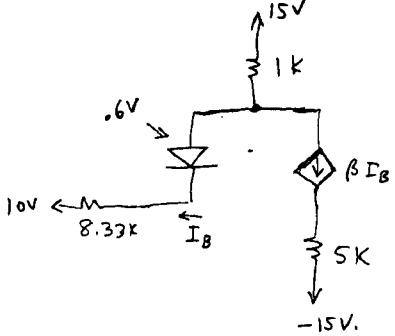

Simplify it

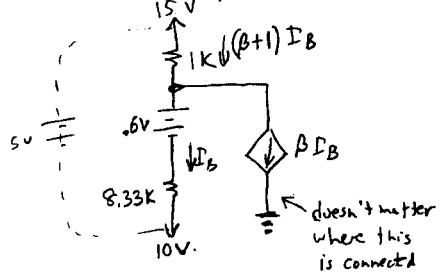

Loop equation.

$$(1K)(\beta+1)I_B + .6 + (8.33K)I_B = 5$$

$$(51K)I_B + .6 + (8.33K)I_B = 5$$

$$(59.33K)I_B = 4.4$$

$$I_B = \frac{4.4}{59.33K} = 7.4 \times 10^{-9}$$

$$= 74 \mu A$$


$$I_C = \beta I_B = .0037 A$$

$$V_{RE} = I R = (.0037)(5000) = 18.5$$


$$I_E = (\beta+1)I_B = .0038 A$$

$$V_{RE} = (.0038)(1000) = 3.8$$

7C
5

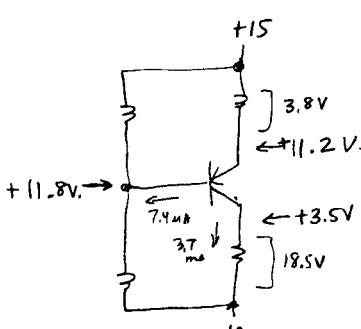

Circuit with Q point.

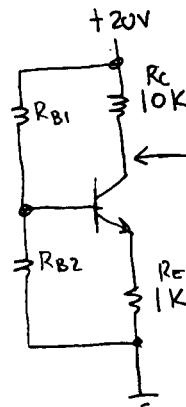

7C
6

Choose R_{B1}, R_{B2}
to get 10V. here

$$\beta = \infty \quad V_{BE} = -0.6$$

$$I_C = \frac{V_{RC}}{R_C} = 1 \text{ mA}$$

$$I_E \approx 1 \text{ mA}$$

$$V_E = V_{RE} = (1 \text{ mA})(1K) = 1$$

$$V_B = V_E + V_{BE} = 1 + .6 = 1.6$$

Choose R_{B1}, R_{B2} for 1.6V at junction.
How about -- $R_{B1} = 16K$ ($I = .1 \text{ mA}$)

$$R_{B2} = \frac{20-1.6}{.1 \text{ mA}} = \frac{18.4}{.1 \text{ mA}} = 184K$$

Any resistors in this ratio will work.
The higher the better, but
you need to account for base current.

Same circuit -
 $10V < V_C < 11V$.

$$\beta > 50 \quad V_{BE} = .6$$


↑
could be infinite

Observe -- Base current makes V_B go down
 which makes V_E go down
 and V_C go up.

Analyze for $\beta = 50$ ($d = \frac{50}{51} = .98$)

$$\text{If } I_C = 1\text{ma}, \quad I_B = .02 \text{ ma}$$

Base resistors equivalent circuit

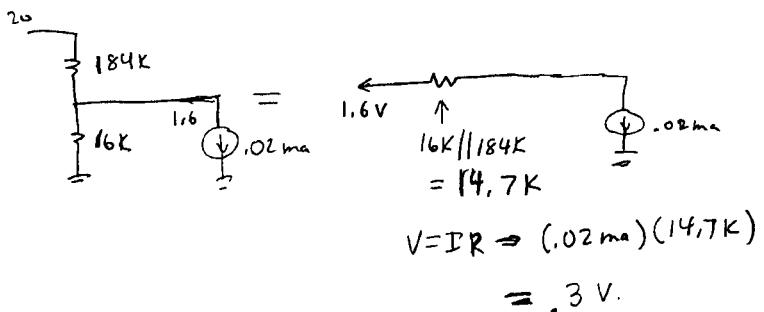

$$V_{RE} = 1.3 - .6 = .7$$

$$I_E \quad I_{RE} = \frac{V}{R} = \frac{.7}{1k} = .7 \text{ ma}$$

$$I_C = \alpha I_E = (.98)(.7 \text{ ma}) \approx .7 \text{ ma} \quad \leftarrow \text{close enough}$$

$$V_{RC} = (.7 \text{ ma})(10k) = 7 \text{ volts.}$$

$$V_C = 13V. \quad \leftarrow \text{out of spec!}$$

7C
6



How to figure R_{B1} , R_{B2} correctly

$$\beta = \infty \quad V_C = 10, \quad V_E = 1$$

$$\beta = 50 \quad V_C = 11, \quad V_E = .9$$

Need base voltage: 1.6 with $\beta = \infty$, $I_B = 0$
 1.5 with $\beta = 50$, $I_B = \frac{.9 \text{ ma}}{50} = .018 \text{ ma}$

Base resistors equivalent circuit:

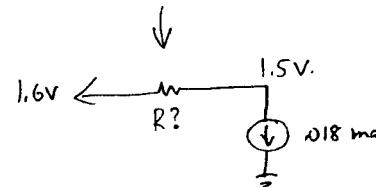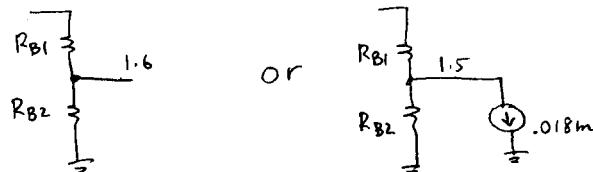

$$R = \frac{V}{I} = \frac{1.6 - 1.5}{.018 \text{ ma}} = \frac{.1}{.018 \text{ ma}} = 5.5556 \text{ K}$$

Value of R_{B1} , R_{B2}
 in Parallel

To get 1.6V, open circuit

$$\text{the ratio must be } \frac{R_2}{R_1 + 18.4} = \frac{V_{R1}}{V_{R2}} \quad \frac{18.4}{1.6} = 11.5$$

$$R_{B2} = 11.5 R_{B1}$$

$$\text{so } \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 5.56 \text{ K} = \frac{(R_{B1})(11.5 R_{B1})}{R_{B1} + 11.5 R_{B1}} =$$

$$5.56 \text{ K} = \frac{11.5 R_{B1}^2}{12.5 R_{B1}} = \frac{11.5}{12.5} R_{B1} \rightarrow R_{B1} = (5.56 \text{ K}) \left(\frac{12.5}{11.5} \right) = 6.03 \text{ K}$$

$$R_{B2} = 69 \text{ K}$$

7C
8