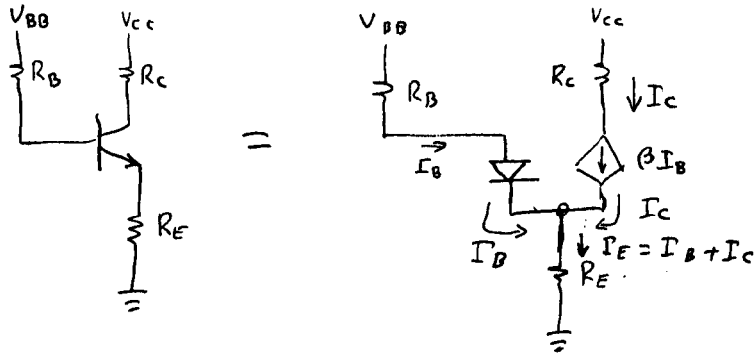


Analysis tricks ...

Moving components through nodes:


Consider this:



Split RE into 2 parts, in parallel:

Part ① has  $I = I_B$  - call it "RE1"  
 Part ② has  $I = I_C$  call it "RE2"

Put them in parallel!

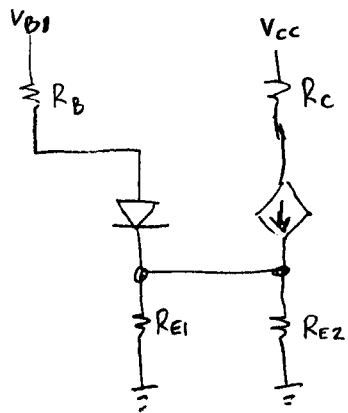

$$V_{RE} = I_E R_E$$

So...

$$R_{E1} = \frac{V_{RE}}{I_B}$$

$$R_{E2} = \frac{V_{RE}}{I_C}$$

8A  
1

ohm's law:

$$V_{RE} = I_E R_E$$

sub for IE:

$$V_{RE} = (I_B + I_C) R_E = (\beta + 1) I_B R_E$$

Values of RE1, RE2:

$$R_{E1} = \frac{V_{RE}}{I_B} = \frac{(\beta + 1) I_B R_E}{I_B}$$

$$R_{E1} = (\beta + 1) R_E$$


$$\approx \beta R_E$$

$$R_{E2} = \frac{V_{RE}}{I_C} = \frac{V_{RE}}{\beta I_B} = \frac{(\beta + 1) I_B R_E}{\beta I_B}$$

$$= \frac{\beta + 1}{\beta} R_E = \frac{R_E}{\alpha}$$

$$\approx R_E$$

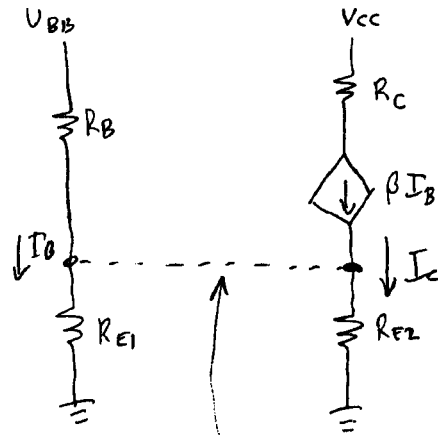$\approx$  is valid when  $\beta \gg 1$ . It usually is.




Treat this as a "virtual short" -  $V=0, I=0$ .


8A  
2

Do last time's example again:

(8A)  
3

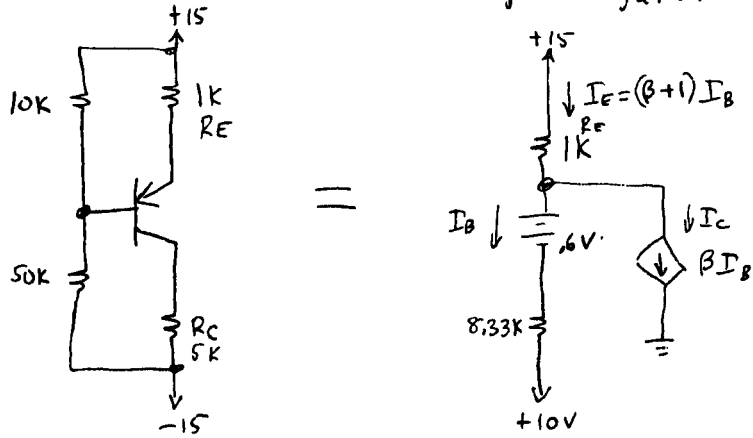

Split  $R_E$ :

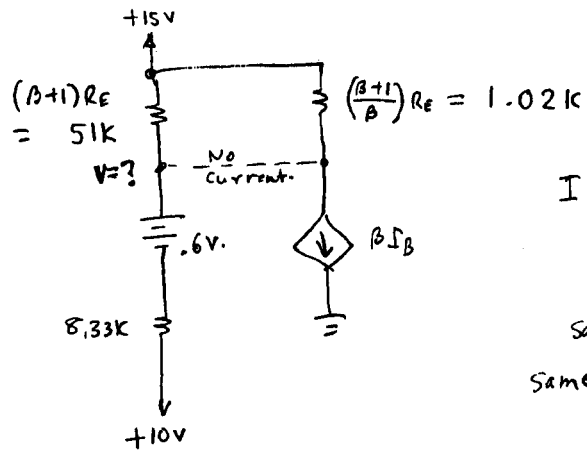

$$I = \frac{15 - 10 - .6}{51k + 8.33k} = 7.4 \times 10^{-5}$$

Same answer  
Same equations, too.