

CONTINUING THE MOPPEL EXAMPLE


$R_1 = 2\text{meg}$   $R_2 = 3\text{meg}$

108  
①

$V_{GS} = 3 \Rightarrow V_{GS} - V_{TH} = 2$

Try saturated:

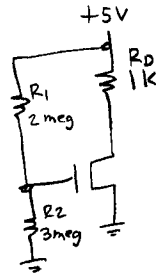$I_D = K (V_{GS} - V_{TH})^2$   
 $= 2 (2)^2$   
 $= 8\text{ ma}$



$V_{RD} = I_D R = (8\text{ ma})(1\text{K}) = 8\text{ volts} ???$

Saturated is a Bad assumption.

Try triode:

$I_D = K (2 (V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$

2 unknowns - need another equation -

$V_{RD} = I_D R_D \Rightarrow I_D = \frac{V_{RD}}{R_D}$   
 $V_{RD} = V_{DD} - V_{DS} = \frac{V_{DD} - V_{DS}}{R_D}$

substitute:

$\frac{V_{DD} - V_{DS}}{R_D} = K (2 (V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$

$\frac{V_{DD}}{R_D} - \frac{V_{DS}}{R_D} = K (2 (V_{GS} - V_{TH}) V_{DS}) - K V_{DS}^2$

$K V_{DS}^2 + (-2K (V_{GS} - V_{TH}) + \frac{1}{R_D}) V_{DS} + \frac{V_{DD}}{R_D} = 0$

Put in values ---

108  
2

$.002 V_{DS}^2 + (-2(.002)(2) - \frac{1}{1000}) V_{DS} + \frac{5}{1000} = 0$

$.002 V_{DS}^2 + (-.008 - .001) V_{DS} + .005 = 0$

$2 V_{DS}^2 + (-9) V_{DS} + 5 = 0$

Quadratic formula -

$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

$a x^2 + b x + c = 0$

$V_{DS} = \frac{9 \pm \sqrt{9^2 - (4)(2)(5)}}{2(2)}$

$= \frac{9 \pm \sqrt{81 - 40}}{4}$

$= \frac{9 \pm \sqrt{41}}{4}$

$= 2.25 \pm 1.601$

because for triode region --  $(V_{GS} - V_{TH}) > V_{DS}$   
 $2 > 3.8 ?$

$V_{DS} = \begin{cases} 3.851 \leftarrow \text{doesn't make sense} \\ .649 \leftarrow \text{this one looks good.} \end{cases}$

$V_{RD} = 5 - .649 = 4.351$

check:  $I_D = \frac{V_{RD}}{R_D} = \frac{4.35}{1000} = .00435\text{ A} = 4.35\text{ mA}$



$I_D = K (2 (V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$   
 $= .002 (2 (2) (.65) - (.65)^2)$   
 $= .00435 = 4.35\text{ mA}$

Matches = good.

# Finding the gain -- Small signal model

(10B)  
3

Recall --- the large signal model:

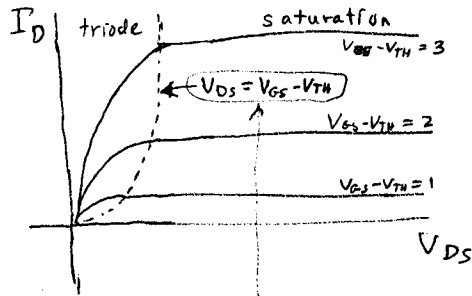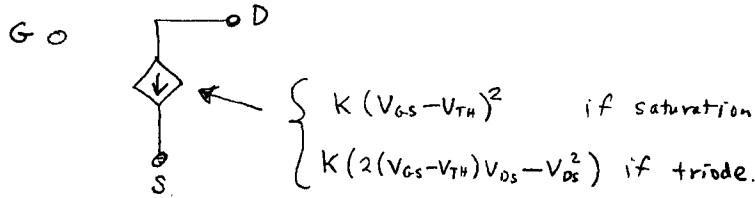

For amplifier --  
use saturation region.

Recall ---


$$I_D = K(V_{GS} - V_{TH})^2$$

want to find  $\frac{dI_D}{dV_{GS}}$  = "transconductance"

$$\frac{dI_D}{d(V_{GS} - V_{TH})} = 2K(V_{GSQ} - V_{TH}) = g_m$$


↑  
constant

So --  $i_d = g_m v_{gs}$

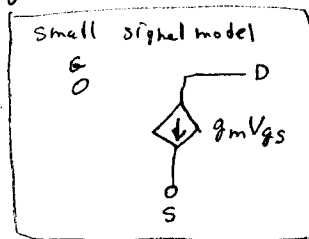


For common source amplifier:


(10B)  
4

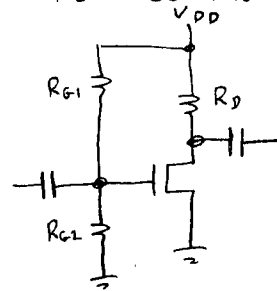

Substitute the model:

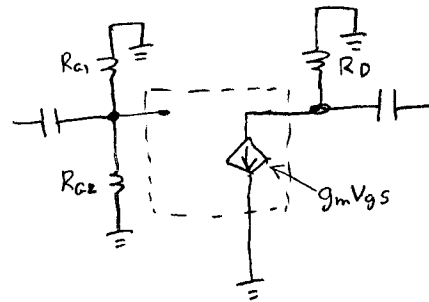

$$V_{in} = V_{gs}$$

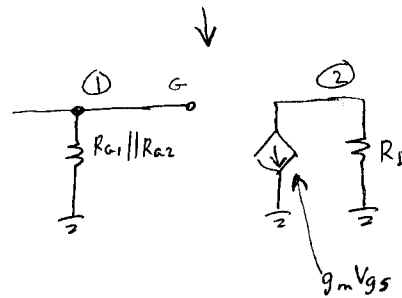


Voltage at node 2:

$$V = IR = g_m R_D V_{gs}$$

$$\frac{V_{out}}{V_{in}} = g_m R_D$$

Example!

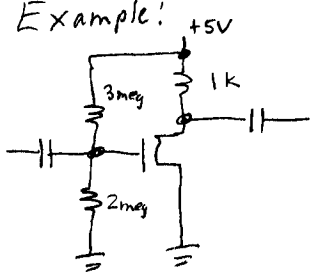

What is voltage gain?

First - check bias - From previous example:  
 $V_{GS} - V_{TH} = 1$      $V_{DS} = 3$      $I_D = 2\text{ma}$

Find transconductance:

$$g_m = 2k(V_{GS} - V_{TH})$$

$$= 2(.002)(1)$$

$$= .004 \frac{\text{Amp}}{\text{Volt}} \quad \text{or} \quad 4 \frac{\text{mA}}{\text{VOLT}}$$

$$\frac{V_{out}}{V_{in}} = g_m R_D = (.004)(1000) = \underline{4}$$

FET gain is lower  
than BJT gain


Note -- With BJT's you can use transconductance, too.

$$g_m = \frac{\beta}{r_{\pi}}$$


10B  
5

Resistor tricks -

our circuit ...

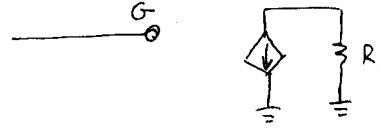

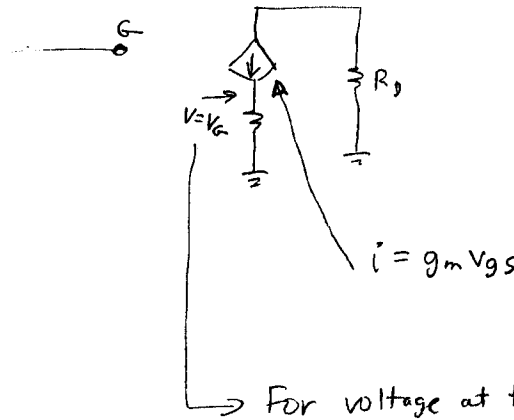Add a resistor in series with the current source




For voltage at this node =  $V_G$

$$V = iR \Rightarrow V_{GS} = (g_m V_{GS}) R$$

$$g_m = \frac{1}{R}$$

so - we can do:

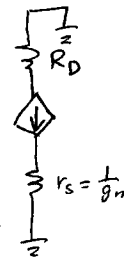

If  $g_m = .004$   
then  $r_s = 250\Omega$

$$\text{Gain} = -\frac{R_D}{r_s} = -\frac{1000}{250} = 4$$

10B  
6