

The diode equation —

10
1

Remembering the formula.

- ① It's exponential (rapid growth in forward region, flat in reverse region)
 $\Rightarrow e^x$
x is related to voltage

- ② Crosses through zero at $V=0$

e^x is always positive
approaches zero for negative x.

is 1 for $x=0$

What is like e^x but = 0 for $x=0$?

$$\Rightarrow e^x - 1$$

- ③ Now, scale it for "reverse saturation current"

so that is the value for negative x.
(above formula is = -1)

$$\Rightarrow I_s (e^x - 1)$$

- ④ x is related to voltage, but how?


$$x = f(V) = \frac{V}{\text{Some } V\text{-reference}}$$

call the reference V_T (thermal voltage)
(and use n as a fudge factor)

$$\Rightarrow I = I_s \left(e^{\frac{V}{nV_T}} - 1 \right)$$

Approximate model of a diode (1,3,2)

IC 2

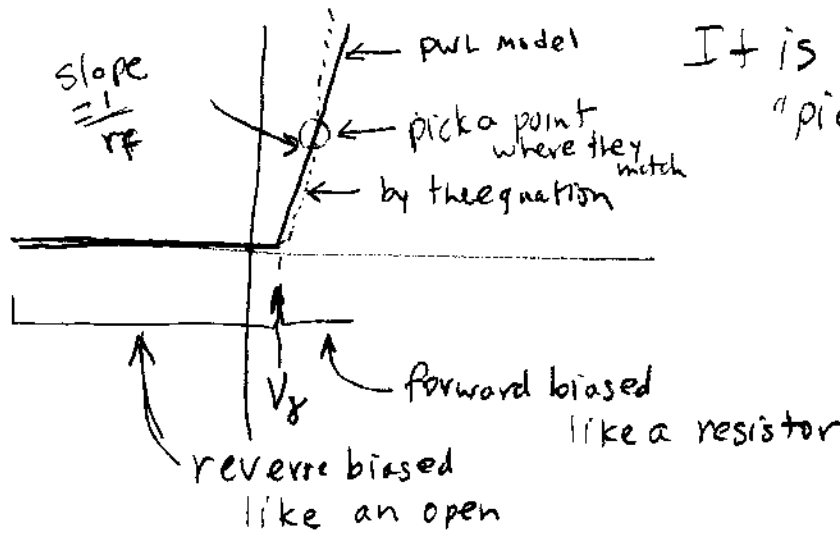

It is close to this "piecewise linear model"


$V_\gamma =$ turn-on voltage

$r_f =$ forward resistance

↑
It varies,
so measure at
some point.

$$I = \begin{cases} 0 & V_D < V_\gamma \\ \frac{V_D - V_\gamma}{r_f} & V_D > V_\gamma \end{cases}$$

A circuit with a diode

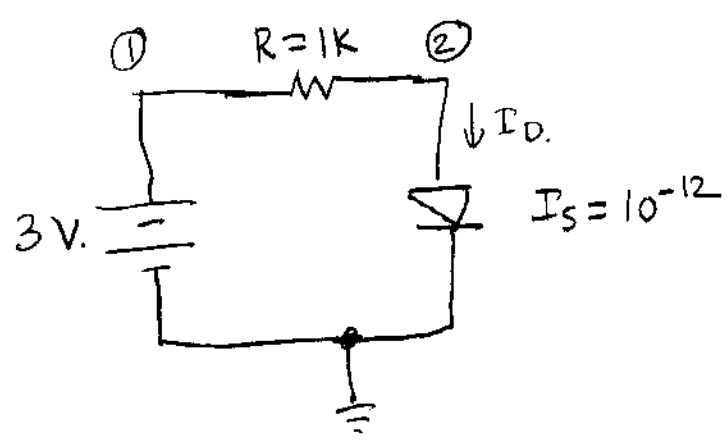

What is V_D ?
 I_D ?

Do nodal analysis at node 2.

Book uses a loop equation
 $V_{\text{battery}} = V_R + V_D$

$$\frac{V_2 - V_1}{R} + I_S \left(e^{\frac{V_2}{V_T}} - 1 \right) = 0$$

$$\frac{V_2 - 3}{1000} + 10^{-12} \left(e^{\frac{V_2}{.026}} - 1 \right) = 0$$

How to solve this? \rightarrow iteration.

Solve for V_2

$$V_2 - 3 + 10^{-9} \left(e^{\frac{V_2}{.026}} - 1 \right) = 0$$

$$V_2 = 3 - 10^{-9} \left(e^{\frac{V_2}{.026}} - 1 \right) = 0$$

Guess -- $V_2 = 1$

Iterate -- $V_2 = -50$

$V_2 = 4 \rightarrow$ diverges

Don't use this method.

Try bisection --

IC
4

Guess $x = f(x)$

1	5×10^7
0	-3
.5	-2.27
.75	3368
.625	25
.562	.0022 ←
.531	-1.7
.546	-1.13
.554	-.65 ←

$$f(x) = V_2 - 3 + 10^{-9} \left(e^{\frac{V_2}{10^6}} - 1 \right)$$

↑
Loop equation.
 $V=0$

between .554 and .562

call it .56.


$$\text{So } \rightarrow V = .56$$

$$I = .0022596$$

(using Octave)

Load line analysis


Try a simple circuit first..

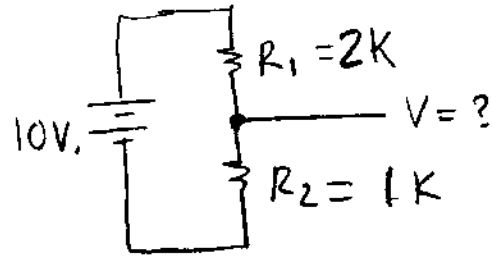

The voltage V is somewhere between 0 and 10 volts.

Plot ① I_{R2} vs. V . $\rightarrow V = V_{R2}$

② I_{R1} vs. V . $V = 10 - V_{R1}$

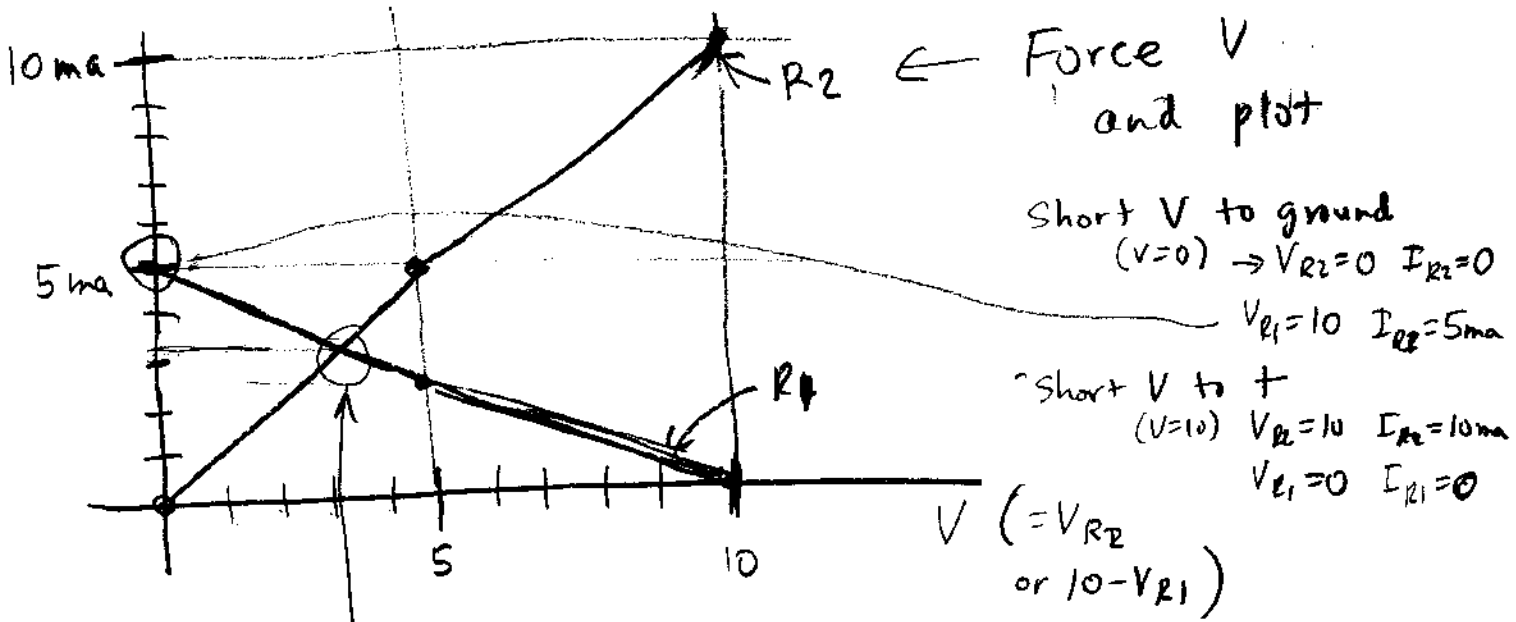


This is the operating point

$$V \approx 3.3 \text{ V}$$

$$I \approx 3.3 \text{ mA}$$

Read it from the graph.


Load line analysis with diode

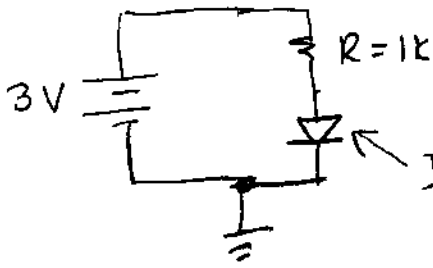

$$I = I_s \left(e^{\frac{V}{V_T}} - 1 \right)$$

$$= 10^{-12} \left(e^{\frac{V}{V_T}} - 1 \right)$$


V	I
0	0
.1	$4.6e-11$
.2	$2.9e-9$
.3	$1e-7$
.4	$4.8e-6$
.5	$2.24e-4$
.6	$1.5e-2$
.7	$4.9e-1$
.8	$2.3e+1$
.9	$1.1e+3$
1.0	$5.1e+4$

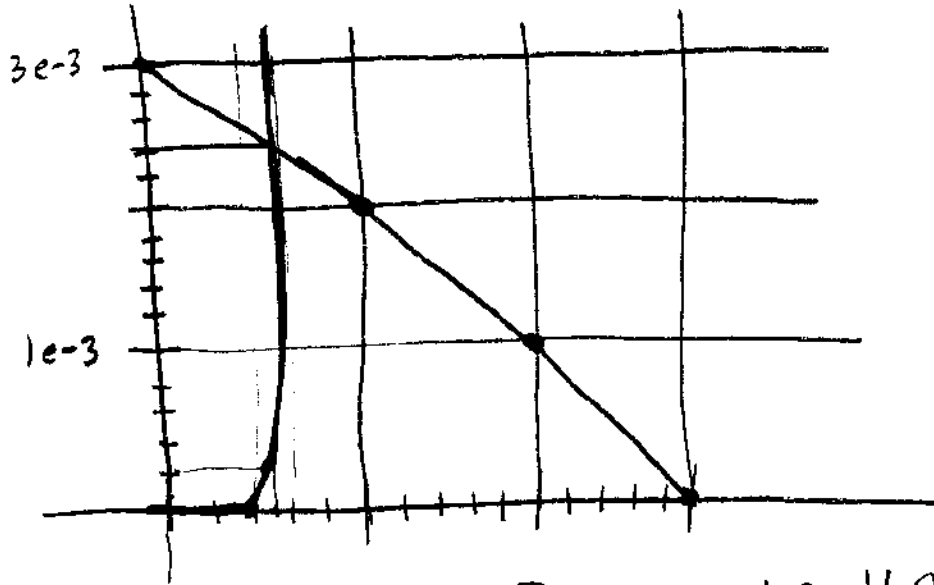

From graph: $V \approx .55$

$I \approx 2.4 \text{ ma}$

Simulation (1.3.3)

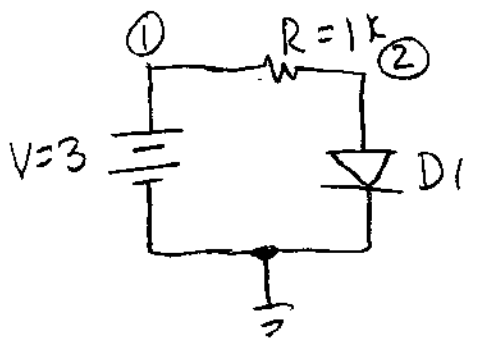

Spice netlist:

```
V1 1 0 DC 3
R1 1 2 1K
D1 2 0 MYDIODE
```


New for Diode

```
.model my diode : D IS = 1E-12
.print op V(D1) I(D1)
.OP
```


V = .55907

I = .0024409

Diode element:

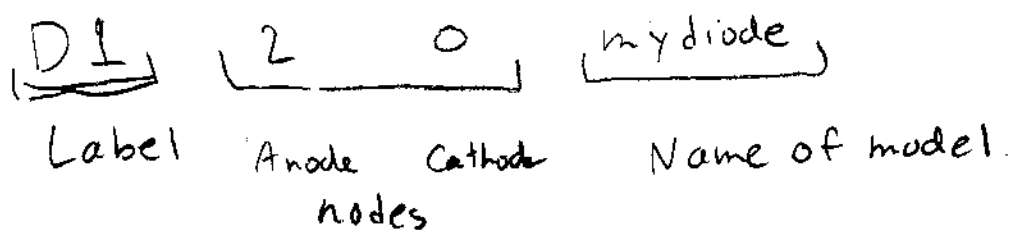

Diode model statement:

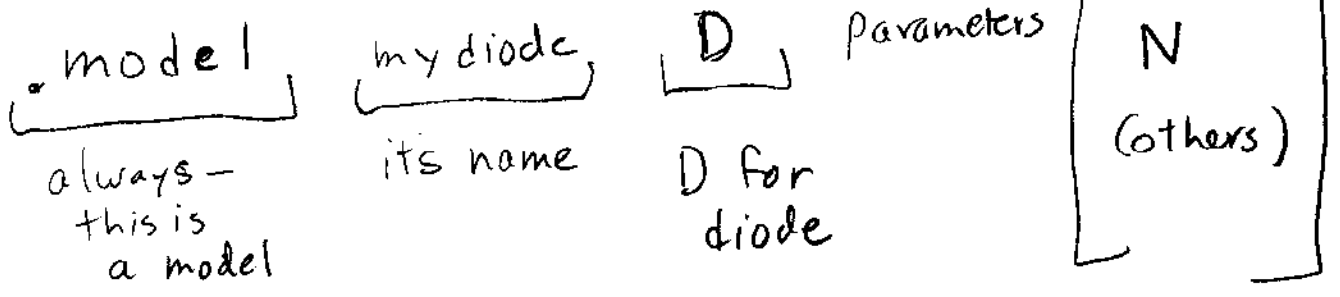

Exercises (not to hand in)

Page Exercise

26 13, 14

29 15 Do c first.

16

44 25

27

32

] Some added complexity -
node or mesh analysis.