

Diode circuits

203
1

Outline:

- 0 - simple transfer function
- 1 - Rectifier
- 2 - Zener diode
- 3 - Clipper & clamper
- 4 - Multiplier diode
- 5 - Photo & LED

Diode circuits for simple transfer functions

We want: —



A simple circuit with a nonlinear in-out characteristic.

Example: A clipper circuit —



Output is limited to ± 10 Volts

OUT


(Assume $V_D = 0.6$)

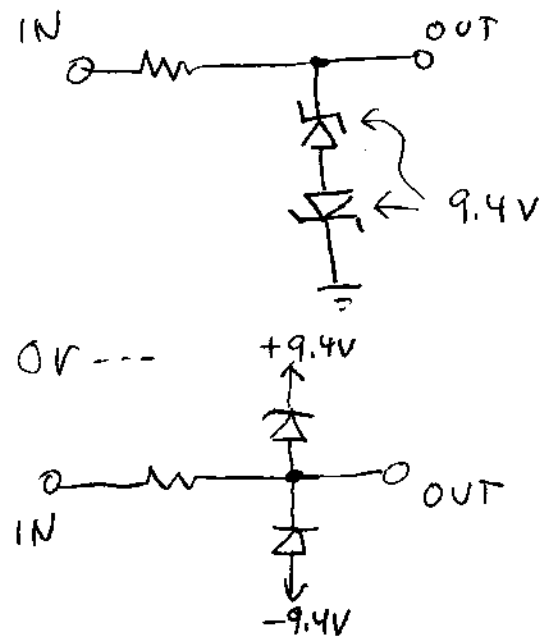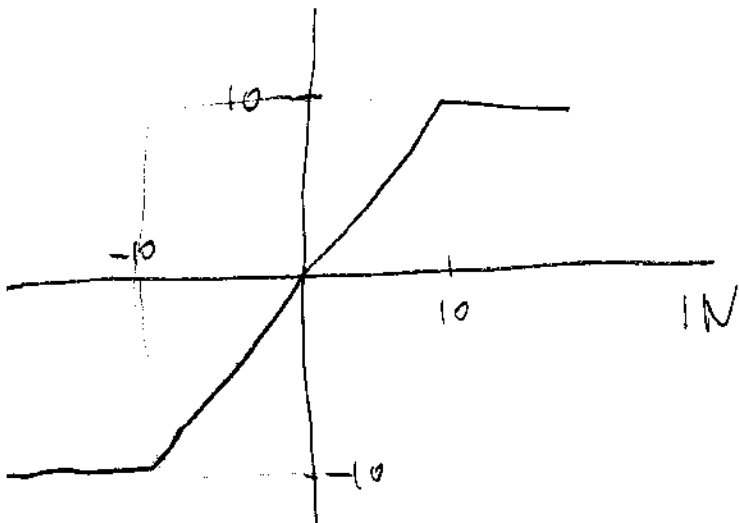

A nonlinear resistor

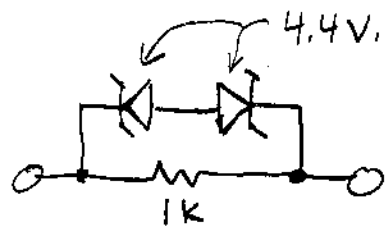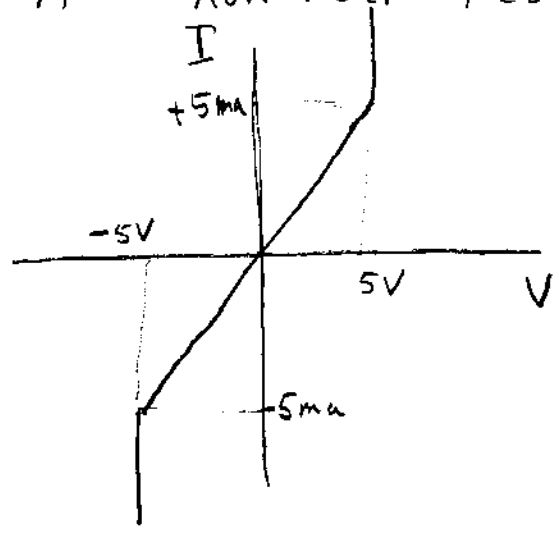

or--

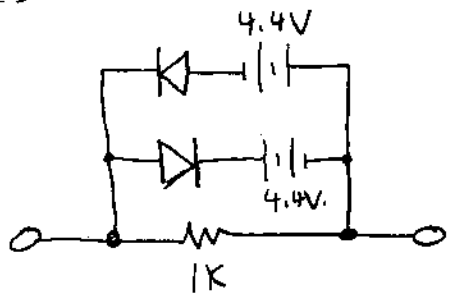


"Rectifier" circuits

(Diodes in Power supplies)


Design requirement:

We need to supply DC power
at a particular voltage,
but we have only AC (60Hz).

Idea:

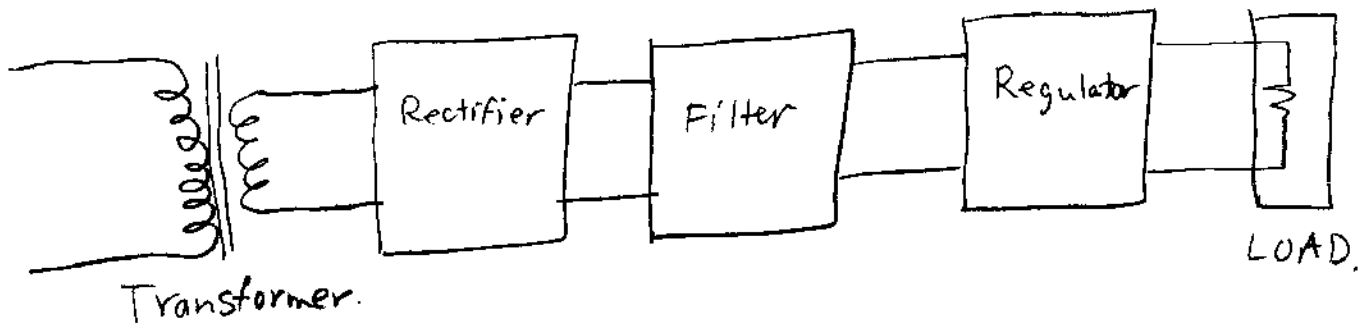

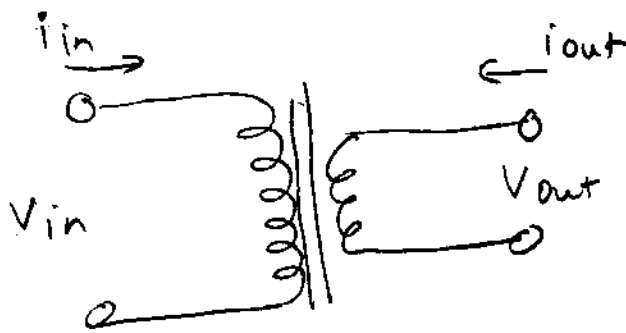A transformer converts one voltage (review)?
to another, determined by the
turns ratio




$$\frac{V_{in}}{V_{out}} = \frac{\text{primary turns}}{\text{secondary turns}}$$

$$\frac{i_{in}}{i_{out}} = \frac{\text{secondary turns}}{\text{primary turns}}$$

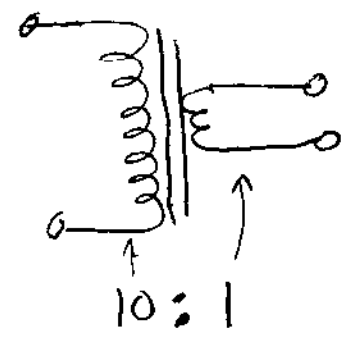Example: We need 12 volts
We have 120 volts.

$$\text{Turns ratio} = \frac{120}{12} = 10 \left(\frac{\text{primary}}{\text{secondary}} \right)$$



10:1
usually specified this way.

No standard on which goes first!

(We didn't say exactly how many turns - just the ratio.)

Current ratio - suppose the secondary current is 1 Amp.

What is the primary current? _____

For 1 Amp, the resistance of the load must be 12 ohms.


What do I see looking into the primary? _____

For a turns ratio of N:1


What is "impedance" ratio? _____

(This should be 313 review).

Half wave rectifier (2.1.1)

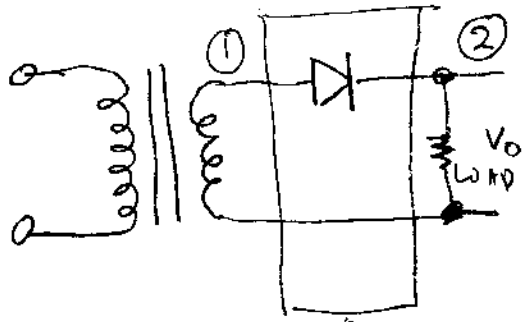


Voltage at ① ②
One graph!

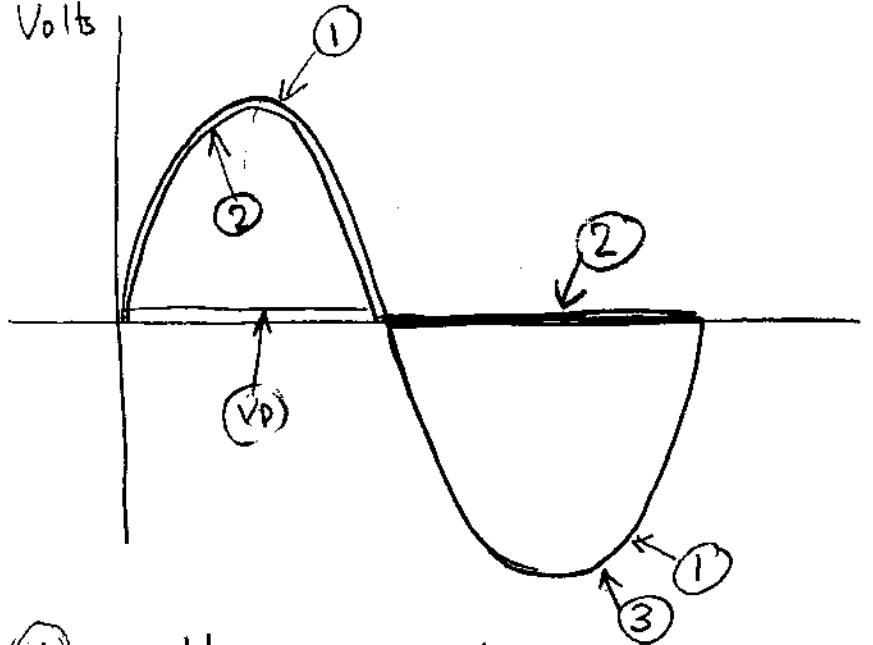


① = voltage across diode

3 graphs!

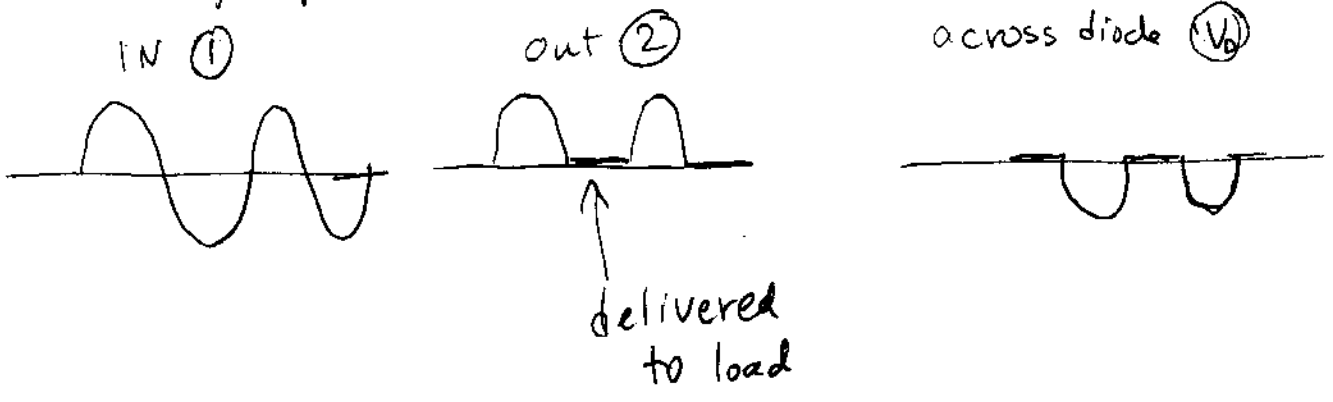


Full wave rectifier (2.1.2)

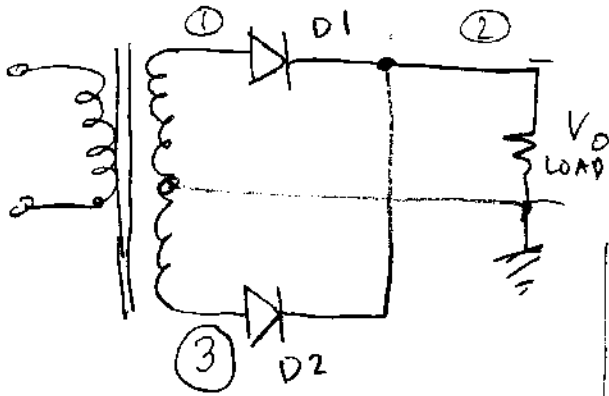
By adding another secondary, we can get both sides.



one graph:

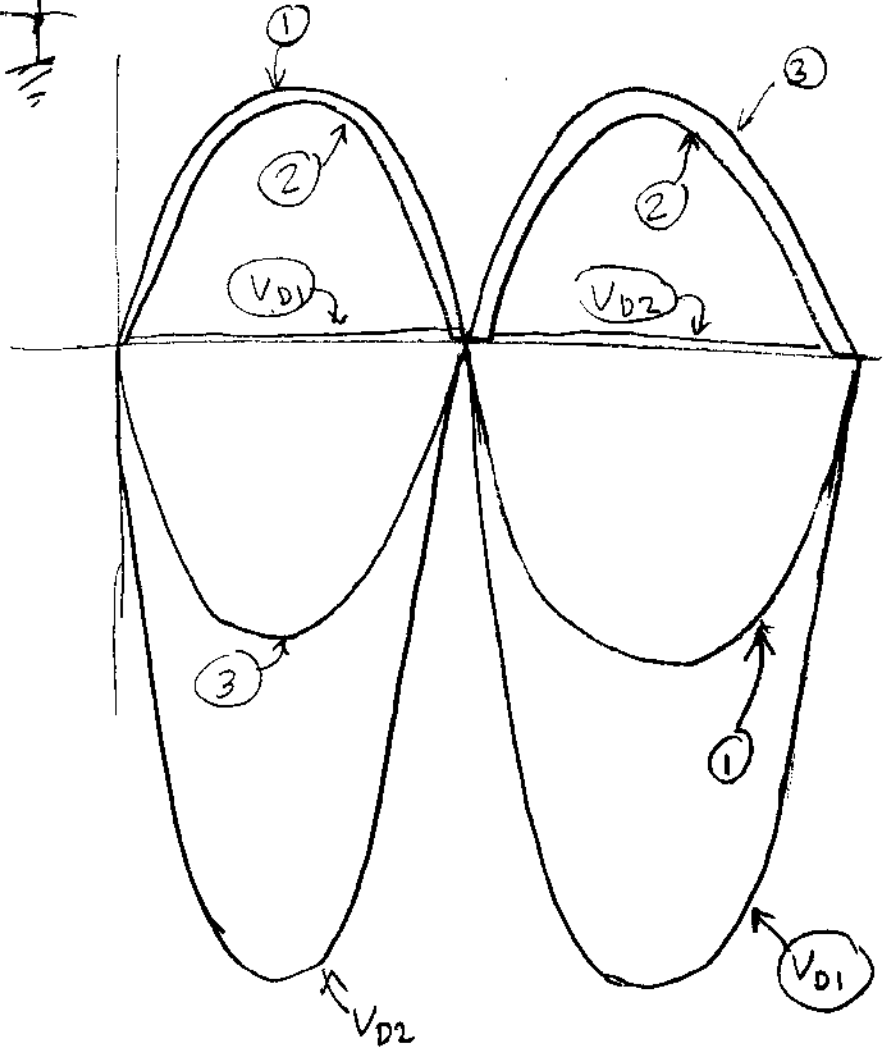

5 graphs

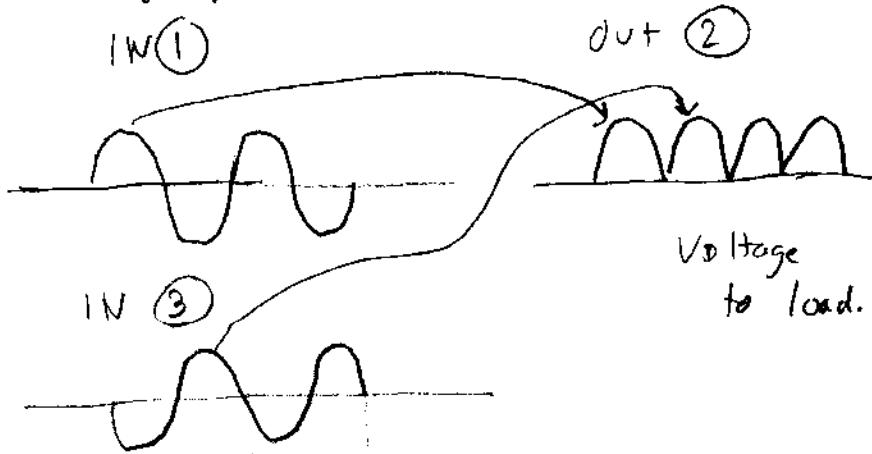

Advantages:

- ← Twice the frequency
- Smoother
- Easier to filter.

Disadvantages:


- Twice the reverse diode voltage.

Bridge rectifier

20
7

Instead of the extra secondary, use an extra pair of diodes;


Half wave:

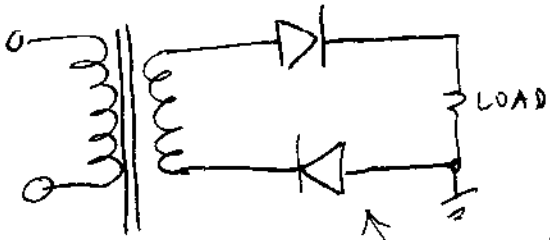

works like the old half wave rectifier


Two diodes in series are redundant, but leads to an idea:

Full wave.

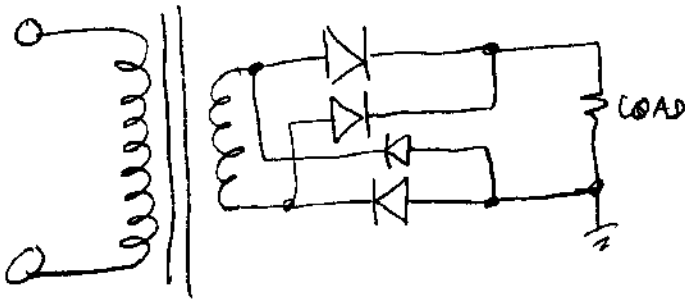

Works almost like the other full wave, without the extra winding.

usually draw it like this:

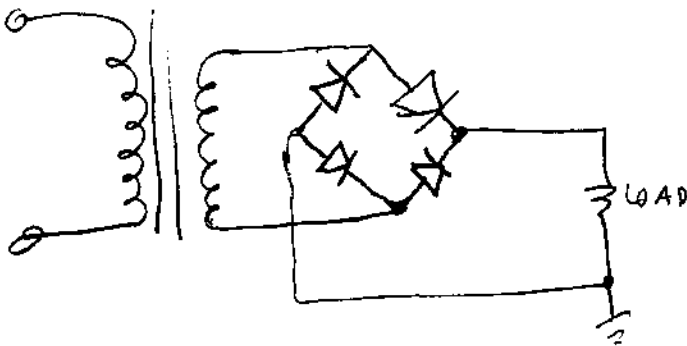



Advantages:

Like other full wave
Same reverse voltage as half wave


Disadvantages

Twice the diode loss.

Positive half

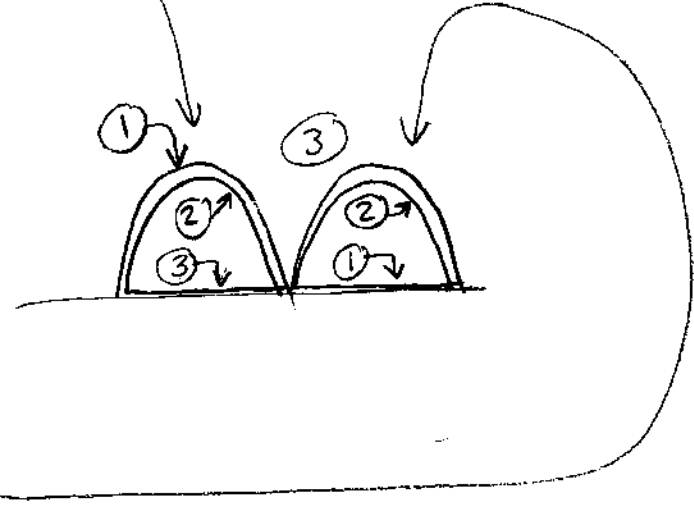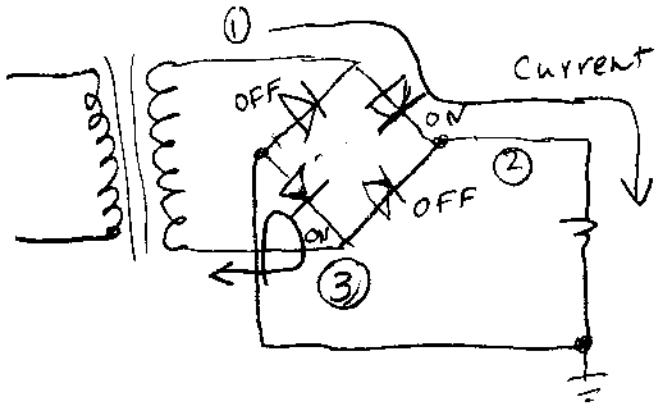

Negative half

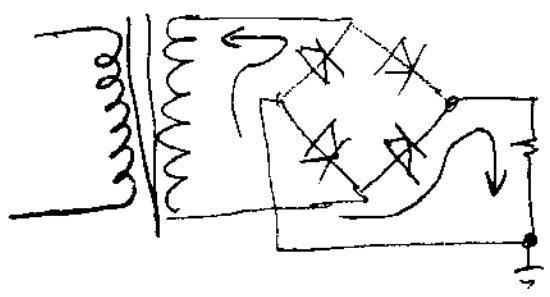

Using a bridge for both positive and negative voltages

