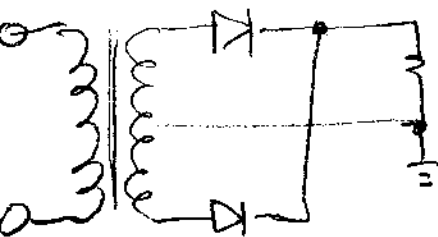


Power supply filters (2.1.3)


Recall ---

A rectifier puts out something like this!




We want DC, without ripple.

Idea: Add a capacitor

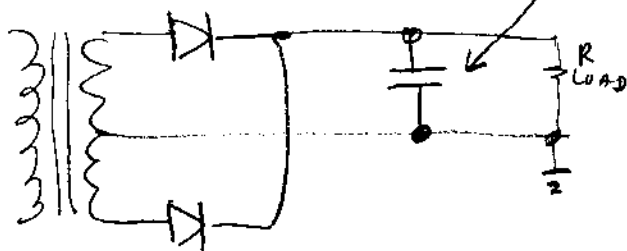

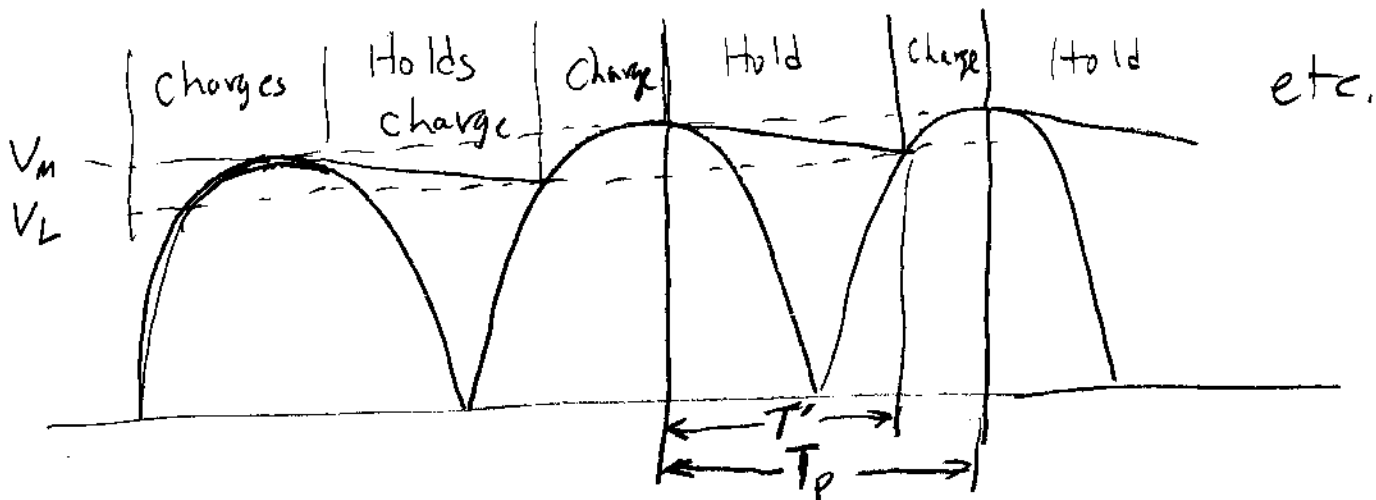It charges when the diode is on, then holds the charge.




The capacitor holds the voltage to nearly the peak voltage.

The diode is only on for a short period at the peak (marked "charge" here).
The output has a small (?) ripple.

Recall --- The formula for a capacitor voltage decaying --


$$V_o(t) = V_m e^{-\frac{t}{\tau}}$$

t = time s/n
 τ = time constant
= RC

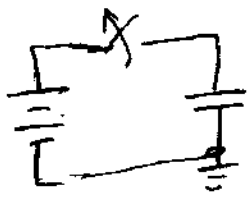

← Switch opens at $t=0$

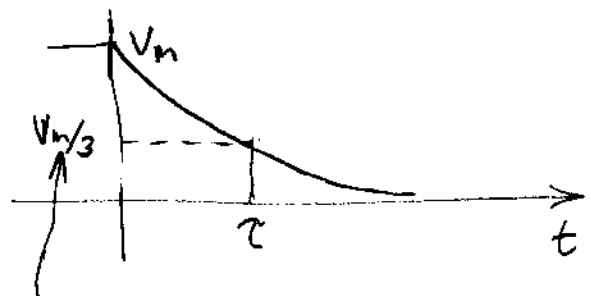(It is like the input dropping so the diode turns off)



For power supply filters,
we can only tolerate
a little ripple,
so τ is much longer
than the ripple period. (T_p)
(time between peaks)

approximately.
(Actually -- $.368 V_m$
 $.368 = e^{-1} \approx \frac{1}{3}$)

The smallest output voltage is when the
diode turns back on -- after time T'

$$V_L = V_m e^{-\frac{T'}{\tau}}$$

Ripple voltage is the difference --

$$V_r = V_m - V_L = V_m \left(1 - e^{-\frac{T'}{\tau}}\right)$$

Recall --

3A
3

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$$

(Taylor series)

If x is small, $1+x$ is a good approximation.

so...

$$e^{-\frac{T'}{\tau}} \approx 1 - \frac{T'}{\tau}$$

$$V_r \approx V_M \left(1 - \left(1 - \frac{T'}{\tau} \right) \right)$$
$$= V_M \left(\frac{T'}{\tau} \right)$$

T' is a little less than T_p .
and hard to solve

Substitute T_p for T' -

The error is small and in the
safe direction.

so (also sub. $\tau = RC$)

$$V_r \approx V_M \left(\frac{T_p}{RC} \right)$$

Actual ripple
will be a little less.
This is close enough.

For half wave rectifier

$$T_p = \frac{1}{f}$$

f is the AC "signal?"
frequency,

For full wave rectifier

$$T_p = \frac{1}{2f}$$

Example:

A power supply must deliver 100 volt at 100 ma with less than 10 volts (peak to peak) ripple. What is C? for half wave? full wave?

Power frequency = 60Hz.

Solution: $R_{LOAD} = \frac{100V}{.1A} = 1000 \Omega$

$$V_r \approx V_m \left(\frac{T_P}{RC} \right) \Rightarrow C \approx \frac{V_m}{V_r} \frac{T_P}{R} \approx \frac{V_m}{V_r R f}$$

$$\frac{V_m}{V_r} = 10 \quad R = 1000 \quad T_P = \begin{cases} \frac{1}{60} = .0167 \\ \frac{1}{120} = .008333 \end{cases}$$

Half wave:

$$C = \frac{100}{(10)(1000)(60)} = 167 \mu f$$

Full wave:

$$C = \frac{100}{(10)(1000)(120)} = 83.3 \mu f$$

Normally, you will use the next larger standard value \rightarrow 100 μf for full wave
200 or 220 μf for halfwave.

Variants of the formula --

$$C = \frac{V_m}{V_r} \frac{T_p}{R}$$

With current -- $V_m = IR$

$$C = \frac{IR}{V_r} \frac{T_p}{R} = \frac{I T_p}{V_r}$$

← Usually, this is the easiest form to use.

$$\text{or } C = \frac{I}{V_r f}$$

Half wave : $C = \frac{.1}{(10)(60)} = 167 \mu\text{f}$

Full wave : $C = \frac{.1}{(10)(120)} = 83.3 \mu\text{f}$



Diode current and Capacitor current

(3A)
6

Diode current flows only in a small part of the cycle, yet load current flows continuously.

It comes from the capacitor.

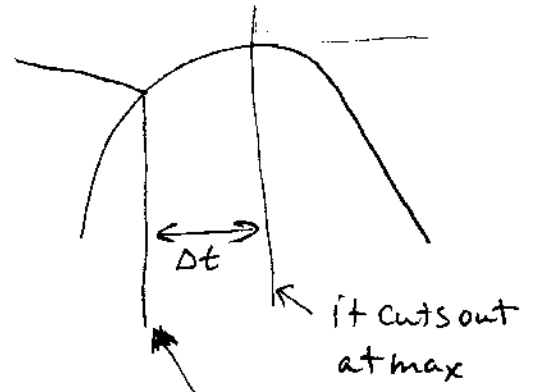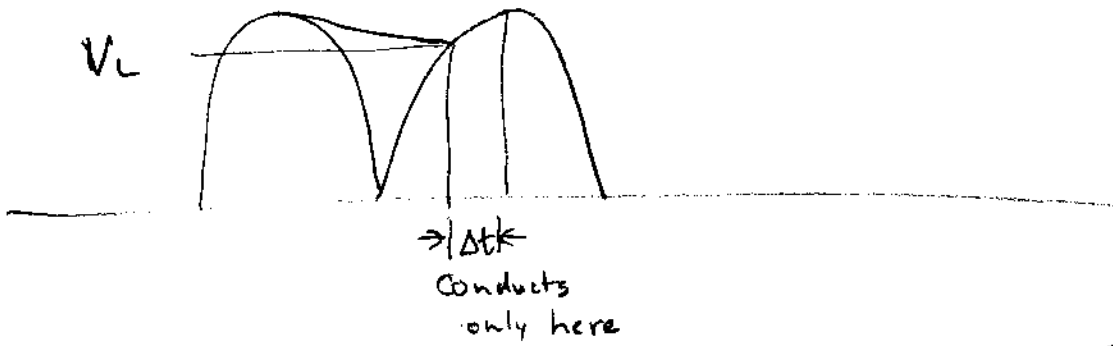Peak current is much higher than average current.



To calculate Δt ----

$$V_L = V_M \cos(\omega \Delta t)$$

Taking the first 2 terms of the Taylor series -

$$\cos(x) \approx 1 - \frac{1}{2} x^2$$

$$V_L = V_M \left(1 - \frac{1}{2} (\omega \Delta t)^2 \right)$$

$$V_M - V_r = V_M \left(1 - \frac{1}{2} (\omega \Delta t)^2 \right)$$

$$V_M - V_r = V_M - \frac{V_M}{2} (\omega \Delta t)^2$$

$$V_r = \frac{V_M}{2} (\omega \Delta t)^2$$

$$\frac{2V_r}{V_M} = (\omega \Delta t)^2$$

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_M}}$$

$$\Delta t = \frac{\sqrt{\frac{2V_r}{V_M}}}{\omega}$$

Example:

$$\Delta t = \frac{\sqrt{\frac{2(10)}{100}}}{2\pi 60} = 1.18 \times 10^{-3}$$

example:
 $\sqrt{\frac{2(10)}{100}} = .44$ rad
 $= 25 \text{ deg.}$

in here --
at min

Charge lost by capacitor to load;

$$Q = CVr \quad \text{also} \quad Q = IT_p \quad (Q = \frac{di}{dt})$$

This charge must be restored when the diode is on..

$$Q = i_{cap} \Delta t$$

↑ ↑
avg. current during charge Charge time

Example:

$$Q = (167 \mu F)(10) = 1.67 \times 10^{-3} \text{ coul.}$$

Example:

$$i_{cap} = \frac{1.67 \times 10^{-3}}{1.18 \times 10^{-3}} = 1.415 \text{ Amp.}$$


$$i_{cap} = \frac{Q}{\Delta t}$$

Diode current = cap current + load current

$$i_{diode} = i_{cap} + i_{load}$$

$$i_D = 1.415 + 0.1 = 1.515$$

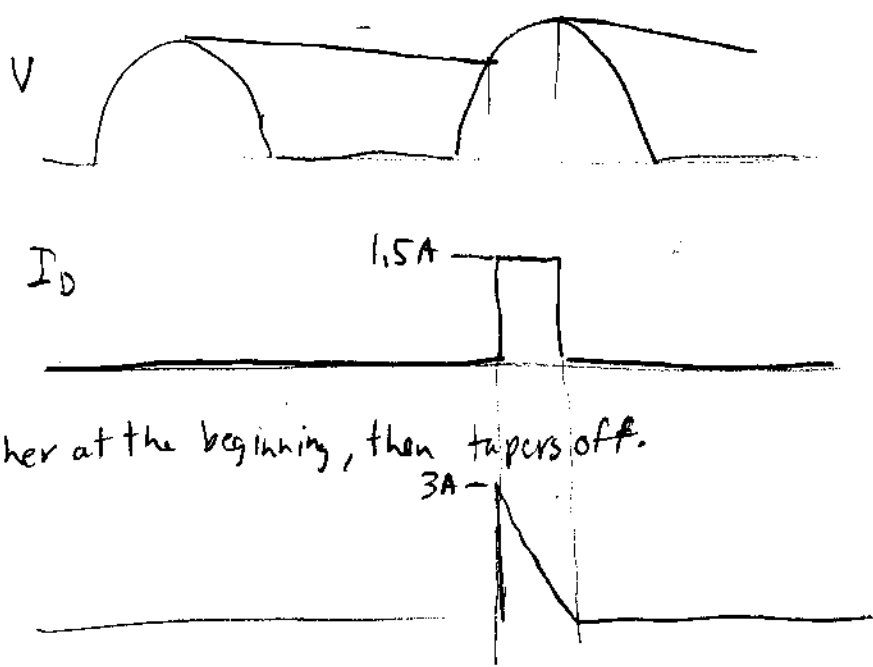But that assumes it is uniform:
It isn't.



Actual is higher at the beginning, then tapers off.

It is roughly triangular,
so the peak is about twice the average.
(3A for this example.)

Exercises:

3A
8

(Not to hand in)

<u>P</u>	<u>#</u>
61	1
62-63	2, 3, 4, 5
87	4, 8, 11

To hand in:

P. 95 D 2.53

It doesn't come out exact.

Get as close as you can.

Assume $V_D = 0.7$

What is peak diode current?

peak inverse diode voltage?