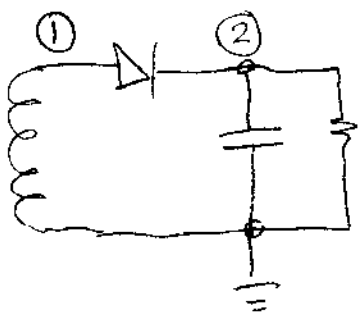


Reverse voltage across diodes - with filter


Here's a circuit




Recall ...
The output voltage is: (node 2)



The voltage at node 1 is:

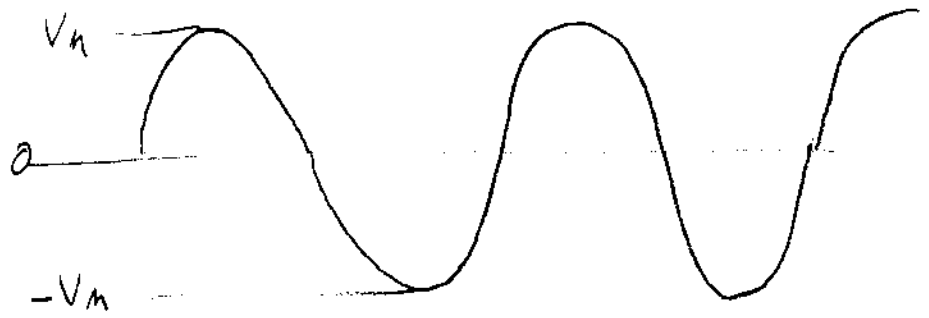

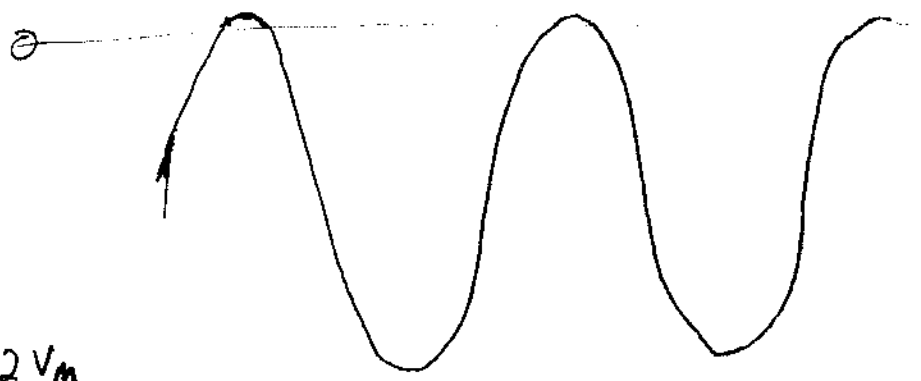The voltage across the diode is:
(V(2) - V(1))



The peak voltage across the diode is twice the max delivered voltage.



$\approx -2V_m$

Twice what it was with no capacitor.


What about full wave? _____

bridge? _____

Designing a power supply

3B
2

① Pick a topology

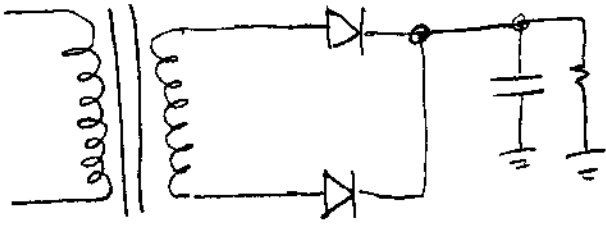

② Determine V_m , V_L from specs.

③ Take V_m .

Add voltage lost in diodes.

④ Add transformer loss.
(like a resistance)

→ This is peak secondary voltage

⑤ Convert to RMS if needed.
(depends on specs)

⑥ Calculate turns ratio
 $\frac{V_{sec}}{V_{pri}}$ or $\frac{V_{pri}}{V_{sec}}$

Express as $n : 1$ (step down)
or $1 : n$ (step up)

⑦ Determine capacitor value

⑧ Determine voltage, power, current ratings of components.

Example

313
3

You are designing a power supply for the high voltage on a cathode ray tube.

Your power source is 7 volts AC (10 volts peak)
20 KHz

The supply must deliver 20-25 kV.
(25 kV max, 20 kV min, 5 kV max ripple)

With a load current of 1 ma.


Assume a 10 volt drop in the diode.
(It is really 16 diodes in series.)

Choose a topology.

Then find:

- Turns ratio (pri : sec)
- Capacitor
- Voltage rating of diode
- Peak diode current
- Average primary current
- Power delivered to load

Topology: half wave.

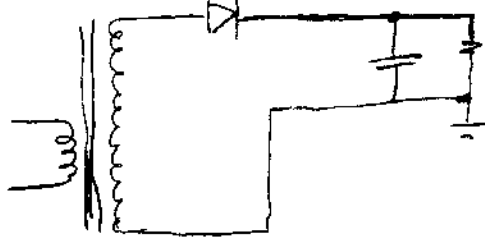

Ignore 10 volt diode loss.

$$V_m = 25 \text{ KV}$$

$$V_L = 20 \text{ KV}$$

$$V_r = 5 \text{ KV.}$$

Ignore transformer resistance.

Power delivered to load:

$$(25 \text{ KV})(1 \text{ ma})$$

$$= 25 \text{ watts}$$

Average primary current

$$(1 \text{ ma})(2500) = 2.5 \text{ A.}$$

$$\text{Turns ratio} = \frac{25000}{10} = 2500$$

$$1:2500$$

Capacitor:

$$C = \frac{I}{V_r f}$$

$$= \frac{1 \times 10^{-3}}{(5 \times 10^3)(2 \times 10^4)}$$

$$= 10 \times 10^{-12}$$

$$= 10 \text{ pF}$$

Voltage rating of diode:

$$50 \text{ KV.}$$

(10 5KV diodes)

Peak diode current:

$$Q = CV = (10^{-11})(5 \times 10^3)$$

$$= 50 \times 10^{-9}$$

$$= IT_p = (10^{-3})(50 \times 10^{-6})$$

$$= 50 \times 10^{-9}$$

$$\Delta t = \frac{\sqrt{\frac{2V_r}{V_m}}}{\omega} = \frac{\sqrt{\frac{(2)(5)}{25}}}{2\pi(20 \text{ K})}$$

$$= \frac{\sqrt{\frac{10}{25}}}{126 \times 10^3} = \frac{.632}{126 \times 10^3}$$

$$= 5 \times 10^{-6} = 5 \mu\text{S}$$

$$i_{\text{cap}} = \frac{Q}{\Delta t} = \frac{50 \times 10^{-9}}{5 \times 10^{-6}} =$$


$$= 10 \text{ ma (avg when on)}$$

$$i_{\text{cap}} \approx 20 \text{ ma.}$$

peak


Voltage multiplying circuits (2.1.4)

Voltage doubler:

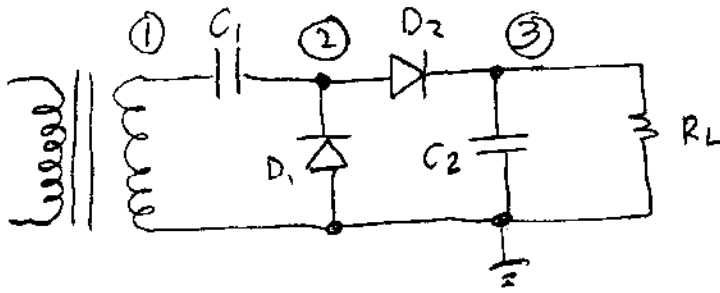

Negative half cycle:

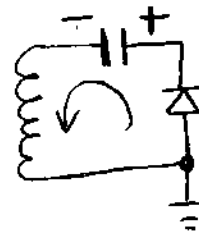D_1 is on. D_2 is off.
 C_1 charges to the peak voltage.




Positive half cycle


D_1 is off D_2 is on

Since C_1 is charged and it is AC coupled,

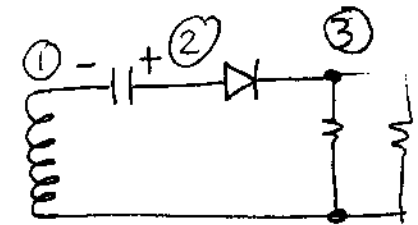The peak voltage is twice the input peak.




Waveforms

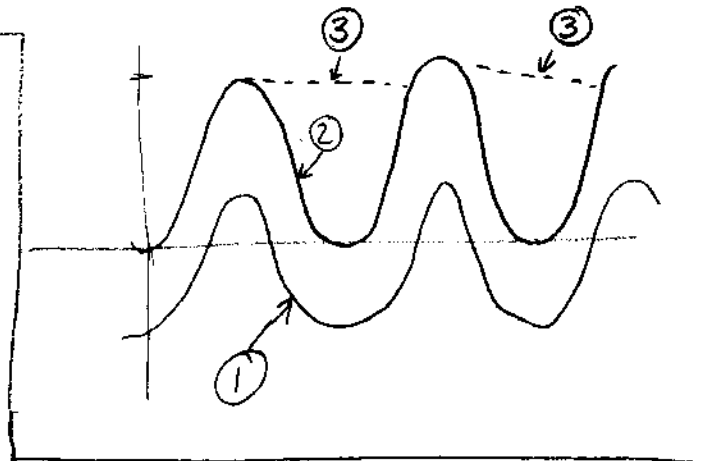


The book's circuit.

Move C_1

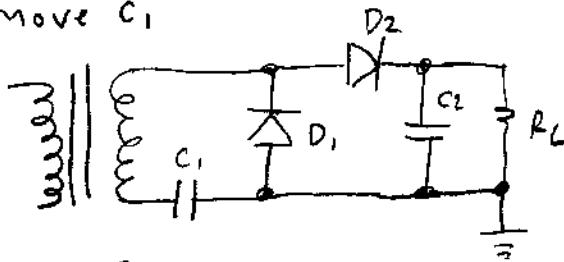


Move C_2

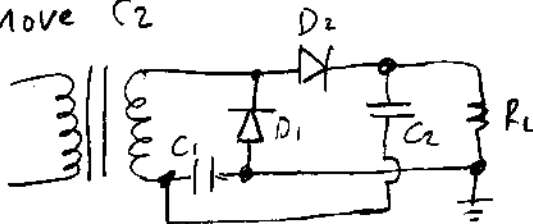


Higher voltages

It is AC coupled, so you can repeat.

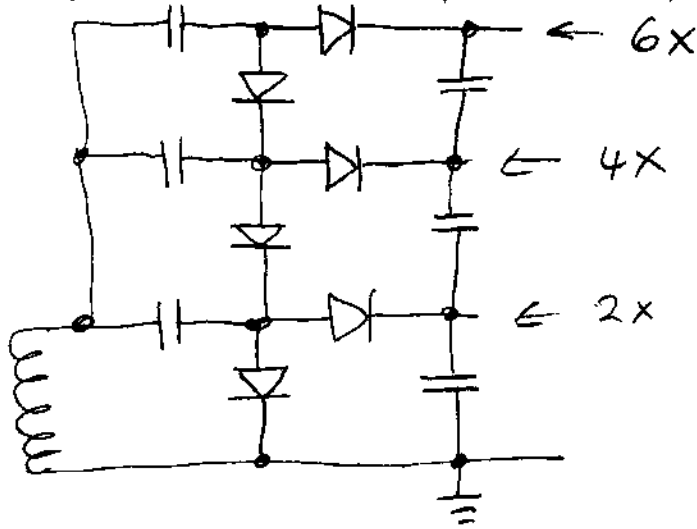


Used when you need a high voltage at low current.


You don't even need a transformer;

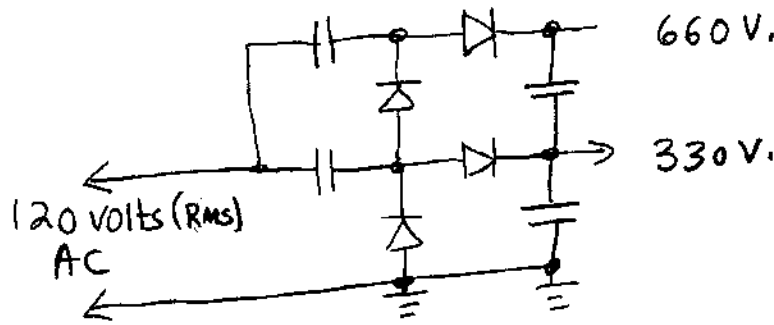

The book's circuit - another view

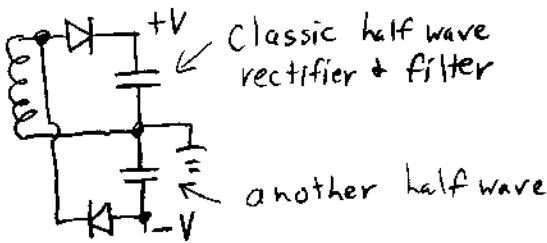

Move the ground so it is all positive

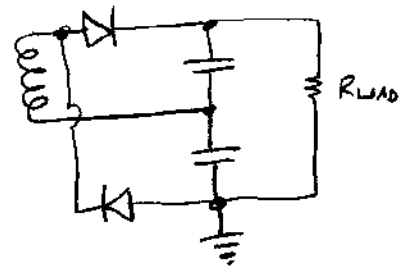

Advantages: Half the voltage across C_2

Disadvantage: The transformer floats.