
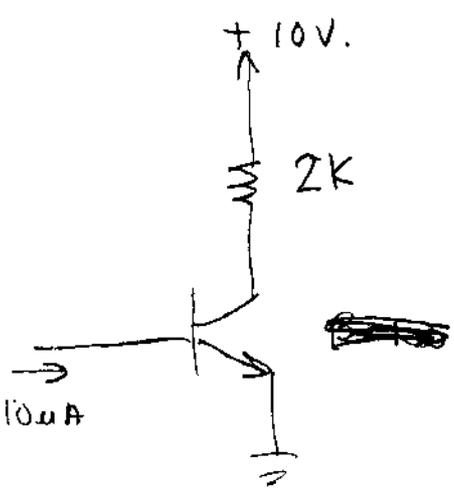


# Load line analysis of transistor circuit

Like a diode

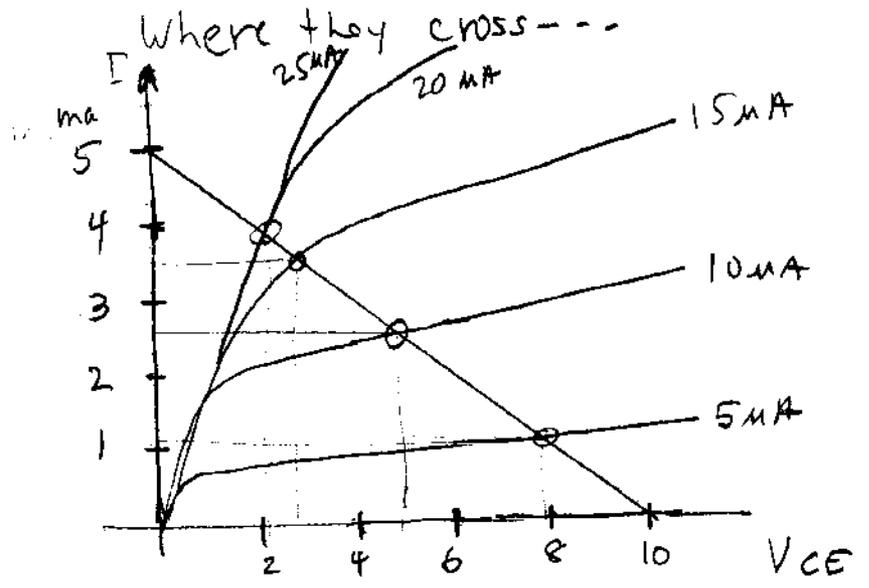

Plot transistor curve and load line on same graph -



Transistor:  $I_C$  vs.  $V_{CE}$

Resistor:  $I$  vs  $V_{CE} \leftarrow V_{CE} + V_R = 10$

So  $V_{CE} = 10 - V_R$

From graph:

$I_B$	$V_{CE}$	$I_C$
10µA	4.9	2.6
5µA	1.1	7.9
15µA	2.8	3.6
20µA	2.1	4.0
25µA	2.1	4.0

saturation.

Resistor:

$V_R$	$I$	$V_{CE}$
0	0	10
10	5ma	0


plot this.

Real saturation voltage  $\approx 0.2$

# Another circuit

# Biassing a transistor amplifier

7C  
2

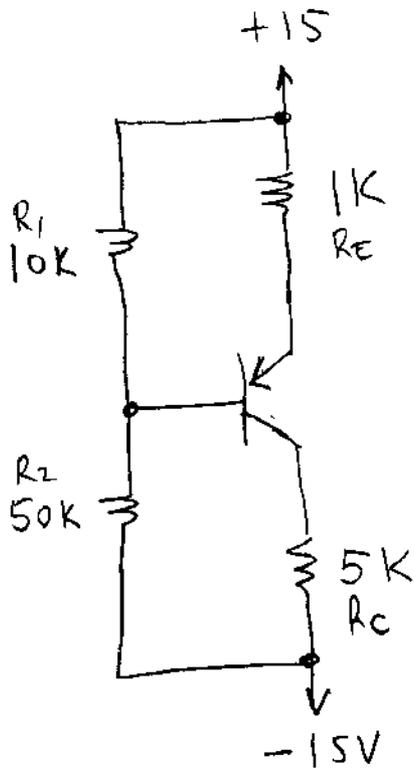

Find operating point.

$\beta = 50$        $V_{BE} = -6$

Make Thevenin equivalent of base circuit.

$$\frac{R_1}{R_1 + R_2} = \frac{V_{R1}}{V_{total}}$$

$$\frac{10K}{60K} = \frac{V_{R1}}{30}$$

$$V_{R1} = \frac{10K}{60K} \times 30 = \frac{30}{6} = 5$$

$$V_{R2} = 25$$


$$V_B = 10$$

$$R = R_1 \parallel R_2 = \frac{(10K)(50K)}{10K + 50K}$$


$$= \frac{500 \text{ Meg}}{60K}$$

$$= \frac{50}{6} K$$


$$= 8.33 K$$

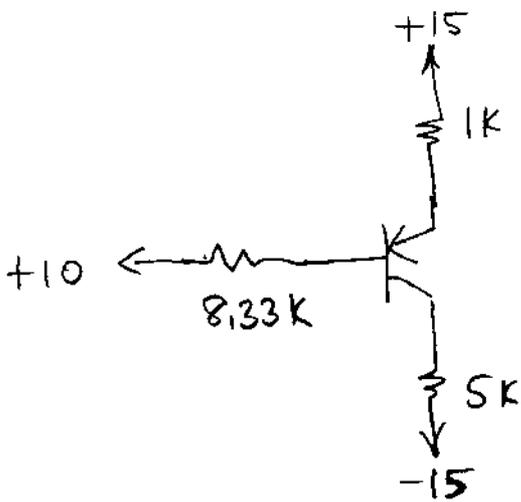

Substitute the model -

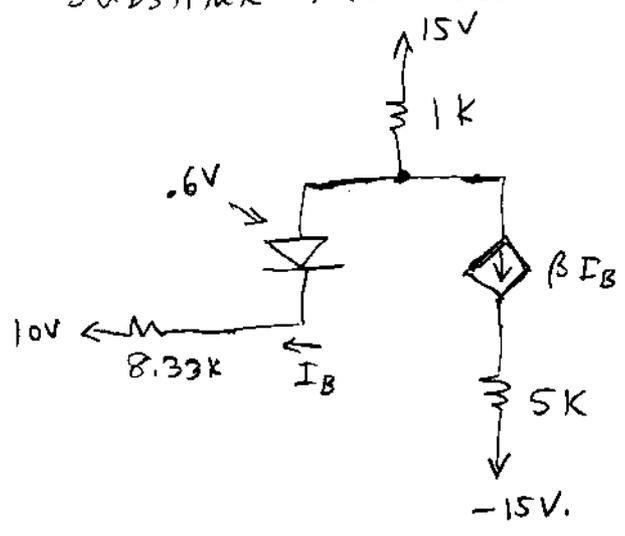

Simplify it

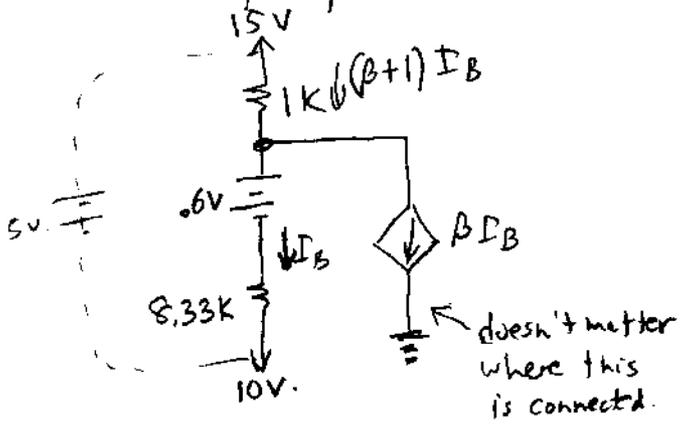

Loop equation.

$$(1k)(\beta+1)(I_B) + .6 + (8.33k)(I_B) = 5$$

$$(51k)(I_B) + .6 + (8.33k) I_B = 5$$

$$(59.33k) I_B = 4.4$$


$$I_B = \frac{4.4}{59.33k} = 7.4 \times 10^{-5} = 74 \mu A$$

$$I_C = \beta I_B = .0037 A$$


$$V_{RC} = I R = (.0037)(5000) = 18.5$$

$$I_E = (\beta+1) I_B = .0038 A$$

$$V_{RE} = (.0038)(1000) = 3.8$$

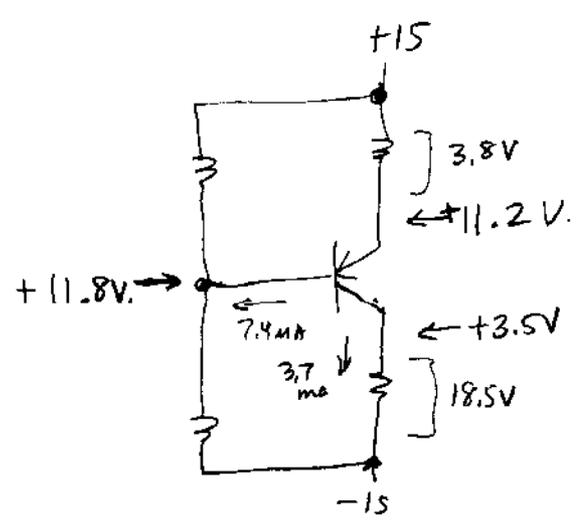

Circuit with Q point.

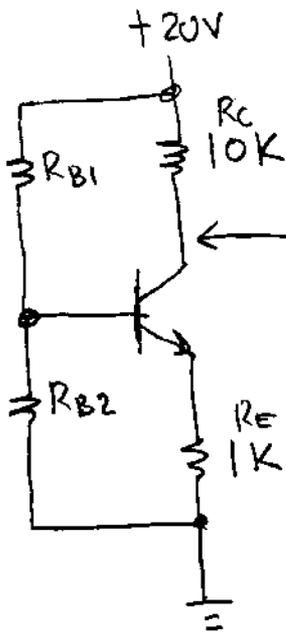

Choose  $R_{B1}$ ,  $R_{B2}$   
to get 10V. here

$$\beta = \infty \quad V_{BE} = .6$$

---


$$I_C = \frac{V_{RC}}{R_C} = 1 \text{ ma}$$

$$I_E \approx 1 \text{ ma}$$

$$V_E = V_{RE} = (1 \text{ ma})(1K) = 1$$

$$V_B = V_E + V_{BE} = 1 + .6 = 1.6$$

Choose  $R_{B1}$ ,  $R_{B2}$  for 1.6V at junction.

How about --  $R_{B1} = 16K$  ( $I = .1 \text{ ma}$ )

$$R_{B2} = \frac{20 - 1.6}{.1 \text{ ma}} = \frac{18.4}{.1 \text{ ma}} = 184K$$

Any resistors in this ratio will work.

The higher the better, but

You need to account for base current.

Same circuit -

$$10V < V_C < 11V.$$

$$\beta > 50 \quad V_{BE} = .6$$

↑  
could be infinite.

Observe -- Base current makes  $V_B$  go down

which makes  $V_E$  go down


and  $V_C$  go up.

Analyze for  $\beta = 50$

$$\left( \alpha = \frac{50}{51} = .98 \right)$$

$$\text{If } I_C = 1\text{ma}, \quad I_B = .02\text{ma}$$

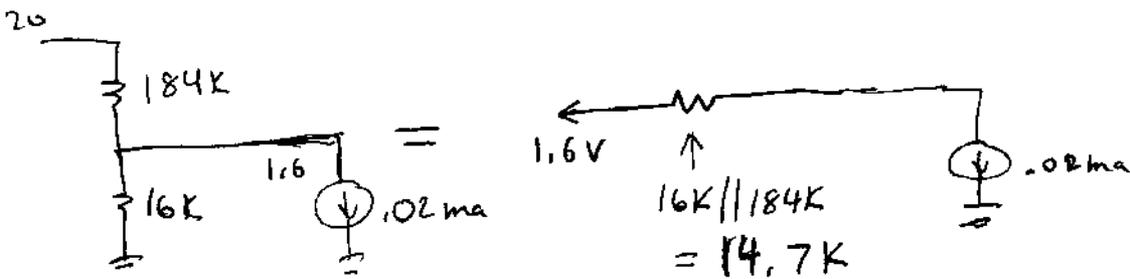Base <sup>resistors</sup> equivalent circuit



$$V = IR \Rightarrow (.02\text{ma})(14.7\text{K}) = .3\text{V}.$$

$$V_{RE} = 1.3 - .6 = .7$$

$$I_E \quad I_{RE} = \frac{V}{R} = \frac{.7}{1\text{K}} = .7\text{ma}$$

$$I_C = \alpha I_E = (.98)(.7\text{ma}) \approx .7\text{ma} \quad \leftarrow \text{close enough}$$

$$V_{RC} = (.7\text{ma})(10\text{K}) = 7\text{volts}.$$

$$V_C = 13\text{V}. \quad \leftarrow \text{out of spec!}$$

# How to figure $R_{B1}$ , $R_{B2}$ correctly



70  
6

$\beta = \infty$       $V_C = 10$ ,  $V_E = 1$

$\beta = 50$       $V_C = 11$ ,  $V_E = 0.9$

Need base voltage: 1.6 with  $\beta = \infty$ ,  $I_B = 0$   
 1.5 with  $\beta = 50$ ,  $I_B = \frac{0.9 \text{ mA}}{50} = 0.018 \text{ mA}$

Base resistors equivalent circuit:

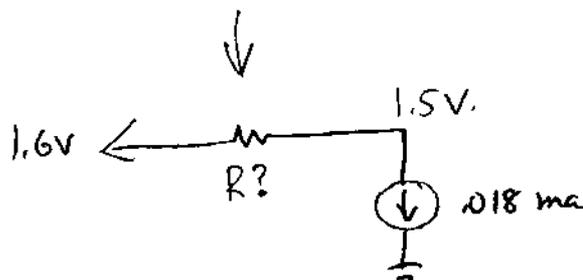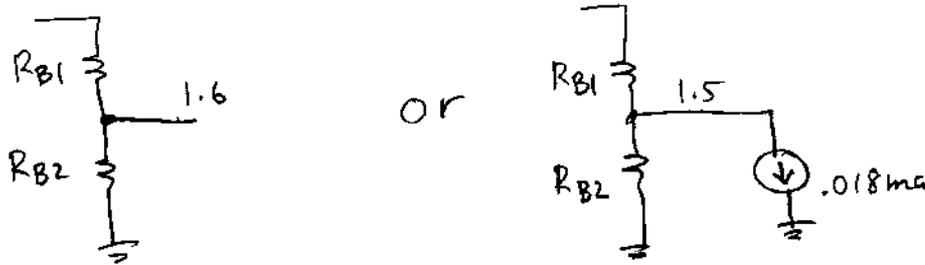

$$R = \frac{V}{I} = \frac{1.6 - 1.5}{0.018 \text{ mA}} = \frac{0.1}{0.018 \text{ mA}} = 5.5556 \text{ K}$$

↑  
Value of  $R_{B1}$ ,  $R_{B2}$   
in parallel

To get 1.6V, open circuit

the ratio must be  $\frac{R_{B2}}{R_{B1}} = \frac{1.6}{18.4} = \frac{V_{R1}}{V_{R2}}$

$$\frac{18.4}{1.6} = 11.5$$

$$R_{B2} = 11.5 R_{B1}$$

$$\text{SO } \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 5.56 \text{ K} = \frac{(R_{B1})(11.5 R_{B1})}{R_{B1} + 11.5 R_{B1}} =$$


$$5.56 \text{ K} = \frac{11.5 R_{B1}^2}{12.5 R_{B1}} = \frac{11.5}{12.5} R_{B1} \rightarrow R_{B1} = (5.56 \text{ K}) \left( \frac{12.5}{11.5} \right) = 6.03 \text{ K} \text{ (6K)}$$

$$R_{B2} = 69 \text{ K}$$

Here's the answer :

Homework: check it.

7C  
7

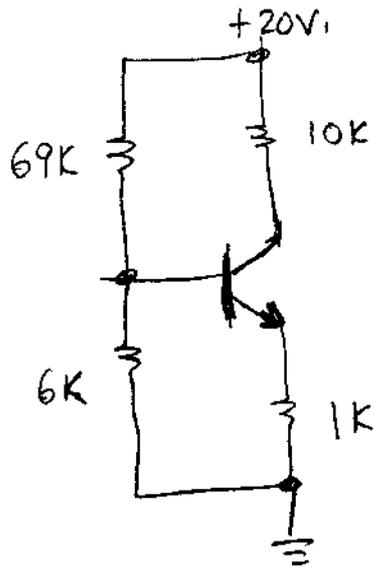

---

HW:	<u>P.</u>	<u>#</u>
	130	14, 15, 16, 17
	154	19, 22, 25, 28