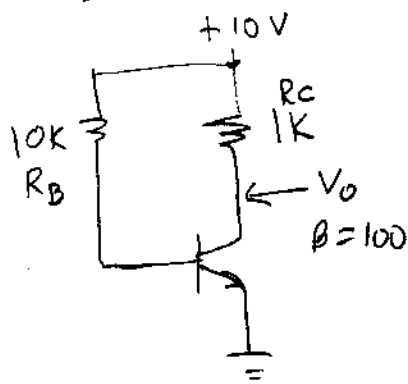


HW	p.	#	p	#
Sec 3.2	125	11, 12, 13	154	19, 22,
	130	14, 15, 16, 17	155	25, 28
Sec 3.3	136	18, 19, 20, 21 (switch) 22 (logic)		

8A
1

Basic Transistor Applications (3.3)

The Switch



What is V_o ?

$$I_B = \frac{V_{RB}}{R_B} = \frac{9.4}{10K} = .94 \text{ ma}$$

If $\beta = 100 \dots$

$$I_C = \beta I_B = 94 \text{ ma} ??$$

No - it is saturated -

can't be more than $\frac{10V}{1K} = 10 \text{ ma}$

We use this as a switch.

Designing a switch -


We need to supply power to a device requiring approx +5 volts at .01 Amps with one side grounded.

This is to be controlled by a logic device, with output level 0 volts for On, 5 volts for off, with maximum current of 1 ma.

The transistors have a minimum β of 50

Solution:

Use a PNP in series:

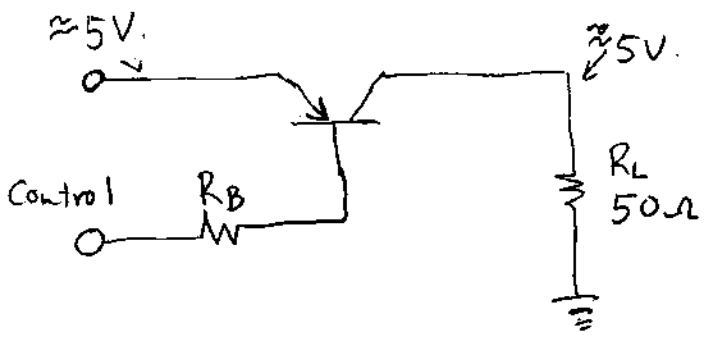

When on the voltage drop across the transistor is .2 volts. Ignore it.

Base current required:

If load current is 100 ma,
You need at least 2 ma to turn it on.

⇒ To guarantee that, make the base current at least twice that.


Make base current 4ma. (as if $\beta = 25$)

$$R_B = \frac{V_{RB}}{I_B} = \frac{5 - .6}{4 \text{ ma}} = \frac{4.4 \text{ V}}{4 \text{ ma}} = 1.1 \text{ K}$$

Multiple switch circuits -

Digital logic -


NOR gate - switches in parallel (NOT-OR)

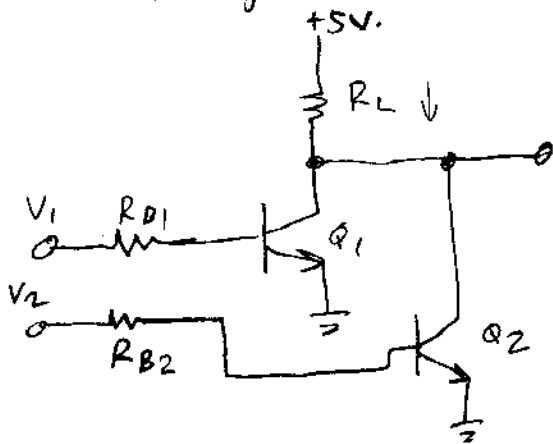

Current flows in R_L if Q_1 or Q_2 is on.


But if we look at the voltage, it is low if Q_1 or Q_2 is on. which is if V_1 or V_2 is high.

NAND gate - just use PNP. (NOT-AND)

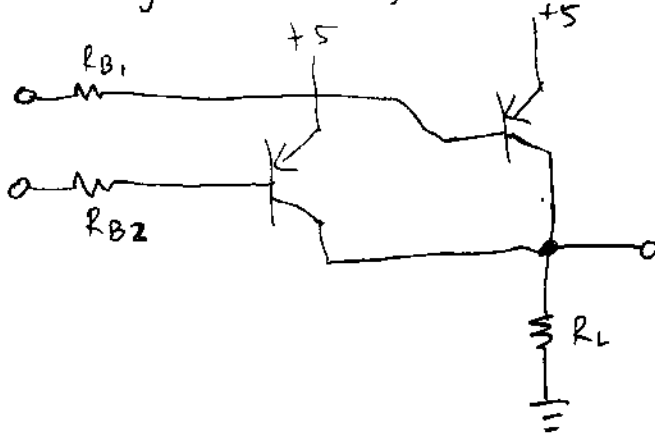


They usually don't do it this way

NAND with NPN - put them in series

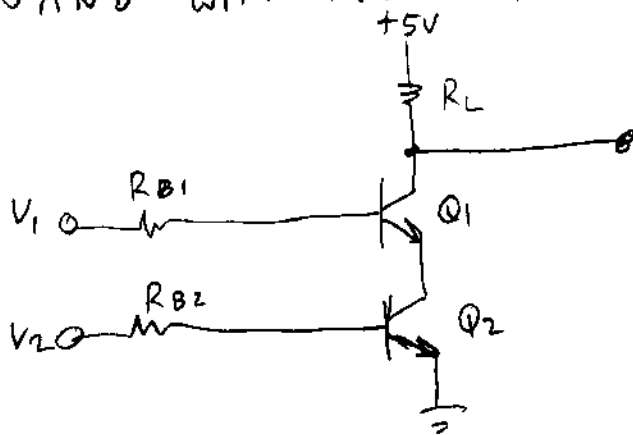

These gates invert the signal.

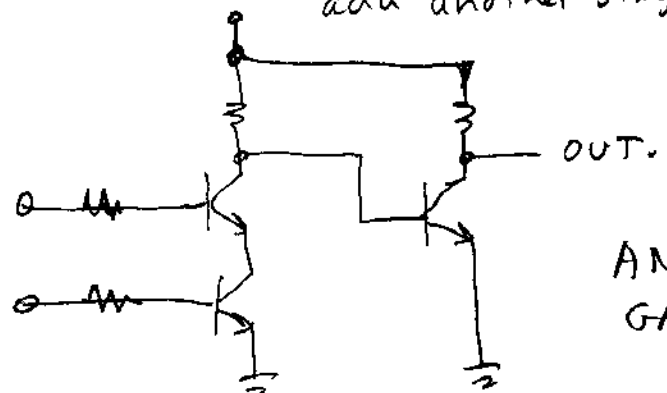If you need non-inverting add another stage




AND GATE

Extra---

Back to the switch (p. 1 & 2)

What if we need the control to be + for on, 0 for off?

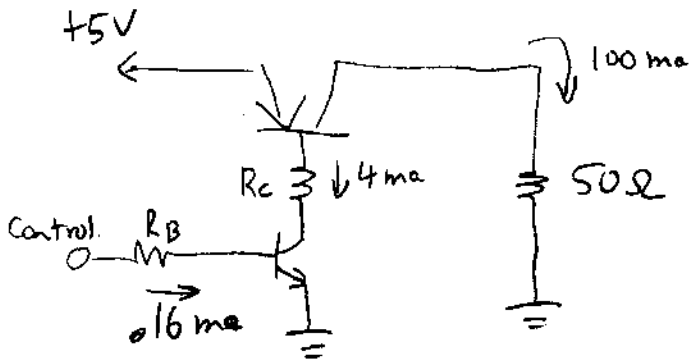Just add an inverter to the control line.



The control current can be lower now -

$$R_C = 1.1 K \text{ (as before)}$$

$$R_B = \frac{4.4 V}{.16 mA} = 27 K$$