

3.4 - Biasing - summary.

9A
1

3.4.1



Very beta dependent


Not used, except as introduction.

3.4.2

Voltage divider biasing.

Add emitter resistor.

Use voltage divider on base

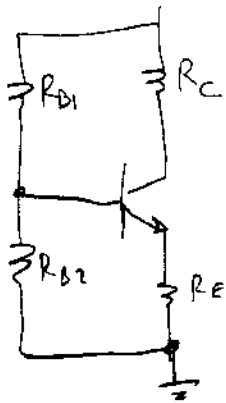

→ R_E reduces DC gain.


→ Some voltage across R_E masks effect of V_{BE} variations.

→ Choose R_{B1} , R_{B2} ratio for proper voltage - open circuit.

→ Then value (scale) for effective series resistance

3.4.3 Current source biasing.


QA
2

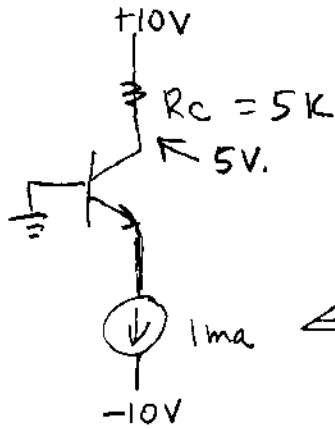

← How to make this ?

Two ways:

Method #1 (not in book)

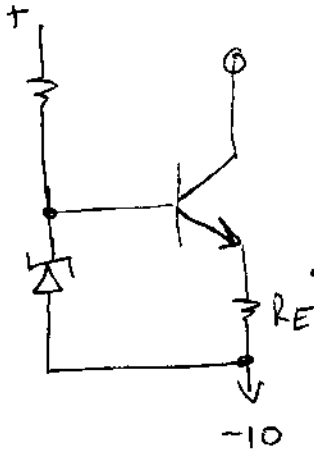

← Set zener and RE for desired current

Example: 5.6V zener makes V_{RE} 5V.

$$R = \frac{V}{I} = \frac{5}{1\text{ma}} = 5\text{K}$$


Hw -

Sec 3.4	P	#	P.	#
3.4.1	140	24, 25	156	31, 34
3.4.2	144-145	26, 27, 28, 29	157	37, 40
3.4.3	147	30, 31	158	43, 46
			159	49, 52

Method # 2 - "Current mirror"

9A
3

Use 2 transistors:

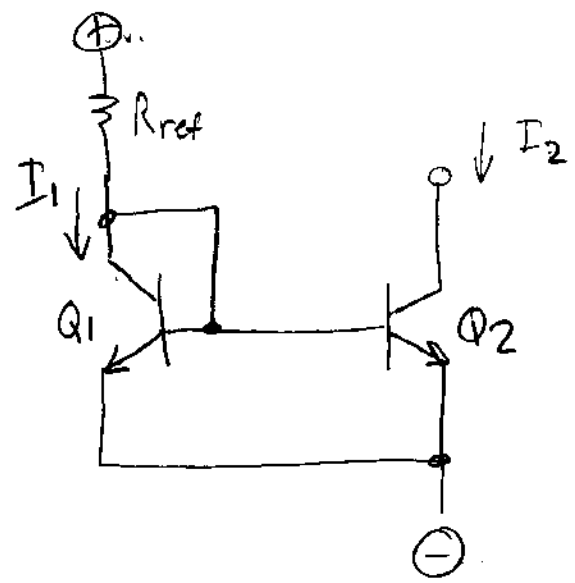

If Q_1 and Q_2 are identical. (exactly!)

$$I_1 \approx I_2$$


(ignoring r_c (Early voltage))

Example For $1\text{ma} \pm 10\text{V}$ supply

$$V_{R_{ref}} = 20 - 0.6 = 19.4$$

$$R_{ref} = \frac{V_{R_{ref}}}{I_1} = \frac{19.4}{1\text{ma}} = 19.4\text{K}$$

More accurately ...

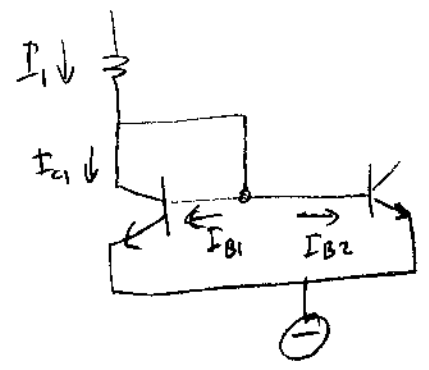

$$I_1 = I_{C1} + I_{B1} + I_{B2}$$

Since Q_1, Q_2 are identical,

$$V_{BE1} = V_{BE2}$$

$$I_{C1} = I_{C2}$$

Substituting --

$$\begin{aligned} I_1 &= I_{C2} + 2I_{B2} \\ &= I_{C2} + 2 \frac{I_{C2}}{\beta} \end{aligned}$$

$$I_1 = I_{C2} \left(1 + \frac{2}{\beta} \right)$$

$$I_{C2} = \frac{I_1}{\left(1 + \frac{2}{\beta} \right)}$$

For $\beta = 100$ --

$$\begin{aligned} 1 + \frac{2}{\beta} &= \\ &= 1 + \frac{2}{100} \\ &= 1.02 \end{aligned}$$