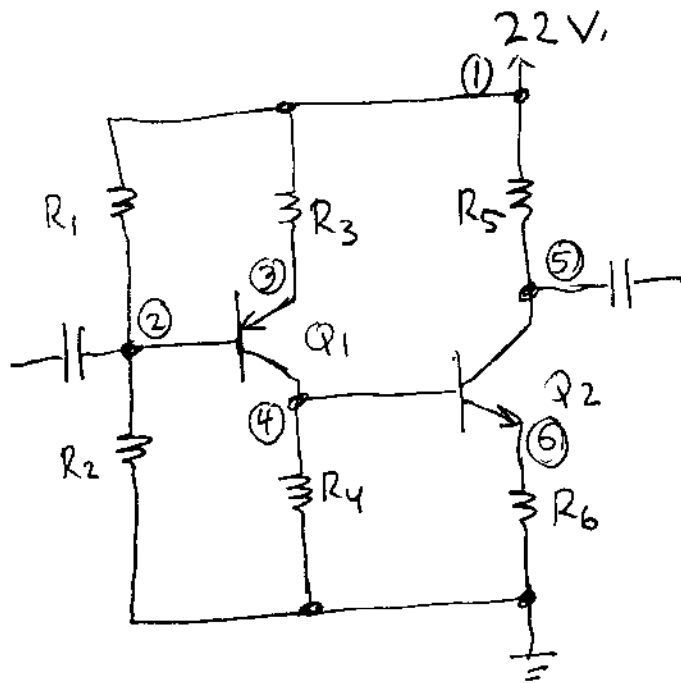


Biasing - (finish it).

10A
1

Multi-stage amplifier design example



Specs:

$$\text{Gain} = 100$$

(10 each stage)

$$R_{out} = 10K$$

Choose resistors
to maximize output
capability.

$$\beta = 100 \quad V_{BE} = .6$$

Procedure:

Choose $R_5 = 10K$ (for R_{out})

then $R_6 = 1K$ (for gain in 2nd stage)

For maximum output capability -

want half of the voltage across the transistor

$$\Rightarrow V_{CE_{Q2}} = 11$$


(this works if there
is no external load -
more next week).

This means the other 11V is in the resistors.

Assume $I_C \approx I_E$ -- then $V_{R5} = 10V$, $I_C = 1ma$

$$V_{R6} = 1V$$

$$I_B = \frac{I_C}{\beta} = .01 ma$$

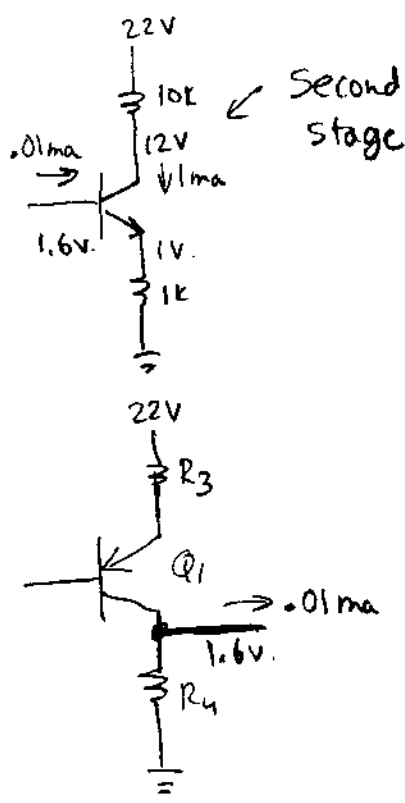

Now, design the first stage.

It must have 1.6V on the collector with 0.1mA to the base of the second stage.

Choose current = 10 x base current of next stage = 0.1mA

$$\Rightarrow R_4 = 16K$$

$$I_{R_4} = 0.1mA$$

$$I_{CQ1} = 0.11mA$$

$$I_E \approx 0.11mA$$

For gain of 10, $R_3 = 1.6K$

$$V_{R_3} = I R = (0.11mA)(1.6K) = 0.17V$$

$$\text{So... } V_3 = 22 - 0.17 = 21.83$$

$$V_2 = 21.83 - 0.6 = 21.23$$

$$I_B = 0.001mA$$

This is a bad design.

The voltage across R3 is too small.

Small variations are amplified.

It will be difficult to get a consistent operating point.


10A
3

Idea: Split R_3 into 2 parts.

Put a big capacitor across one of them.

The unbypassed one determines the gain.

+22V. The total determines the DC bias.

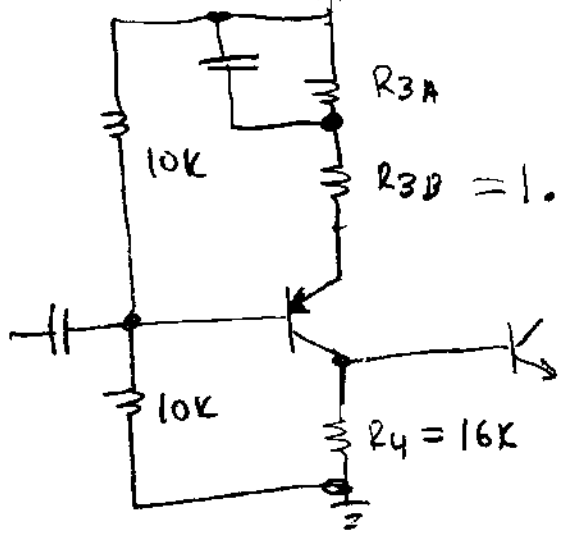

Since not much voltage swing is needed, make R_{3A} fairly large.

Choose to get a good DC voltage.

How about --- make V_B $\frac{1}{2}$ supply = 11V,

Then $R_1 = R_2$

Arbitrarily choose 10k

Then $V_E = 11 + 0.6 = 11.6$

$V_{jct} = 11.6 + 0.2 = 11.8$

$V_{R_{3A}} = 22 - 11.8 = 10.2$


$R = \frac{V}{I} = \frac{10.2}{0.11 \text{ ma}} = 92 \text{ k}$

use 91k

(how much will this change the result?)

Here's the circuit:


10A
4

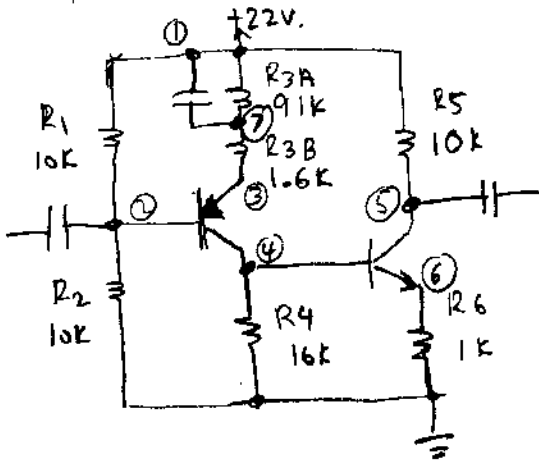

Verify it. (in to out)

$$V_2 \text{ ignoring load: } \left(\frac{40k}{20k} \right) (22v) = 11V.$$

$$R_{eq} = 10k \parallel 10k = 5k$$

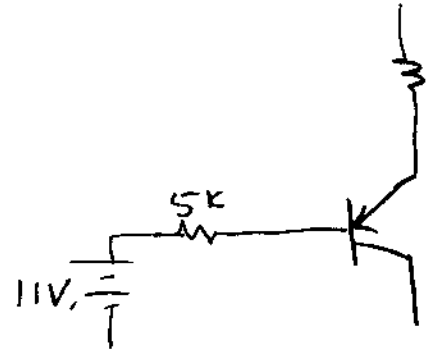

If $V_2 = 11V$, then V_3 must be 11.6V.


$$V_{R3} = 22 - 11.6 = 10.4$$

$$R_3 = R_{3A} + R_{3B} = 92.6k$$

$$I_{R3} = \frac{V}{R} = \frac{10.4}{92.6k} = .112 \text{ ma}$$

If $\beta = 100$, $I_B = .00112 \text{ ma} = 1.12 \mu A$

Correct base voltage --

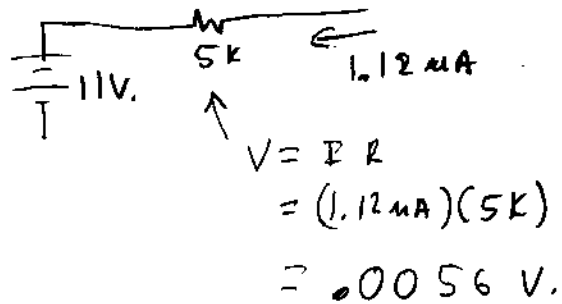


Ignore it.

We could have made R_1, R_2 higher.

Should have.

$$I_{R4} = I_{R3} - I_B = 0.112 \text{ ma} - 0.001 \text{ ma} = 0.111 \text{ ma}$$
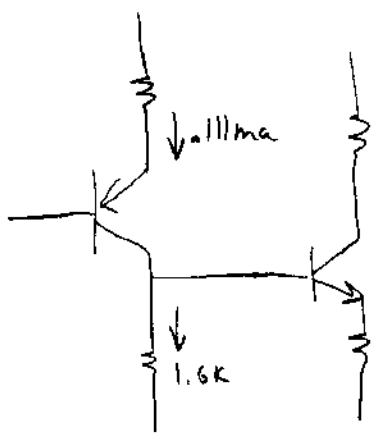
$$V_{R4} = IR = (0.111 \text{ ma})(16 \text{ k}) = 1.78 \text{ (assuming next stage base current = 0)}$$




$$Q2 \quad V_{BE} = 0.6 \text{ (assume)}$$

$$\text{SO } V_{Q2E} = 1.78 - 0.6 = 1.18$$

$$I = 1.018 \text{ ma}$$

$$\text{If } \beta = 100, I_B = 0.0118 \text{ ma} \approx 0.012$$

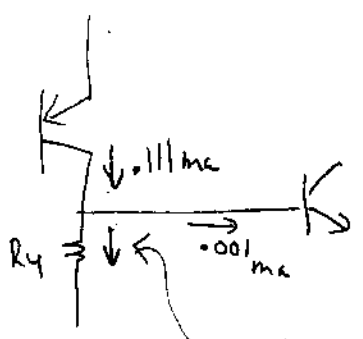Go back to V_{R4} - Calculate again with this assumed base current



$$0.111 - 0.012 = 0.099 \text{ ma} \quad V_{R4} = IR = (0.099)(16 \text{ k}) = 1.58 \text{ V. } \approx 1.6$$

(confirms 1.6 design value)

$$V_{EQ2} = 1.6 - 0.6 = 1.0 \quad I_E = 1 \text{ ma}$$

$$\text{since } I_C = 1 \text{ ma}, V_{R5} = 10, \text{ so } V_5 = 22 - 10 = 12$$

Design:

Start at the output.

Choose voltages, currents and work back toward the input.

Analysis:

Start at the input.

Use thevenin, Norton equivalent circuits

If you don't know something,
like base current,

Assume a value that seems good.

Calculate the voltage you are looking for.

Then calculate the real value for
what you assumed.

Re-calculate the voltage you are looking for.

Usually, this is close enough.

HW:	sec 3.5	$\frac{P}{150}$	$\frac{I}{3.32, 3.33}$	} Not to hand in
		160	3.55	

p. 161 D 3.67 To hand in
Design
Verify with simulation
Due next Monday