

Ch.4 Transistor amplifiers

TOP
1

4.2 Basics.


Small signal analysis..

To analyze the signal properties of an amplifier-

Make a "small signal model"


approximating the behavior at the operating point.

Recall -- transfer characteristic is:

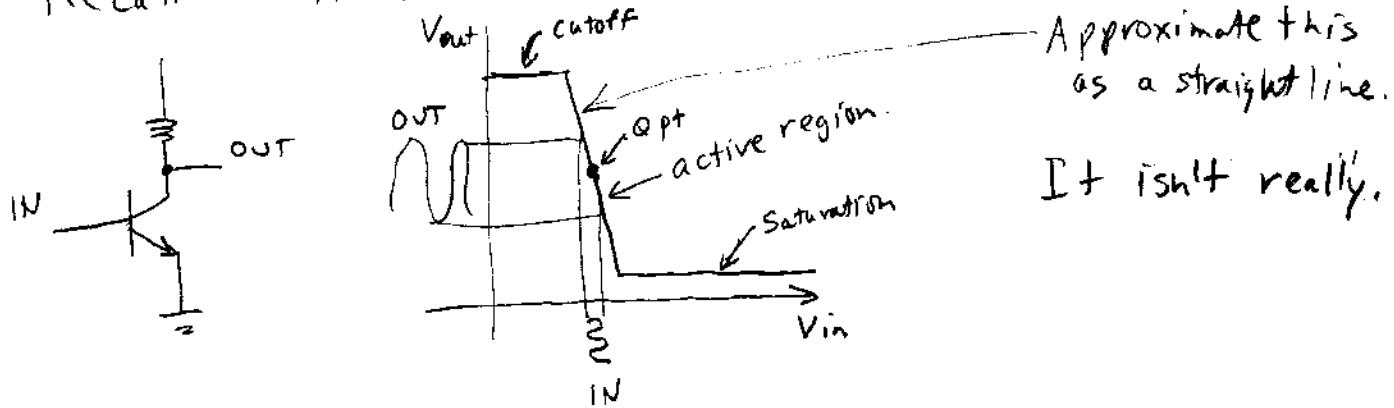



Large signal models:

Active region

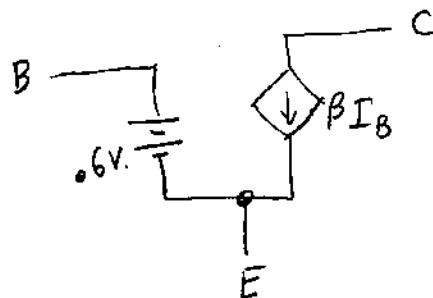



Saturation region

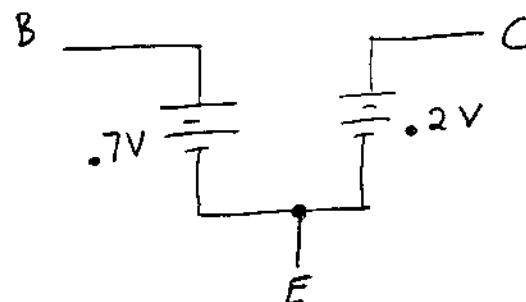

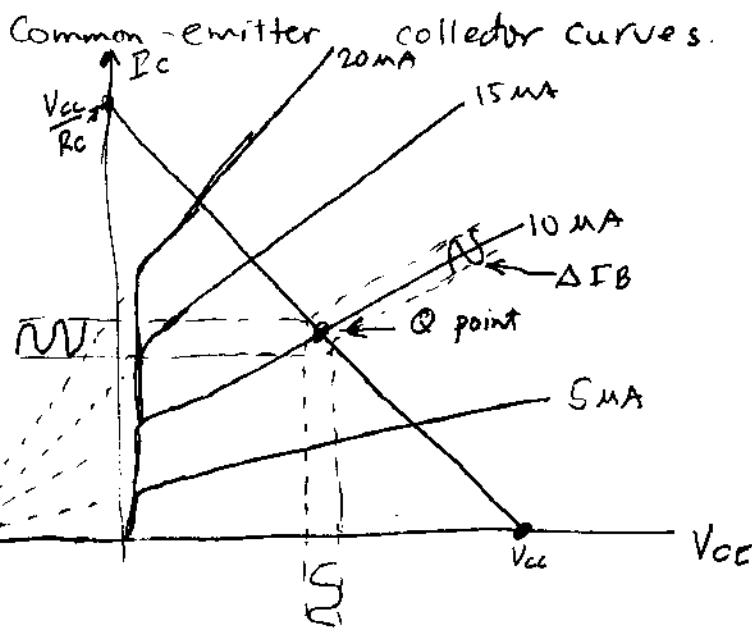

Move the base current a little —
 Collector current changes (Y axis)
 Reflect on load line to see that voltage changes
 Treat it as linear.

Large signal model :

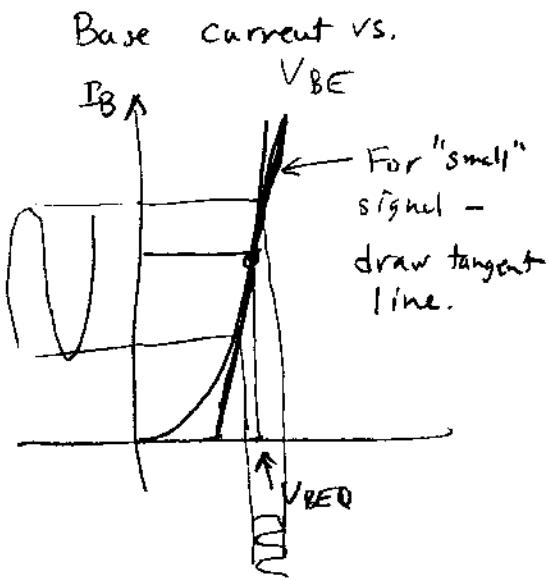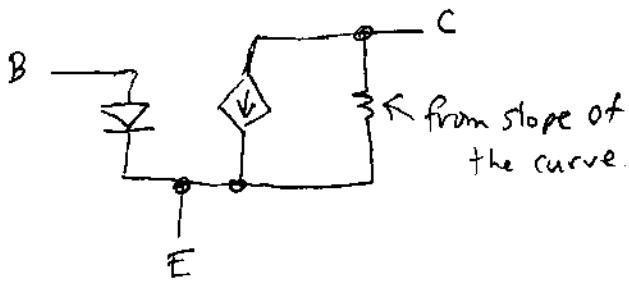

p. 168 shows equations — Read it.

The essence is --

$$i_B = \frac{I_s}{1 + \beta_F} e^{\frac{V_{BE}}{V_T}}$$

For AC, we care only about $\frac{\Delta i_B}{\Delta V_{BE}}$

or $\frac{di_B}{dV_{BE}}$ = derivative of curve.

Substitute the admittance —
 make believe it is linear.

Notation:

Capital letters = LARGE signal
or DC


small letters = small signal or AC

so --- I_B is DC base current


i_b is AC signal current

etc.

New model

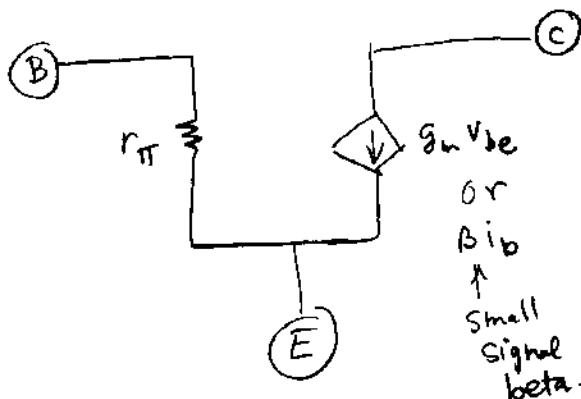


The old circuit,
new labels

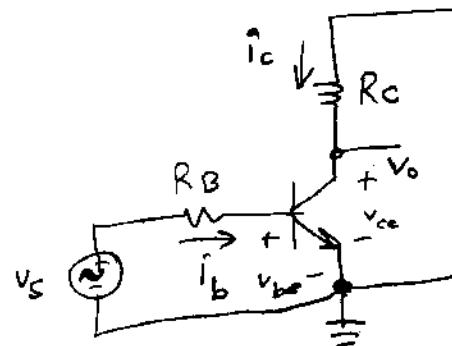

For AC
small signal,
power supply
is just like ground.

Finding the values :

$$\frac{1}{r_{\pi}} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q_{pt}}$$

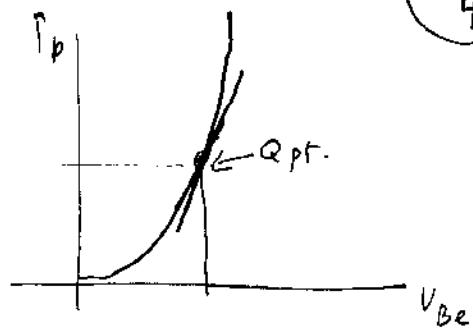

10B
4

recall:

$$I_B = \frac{I_s}{1+\beta} e^{\frac{V_{BE}}{V_T}}$$

$\frac{1}{r_{\pi}}$ at Q pt

This could also be stated as

so:

$$\frac{1}{r_{\pi}} = \left. \frac{\partial}{\partial V_{BE}} \frac{I_s}{1+\beta} e^{\frac{V_{BE}}{V_T}} \right|_{Q_{pt}}$$

$$I_{s_{BE}} e^{\frac{V_{BE}}{V_T}}$$

Saturation current of
Base emitter diode.

Be careful which I_s
you use!!!

Note how they are related.
Ask which one you have if
you are not sure.

$$= \frac{1}{V_T} \left[\frac{I_s}{1+\beta} e^{\frac{V_{BE}}{V_T}} \right] \Big|_{Q_{pt}}$$

$$\text{but since } I_{BQ} = \frac{I_s}{1+\beta} e^{\frac{V_{BE}}{V_T}}$$

$$\frac{1}{r_{\pi}} = \frac{I_{BQ}}{V_T}$$

$$\text{so } r_{\pi} = \frac{V_T}{I_{BQ}} \approx \frac{0.026}{I_{BQ}}$$

r_{π} is "diffusion resistance"

it is the incremental resistance of the BE diode

For small signal, we just say: $\frac{1}{r_{\pi}} = \frac{i_b}{v_{be}}$ small signal
AC values

Transconductance:

$$g_m = \frac{\partial i_c}{\partial V_{BE}}$$

(by definition)

Small signal notation -

$$g_m = \frac{i_c}{v_{be}}$$

Relation to β ---

$$g_m = \frac{\partial i_c}{\partial V_{BE}}, \quad \beta = \frac{\partial i_c}{\partial i_B}, \quad r_{\pi} = \frac{\partial i_B}{\partial V_{BE}}$$

so ---

$$\frac{\partial i_c}{\partial V_{BE}} = \frac{\partial i_c}{\partial i_B} \cdot \frac{\partial i_B}{\partial V_{BE}}$$

$$g_m = \frac{\beta}{r_{\pi}} \quad \text{or} \quad \beta = g_m r_{\pi}$$

It might be specified either way -

You need to convert.

note ---

$$\beta_F = \frac{I_C}{I_B}$$

for small signal -

$$\beta = \frac{\partial I_c}{\partial I_B} \quad \text{or} \quad \frac{i_c}{i_b}$$

Notation: $\beta_F = \text{DC beta}$
 $\beta = \text{AC beta}$

10B
5

More Conversions --

6

For DC --- $\beta = \frac{I_C}{I_B}$, $g_m = \frac{\beta_F}{r_\pi}$, $r_\pi = \frac{V_T}{I_B}$


$$\text{Substituting} \quad \therefore g_m = \frac{\frac{P_C}{I_B}}{\frac{V_T}{I_B}} = \frac{P_C}{V_T}$$

This notation can be confusing —


DC Parameters vs. ac Parameters
↑
large. ↑
small

Alternate model:

We have this model:

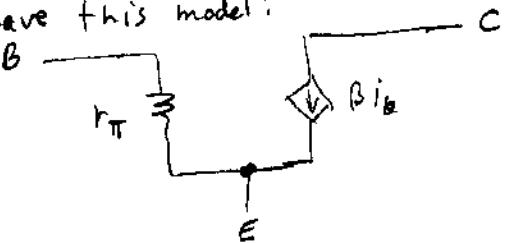


We can reflect r_{II} through a node!

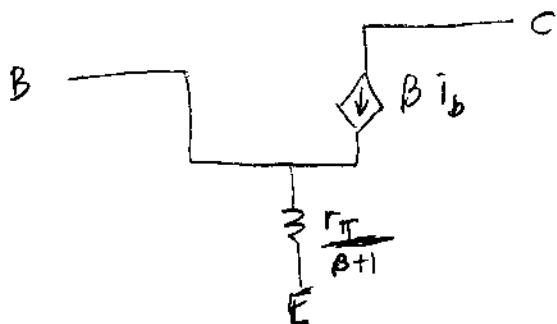

← This circuit is equivalent, and sometimes easier to use.

Example:

10B
7

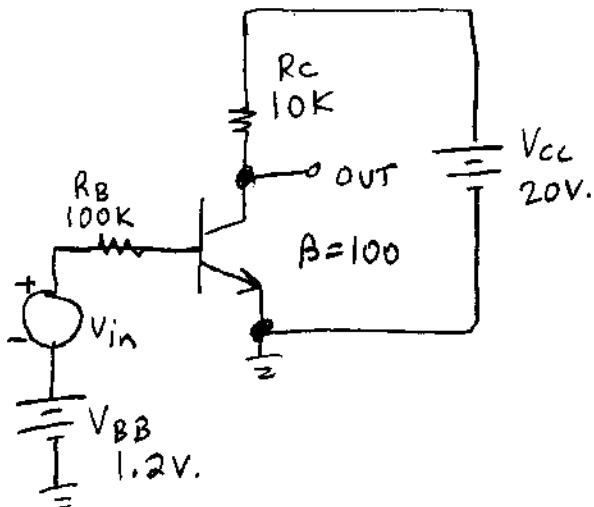

What is small signal voltage gain?

First: Compute the DC operating point

$$I_{BQ} = \frac{1.2 - 0.6}{100\text{ k}} = \frac{0.6}{100\text{ k}} = 6\text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 600\text{ mA}$$

$$V_{RC} = (600\text{ mA})(10\text{ k}) = 6\text{ V.}$$

$$V_{CE} = 20 - 6 = 14\text{ V.}$$

It is in the active region.

AC solution:

$$r_{\pi} = \frac{0.026}{I_{BQ}} = \frac{0.026}{6\text{ mA}} = 4333\text{ }\Omega$$

$$\frac{i_c}{V_{be}} = g_m = \frac{I_{CQ}}{V_T} = \frac{600\text{ mA}}{0.026} = 0.23$$

By ohms law.....

$$g_m R_C = (0.23)(10\text{ k}) = 230.7$$

↑
if $g_m = \frac{i_c}{V_{be}}$ and $V_o = i_c R_C$

$$\text{then } V_o = g_m V_{be} R_C \text{ so } \frac{V_o}{V_{be}} = g_m R_C$$

But we really need to consider the loss in R_B ---


$$\frac{V_{be}}{V_{in}} = \frac{4333}{10433} = 0.04$$

so, real gain is:

$$\left(\frac{V_o}{V_{be}}\right)\left(\frac{V_{be}}{V_{in}}\right) = (0.04)(230) \\ = 9.58$$

Using the alternate model?

10B
8

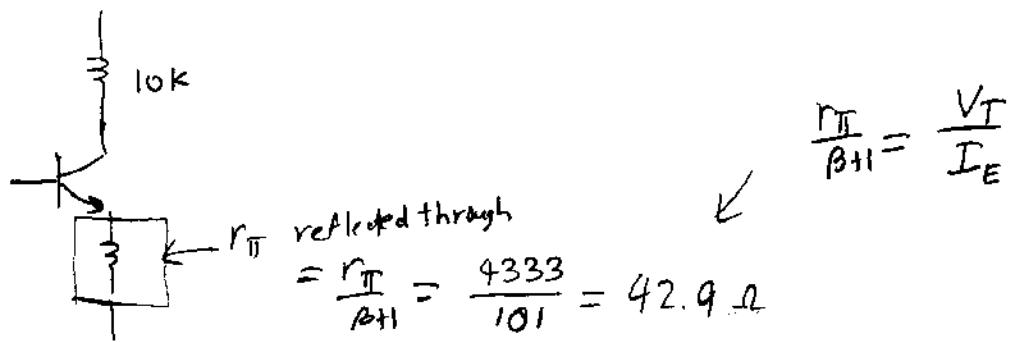

$$\text{Gain} = \frac{10k}{42.9} = 233.1$$

Very close to 230.7 the other way