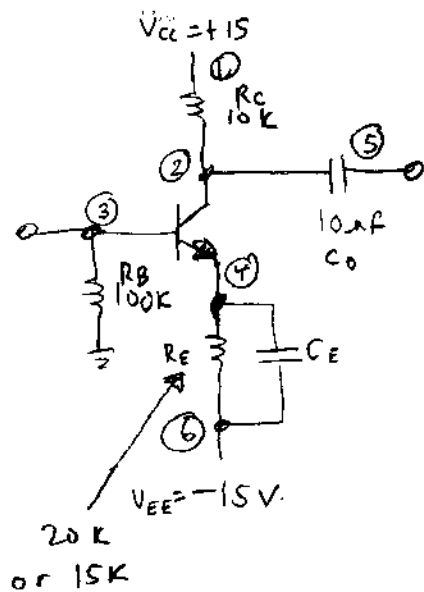


EE 329 Transistor Lab 2

Build this amplifier.



Spice model parameters:

$$I_S = 15f$$

$$\beta_f = 50 \text{ or } 200$$

$$V_A F = 100$$

$$C_{JE} = 25p$$

$$C_{JC} = 10p$$

Pre-lab.

Calculate the capacitors for 50 Hz low frequency corner. (use 100µF)

Hand calculate gain.

Simulate it -

Verify:

operating point

AC Gain at 1kHz.

Input + output impedance.

Frequency response

Transient -

max output before clipping.

Harmonic distortion, 1kHz.

1 Vp-p out.

just below clipping.

Do above for $\beta = 50, 200$
(spice parameter BF)

In lab:

Measure what you simulated,
but with the real transistor.

Report:

How does it compare?

Explain differences.