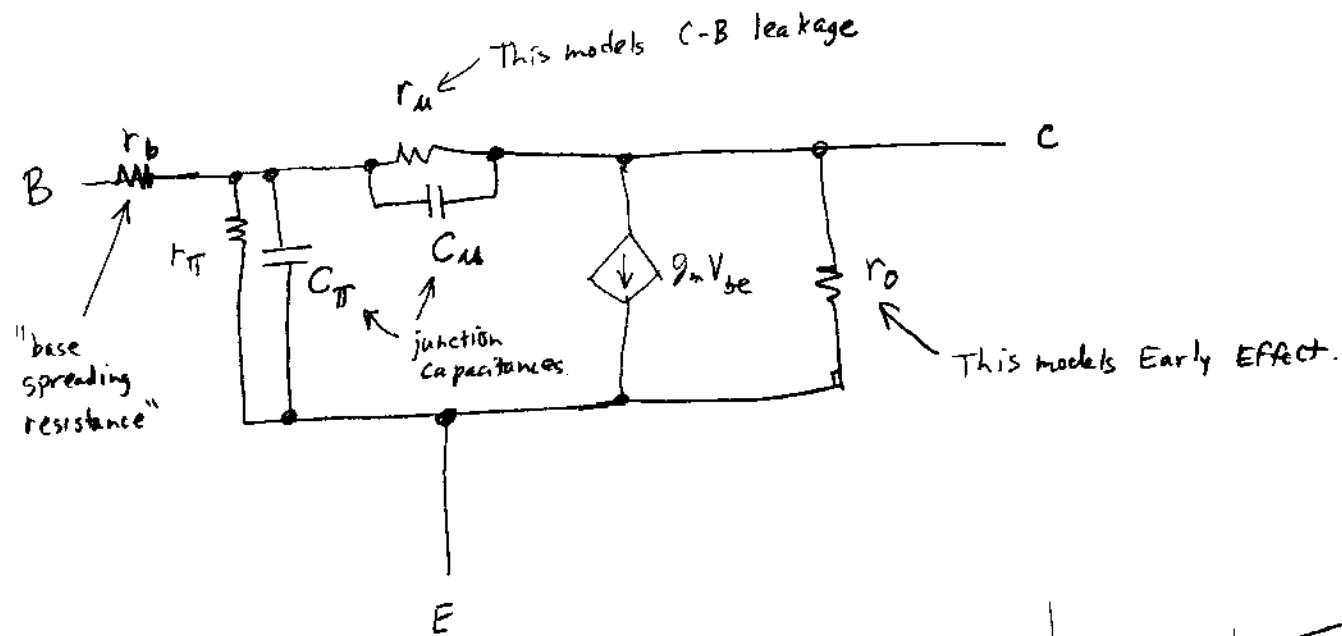


A better small-signal model --

The "hybrid-pi" model --

Add some more complexity to our model -- -



r_o = resistance due to Early effect

Important — it lowers gain

Calculate from curves --

$$r_o = \frac{\Delta V}{\Delta I} \text{ on collector curve}$$

or from V_A --


$$r_o = \frac{V_{CEQ} + V_A}{I_{CEQ}}$$

Example:

$$V_{CEQ} = 10V, V_A = 90V.$$

$$I_{CEQ} = 1mA$$

$$r_o = \frac{100V}{1mA} = 100K$$

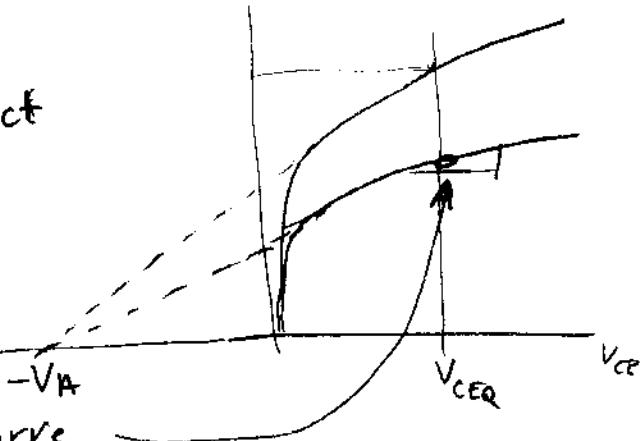

C_{π} = base-emitter capacitance
Spice parameter C_{je}

C_m = base-collector capacitance
Spice parameter C_{jc}

r_u = "reverse-biased diffusion resistance"
similar to r_{π} but for C-B junction
since it is reverse biased, it is very high.

r_b = "base spreading resistance"
usually $\approx 10 \Omega$
usually you can ignore it
(compare to $r_{\pi} \approx 2600 \Omega$)


"H" Parameters - generic 2-port parameters.

(TA
3)

We can express any "2-port" using standardized parameters.

Simplest first --- "Y" parameters
(admittance)

All are in the form of current / voltage

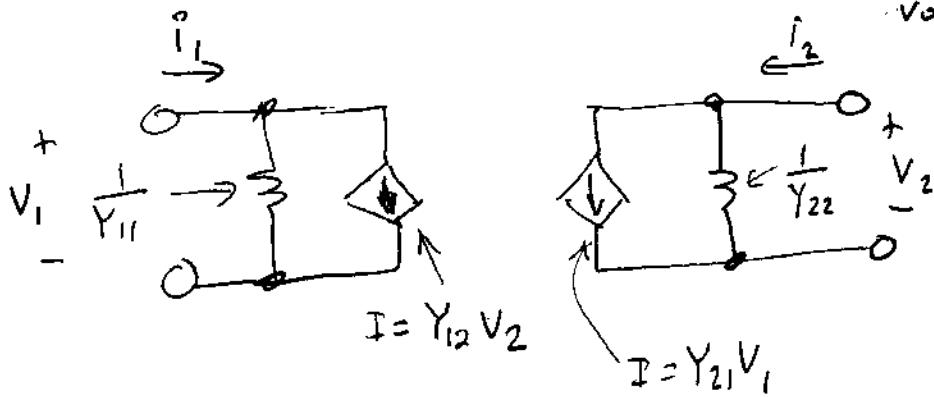

Large signal

$$Y_{11} = \frac{I_1}{V_1}$$

$$Y_{12} = \frac{I_1}{V_2}$$

$$Y_{21} = \frac{I_2}{V_1}$$

$$Y_{22} = \frac{I_2}{V_2}$$

Small signal

$$y_{11} = \frac{i_1}{v_1}$$



$$y_{12} = \frac{i_1}{v_2}$$

$$y_{21} = \frac{i_2}{v_1}$$

$$y_{22} = \frac{i_2}{v_2}$$

There are others ...

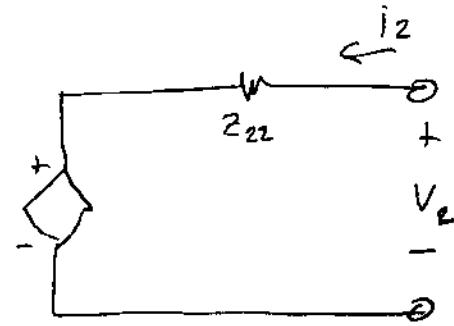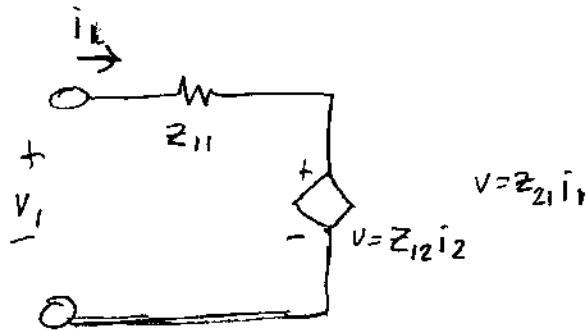Z parameters = impedance = $\frac{V_{11} \text{ Hz}}{\text{amps}}$.



By Thevenin/Norton equivalent circuits —

You can translate between Y and Z parameters —

$$y_{11} = \frac{i_1}{V_1}, \quad z_{11} = \frac{V_1}{i_1} \quad \text{so} \quad y_{11} = \frac{1}{z_{11}} \quad z_{11} = \frac{1}{y_{11}}$$

$$y_{22} = \frac{i_2}{V_2}, \quad z_{22} = \frac{V_2}{i_2} \quad \text{so} \quad y_{22} = \frac{1}{z_{22}} \quad z_{22} = \frac{1}{y_{22}}$$

$$y_{21} = \frac{i_2}{V_1}, \quad z_{21} = \frac{V_2}{i_1} \quad \text{Let } V_1 = \frac{i_1}{y_{11}} \Rightarrow i_2 = y_{22} V_2$$

Substitute

$$y_{21} = \frac{y_{22} V_2}{i_1} = y_{22} y_{11} \frac{V_2}{i_1}$$

$$\frac{y_{21}}{y_{22} y_{11}} = \frac{V_2}{i_1} \quad \dots \quad z_{21} = \frac{y_{21}}{y_{22} y_{11}}$$



$$\text{Let } V_2 = z_{22} i_2, \quad i_1 = \frac{V_1}{z_{11}}$$

$$z_{21} = \frac{z_{22} i_2}{\frac{V_1}{z_{11}}} = z_{11} z_{22} \frac{i_2}{V_1} = z_{11} z_{22} y_{21}$$

$$y_{21} = \frac{z_{21}}{z_{11} z_{22}}$$

H means Hybrid.

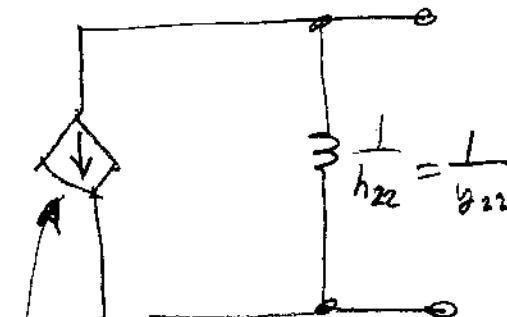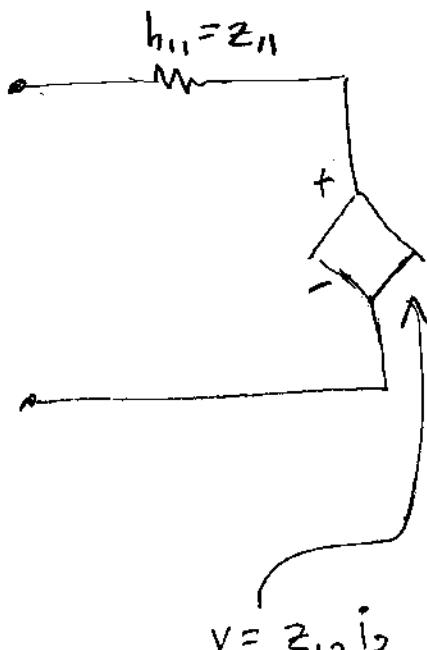Make it like Z parameters on input, Y on output.



$$v = Z_{12} i_2$$

$$i = h_{21} i_1$$

$$v = h_{12} v_2$$

For transistors, port 1 is B-E
 port 2 is C-E
 ↑
 Common emitter.


We have another set of names.

$h_{ie} = h_{11}$ - ie means "input, common emitter"

$h_{re} = h_{12}$ re -- "reverse, common emitter"

$h_{fe} = h_{21}$ fe -- "forward, common emitter"

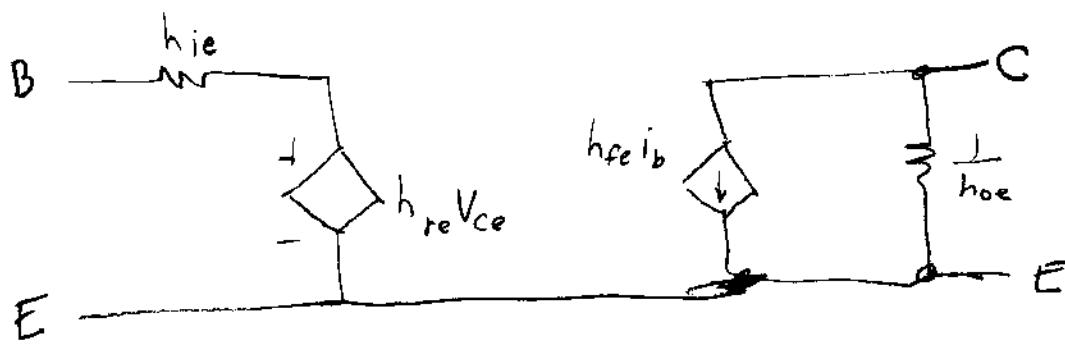$h_{oe} = h_{22}$ oe -- "output, common emitter"



So, if we ignore the capacitances and r_u ...

$$h_{ie} = r_\pi$$

$$h_{fe} = \beta$$

$$h_{oe} = \frac{1}{r_o}$$

$$h_{re} = \frac{r_\pi}{r_\pi + r_u}$$

The book uses
UPPER case letters
when it should use lower
here.

These are smallsignal
parameters.

See graphs - p. 183 of text.

Hw -	P	#
177-178	1,2	
179	3,4	
230	1,4	

Example: $\beta = 100$, $V_A = 90$, $I_{CQ} = 1 \text{ mA}$, $V_{BE} = 10$

$$g_m = \frac{\partial i_c}{\partial v_{be}} = \frac{I_{CQ}}{V_T} = \frac{1 \text{ mA}}{0.026} = 0.038 \frac{\text{A}}{\text{V}} \quad (38 \frac{\text{mA}}{\text{V}})$$


$$r_{\pi} = \frac{\partial v_{be}}{\partial i_b} = \frac{0.026}{I_B} = \frac{0.026}{0.01 \text{ mA}} = 2.6 \text{ k} = 2600 \Omega$$

$$r_o = \frac{\partial v_{ce}}{\partial i_c} = \frac{V_A + V_{CE}}{I_{CQ}} = \frac{90 + 10}{1 \text{ mA}} = \frac{100}{1 \text{ mA}} = 100 \text{ k}$$

$$h_{ie} = r_{\pi} = 2600 \Omega \quad h_{fe} = 100 \quad (= \beta)$$


$$h_{re} = 0 \quad (\text{no info given}) \quad h_{oe} = \frac{1}{100 \text{ k}} = 10^{-5}$$

Gain:

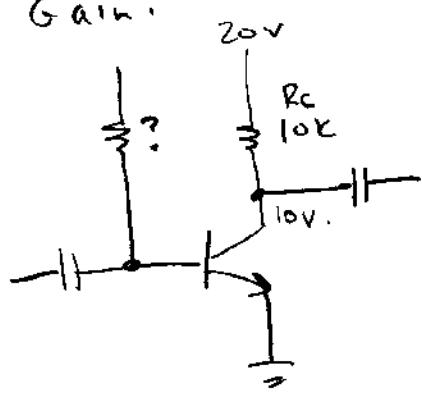

(Transistor as above)

Equivalent circuit:

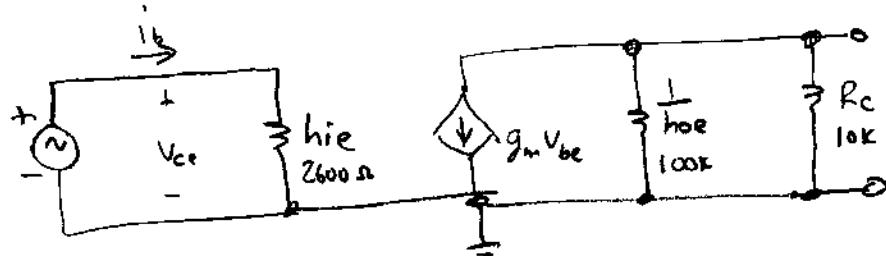

$$\text{Gain} = g_m R_L \quad \text{where } R_L = \frac{1}{h_{oe}} \parallel R_C$$

$$= 9 \text{ K}$$

$$\text{Gain} = (0.038)(9000) = 342$$

(would be 380 if we ignored r_o)