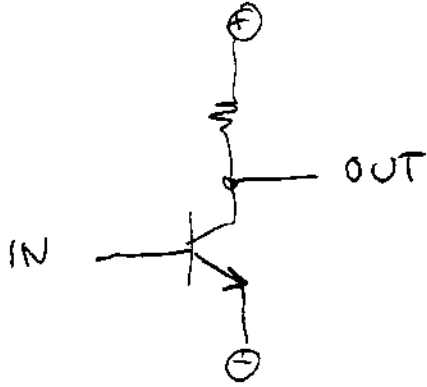


Basic Amplifier Configurations (4.3)

12C
1

Common emitter (4.4, 4.5)




$$A_v > 1$$

$$A_i > 1$$

R_{in} moderate

R_{out} moderate to high

Common collector (4.6)

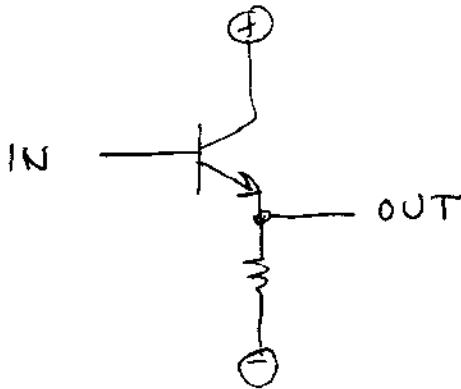


$$A_v \approx 1 \quad (< 1)$$

$$A_i > 1$$

R_{in} high

R_{out} Low

Common base

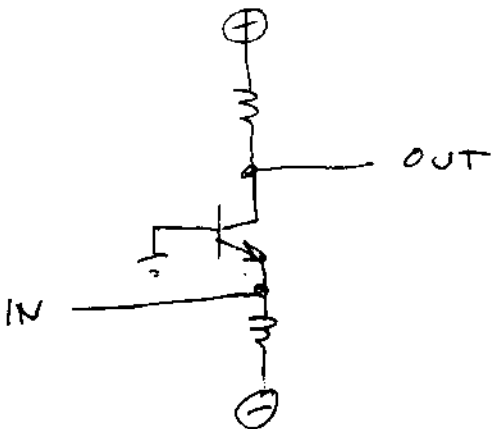

$$A_v > 1$$

$$A_i \approx 1 \quad (< 1)$$

R_{in} Low


R_{out} moderate to high

HW:	<u>P</u>	<u>#</u>	<u>P</u>	<u>#</u>
	177-178	1, 2	230	1, 4
	179	3, 4		
	195	5, 6, 7	231	7, 10
	198	8, 9, 10, 11	232 233	13, 16, 19

AC Load Line Analysis (4.5)

12C
2

Problem:

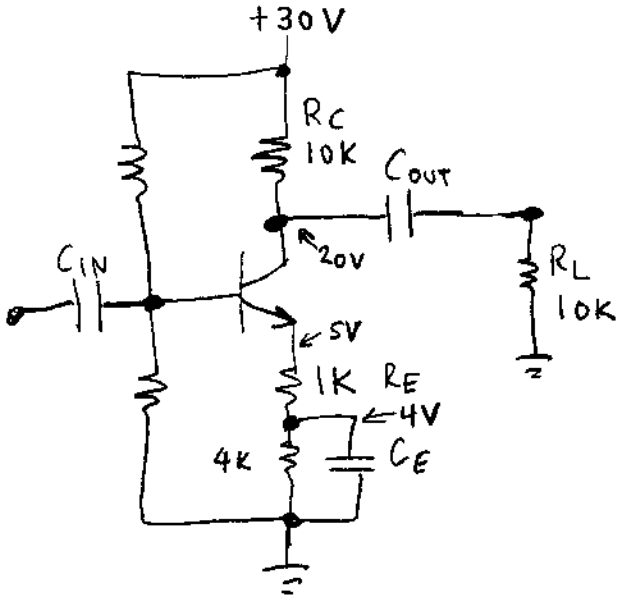

What is gain?

Output swing?

Is it biased correctly, for max symmetric output swing?

$$\beta = 100$$

$$V_A = 85$$

Gain: Reflect r_{π} to emitter

$$\frac{r_{\pi}}{\beta} = \frac{0.26}{I_E} = 26 \Omega$$

Find r_o :


$$r_o = \frac{V_{CE} + V_A}{I_C} = \frac{100}{1\text{mA}} = 100 \text{ k}$$

Now, gain is:

$$\frac{r_o \parallel R_C \parallel R_L}{\frac{r_{\pi}}{\beta} + R_E} = \frac{100\text{k} \parallel 10\text{k} \parallel 10\text{k}}{26 + 1000} = 4.64$$

One approach...



Think of capacitors as batteries...

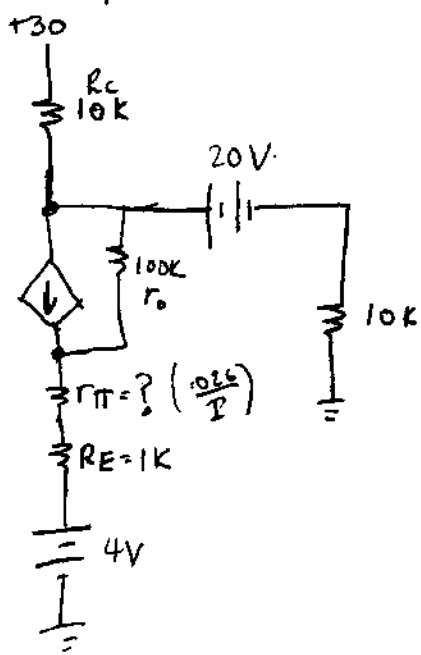

Consider the limits:

Transistor is cut off

Simplify!

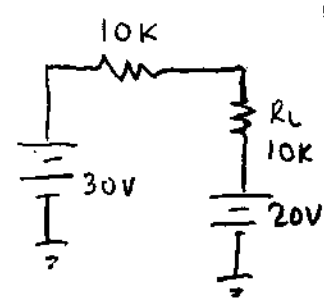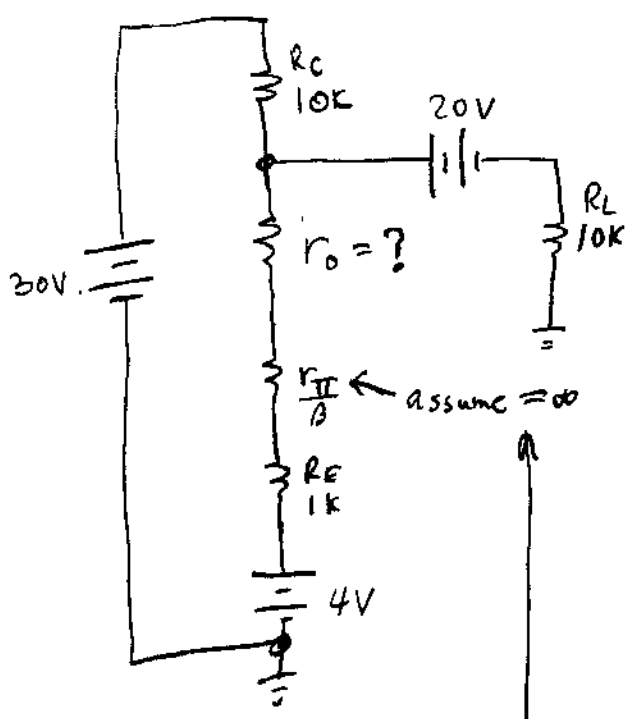


$V = 25$ at collector
 $V = 25 - 20$
 $= 5$ at load



$$\frac{r_{\pi}}{\beta} = \frac{0.26}{I_E} = \frac{0.26}{0} = \infty$$

Transistor is saturated

12C
4

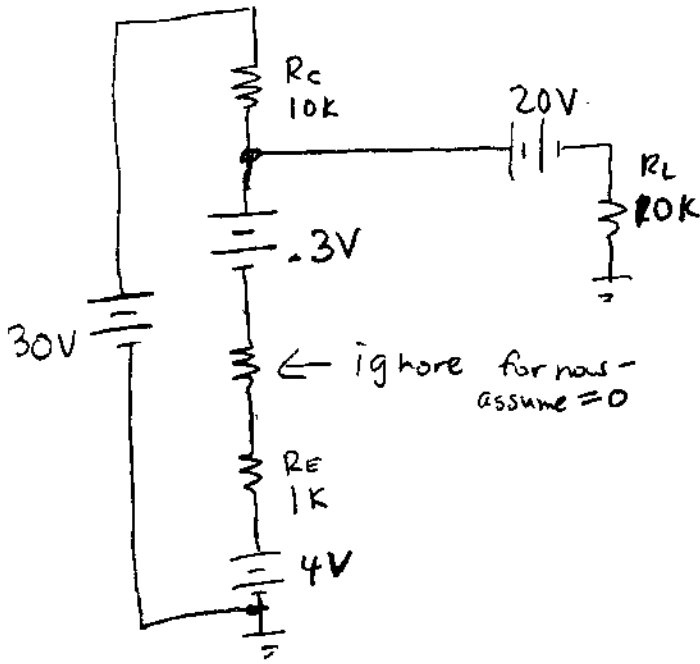

Simplify:

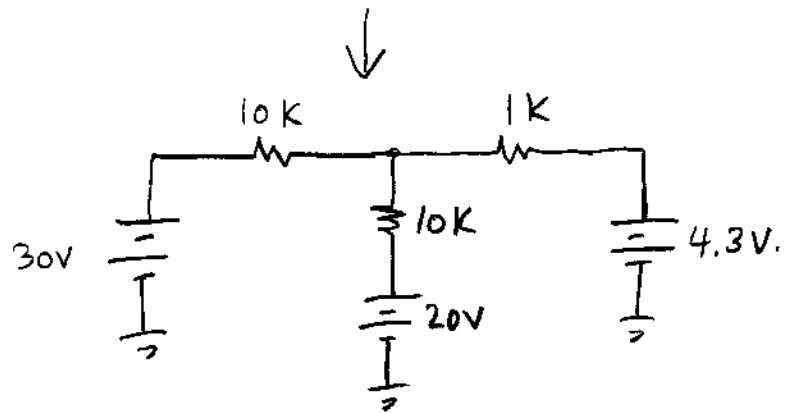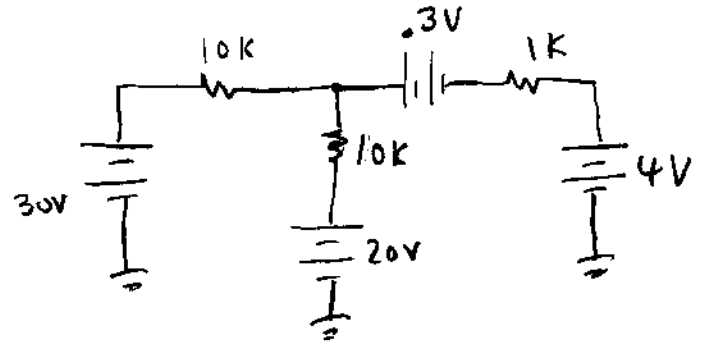

Nodal analysis

$$\frac{V-30}{10K} + \frac{V-20}{10K} + \frac{V-4.3}{1K} = 0$$

$$\frac{V-30}{10K} + \frac{V-20}{10K} + \frac{10V-43}{10K} = 0$$

$$12V - 93 = 0$$

$$V = \frac{93}{12} = 7.75 \text{ at collector}$$

$$V = 7.75 - 20 = -12.25 \text{ at load.}$$

Correct bias?

NO. it clips on top first.

Correct bias is

$$\frac{25 + 7.75}{2} = 16.375$$