
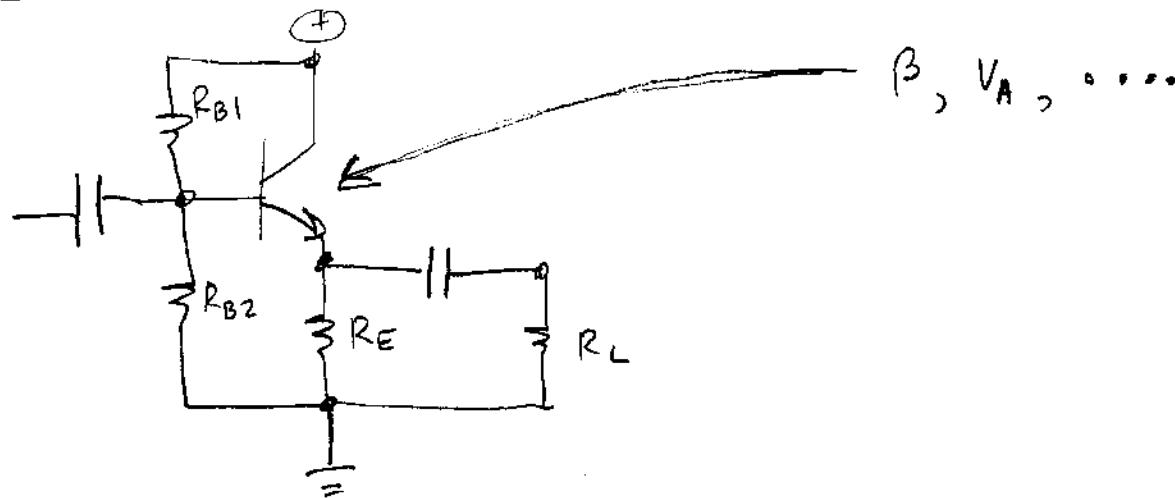


Analysis of the emitter follower


①

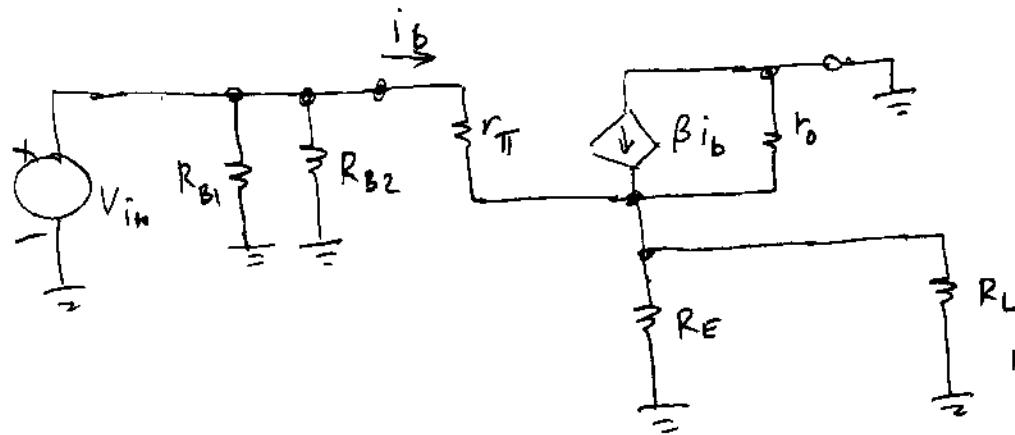


Substitute the model for the transistor!
(remember --- power is ground)




Rearrange:

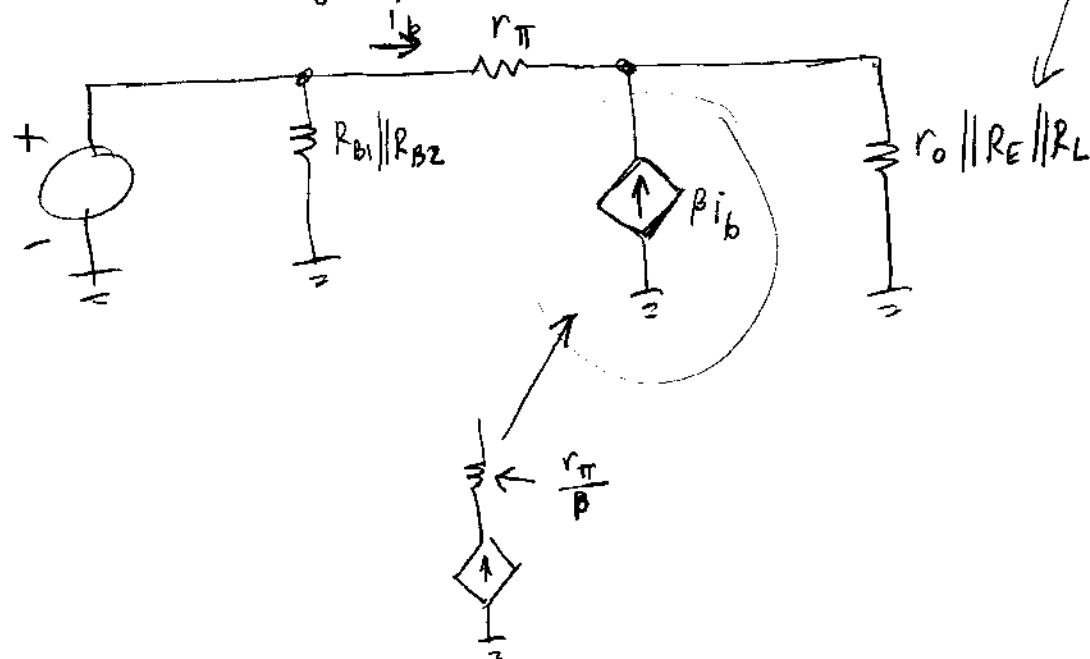

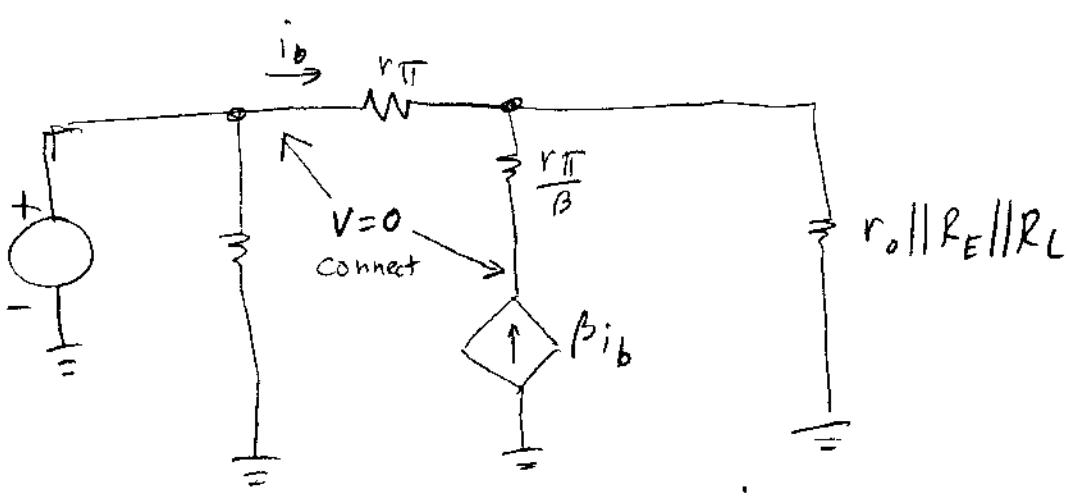To find output
impedance,
leave out
 R_L .



(2)

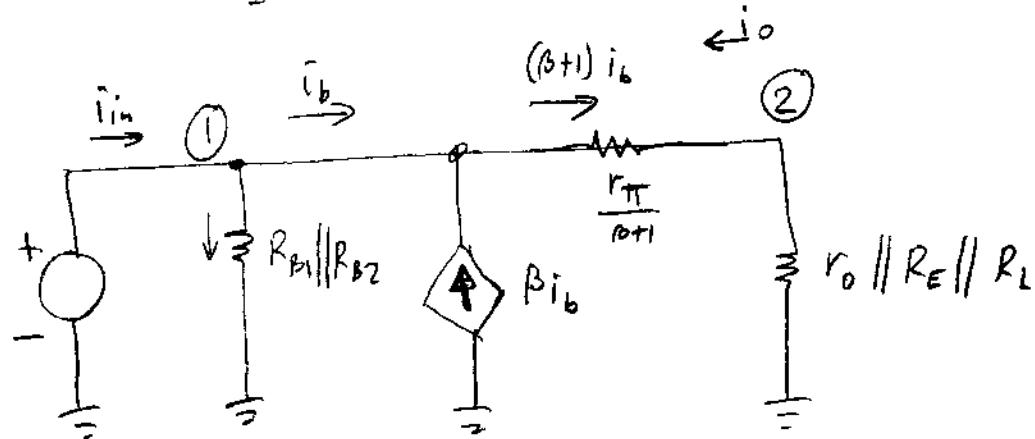

$$\frac{V_2}{V_1} = \frac{r_o || R_E || R_L}{\frac{r_T}{\beta+1} + r_o || R_E || R_L} \approx 1 \quad (\text{a little less})$$

$$R_{in} = \frac{V_1}{I_{in}} \quad i_b + \beta i_b - \frac{V_1}{\frac{r_T}{\beta+1} + r_o || R_E || R_L} = 0$$

$$(\beta+1) i_b = \frac{V_1}{\frac{r_T}{\beta+1} + r_o || R_E || R_L}$$

$$i_b = \frac{\frac{V_1}{r_o || R_E || R_L}}{\frac{\frac{r_T}{\beta+1}}{r_o || R_E || R_L} + \frac{1}{\beta+1}}$$

$$i_b = \frac{i_{LOAD}}{\beta+1}$$

(3)

So -- ignoring R_{B1}, R_{B2}


$$R_{in} = \frac{\frac{V_1}{V_1}}{\frac{\frac{r_\pi}{\beta+1} + r_o \parallel R_E \parallel R_L}{\beta+1}} = \frac{\beta+1}{\frac{r_\pi}{\beta+1} + r_o \parallel R_E \parallel R_L}$$

$$= (\beta+1) \left(\frac{r_\pi}{\beta+1} + r_o \parallel R_E \parallel R_L \right)$$

$$R_{in_{raw}} = r_\pi + (\beta+1) \underbrace{(r_o \parallel R_E \parallel R_L)}_{\text{Effective load.}}$$

$$\text{Real } R_{in} = R_{in_{raw}} \parallel R_{bias}$$



$$R_{out} \triangleq \left. \frac{V_2}{i_o} \right|_{V_{in}=0}$$

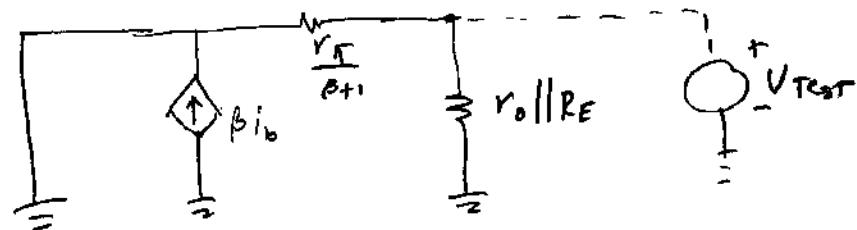

$$\text{For shorted input} -- r_o \parallel R_E \parallel \frac{r_\pi}{\beta+1} \approx \frac{r_\pi}{\beta+1}$$

But --- R_{out} depends on source resistance.

With ~~8~~ Source resistance

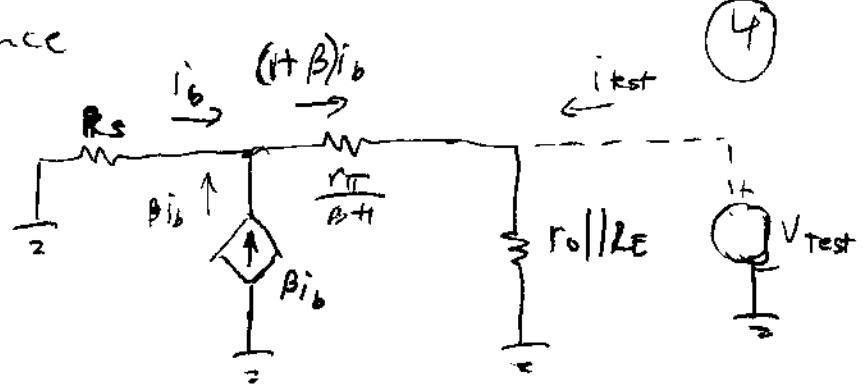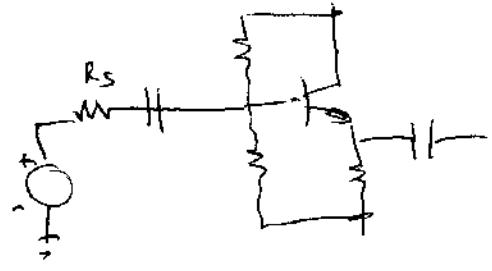

4

<u>HW -</u>	<u>P</u>	<u>#</u>	<u>P</u>	<u>#</u>
Em. follower	209	17, 18	235	33
	213	19, 20, 21	236	37
	214	22, 23	237	40
Common base	217	24	238	44, 47
	218	25, 26		
Multi-stage	225	27, 28, 29	239	50
	226	30	240	53
<u>Power</u>	228	31, 32	241	<u>56, 59</u>

Power considerations (4,10)

This section discusses "Class A" amplifiers.

You should be able to do quiescent power calculations

and power gain, power delivered to load, etc.

Put off (for now) supply and dissipation calculations with signal. — (the integrals)

it is less than quiescent.

Prepare to do it next fall (chapter 8)