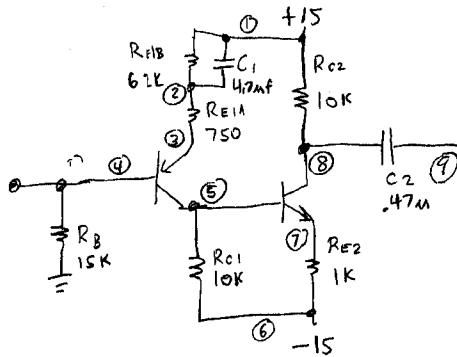


Topology: 2 common emitter stages, direct coupled. (1)




Stage 2:

Choose $R_{C2} = 10K$

$R_{E2} = 1K$ for gain ≈ 10

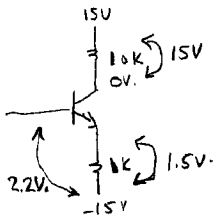Choose $V_{CE2} = 0$ so $V_{RC2} = 15$, $I = 1.5 \text{ ma}$




$$\frac{r_{\pi}}{\beta} = \frac{1026}{.0015} = 17.3 \Omega$$

$$\text{Actual gain} = \frac{10000}{1017} = 9.83$$

$$Z_{in \text{ to stage 2}} = \beta R_E = (50)(1K) = 50K$$

Stage 1:

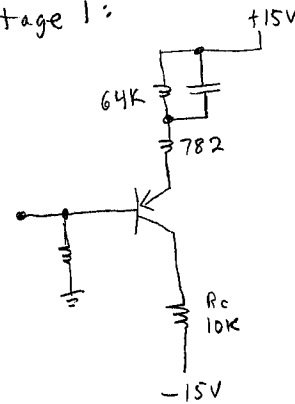

$V_{RC} = 2.2$ from stage 2 (2)

Choose $V_B = 0$

Then $V_E = .7$

Choose $R_C = 10K$

Note -- R_E will be $< 1K$

$Z_{in} \approx \beta R_E \times 50K$
or less.

Making it lower will make Z_{in} lower, bias more critical.

$$I_C = \frac{2.2}{10K} = .22 \text{ ma}$$

$$R_E = \frac{14.3}{.22 \text{ ma}} = 65K$$

$$\frac{r_{\pi}}{\beta} = \frac{1026}{.00022} = 118 \Omega$$

Effective collector load = $10K$ max
 $8.3K$ min ($\beta=50$)
 $9.0K$ typ ($\beta=10$)

Need gain: 112.2 max total
 89.1 min

Design for 100.

$$R_{E \text{ effective}} = \frac{9K}{10} = 900 \Omega$$

$$R_{E1A} = 900 - 118 = 782 \Omega \rightarrow \text{use } 750 \Omega$$

$$R_{E1B} = 65K - 782 \approx 64K \rightarrow \text{use } 62K$$

③

$$Z_{in\ min} = (900)(50) = 45K$$

↑
to amp

$$Z_{in\ required} > 10K$$

$$\text{Choose } R_B = 15K \quad (R_B \parallel 45K > 10K)$$

$$\text{Check: } Z_{in} = 15K \parallel 45K = 11.25K$$

Check base current:

$$I_B = \frac{.22mA}{50} = 4.4\ \mu A$$

$$\text{Voltage drop in } R_B = (4.4\ \mu A)(15K) = .066\ V.$$

Ignore it.

Capacitors:

With no load, C_2 doesn't matter, only C_1 matters.

With 10K load -- Allow 1.5 dB at 100 Hz

Estimate 3 dB at 50 Hz (each stage)
 $\omega = 2\pi f = 314$

$$C_2 = \frac{1}{2\pi f R} = \frac{1}{(314)(100)} = 3.18 \times 10^{-7} = .32\ \mu F \rightarrow \text{use } .47\ \mu F$$

$$C_1 = \frac{1}{2\pi f R} = \frac{1}{(314)(900)} = 3.53\ \mu F \rightarrow \text{use } 4.7\ \mu F$$

FET - analysis.

④

Finding g_m :

$$I_D = K (V_{GS} - V_{TH})^2 = K V_{GS}^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{GS}}{\partial V_{GS}} = (2K V_{GS}) (1) = 2K V_{GS}$$

$$\text{But } I_D = K V_{GS}^2 = (\sqrt{K} V_{GS})^2$$

$$g_m = 2K V_{GS} = 2\sqrt{K}\sqrt{K} V_{GS} = 2\sqrt{K}\sqrt{I_{DQ}} = 2\sqrt{K I_{DQ}}$$

Exercises: p. 266 7, 8, 9

```

list
Vcc 1 0 DC 15.
Vee 6 0 DC -15.
Vin 4 0 GENERATOR
Rb 4 0 15.K
Reib 1 2 62.K
Rela 2 3 750.
Rc1 5 6 10.K
Rc2 1 8 10.K
Re2 7 6 1.K
C1 1 2 4.7u
C2 8 9 470.n
Q1 5 4 3 3 p area=1.
Q2 8 5 7 7 n area=1.
.model n npn ( kf=0. af=1. bf=50. br=1. is=100.E-18 nf=1. nr=1. i
sc=0. c4=0. nc=2. ise=0. c2=0. ne=1.5 rb=0. rbm=0. re=0. rc=0.
cjc=0. cje=0. cjs=0. fc=0.5 mjc=0.33 mje=0.33 mjs=0. vjc=0.75 vje=
0.75 vjs=0.75 xcjc=1. itf=0. ptf=0. tf=0. tr=0. xtf=0. xtb=0. xti=
3. eg=1.11)
*+()
.model p pnp ( kf=0. af=1. bf=50. br=1. is=100.E-18 nf=1. nr=1. i
sc=0. c4=0. nc=2. ise=0. c2=0. ne=1.5 rb=0. rbm=0. re=0. rc=0.
cjc=0. cje=0. cjs=0. fc=0.5 mjc=0.33 mje=0.33 mjs=0. vjc=0.75 vje=
0.75 vjs=0.75 xcjc=1. itf=0. ptf=0. tf=0. tr=0. xtf=0. xtb=0. xti=
3. eg=1.11)
*+()
pr op v nodes
op
#          v(1)      v(2)      v(3)      v(4)      v(5)      v(6)      v(7)
          v(8)      v(9)
300.15    15.      0.90588    0.73538    44.573p   -13.009   -15.      -13.78
8         3.1148    0.
pr op vbe q*
op
#          vbe(Q1)    vbe(Q2)
300.15    -0.73538    0.77868
pr op ic q*
op
#          ic(Q1)     ic(Q2)
300.15    -222.87u    0.0011885
pr ac vdb 4 8
ac 1k
#Freq      vdb(4)      vdb(8)
1.K        -7.7592n     39.212
ac 100
#Freq      vdb(4)      vdb(8)
100.       -7.497n     38.582
del n p
b
.model p pnp bf=100
.model n npn bf=100

op
#          ic(Q1)     ic(Q2)
300.15    -225.07u    0.0013236
ac1k
#Freq      vdb(4)      vdb(8)
1.K        -6.7847n     40.121
del n p
b
.model n npn bf=200
.model p pnp bf=200

op
#          ic(Q1)     ic(Q2)
300.15    -226.19u    0.0014018
ac
#Freq      vdb(4)      vdb(8)
1.K        -6.2901n     40.606

```

```

del n p
b
.model p pnp bf=100 is=1e-15
.model n npn bf=100 is=1e-15

op
#          ic(Q1)     ic(Q2)
300.15    -226.01u    0.0013847
pr op v nodes
op
#          v(1)      v(2)      v(3)      v(4)      v(5)      v(6)      v(7)
          v(8)      v(9)
300.15    15.      0.84739    0.67619    22.601p   -12.878   -15.      -13.60
1         1.1531    0.
ac
#Freq      vdb(4)      vdb(8)
1.K        -6.7852n     40.132
cdl n p
del n p
b
.model n npn bf=100 is=10e-15
.model p pnp bf=100 is=10e-15

op
#          v(1)      v(2)      v(3)      v(4)      v(5)      v(6)      v(7)
          v(8)      v(9)
300.15    15.      0.78865    0.61674    22.694p   -12.875   -15.      -13.54
           0.54212    0.
ac
#Freq      vdb(4)      vdb(8)
1.K        -6.7857n     40.143
>

```