

# Amplifier design -

①

50 watts,  $8\Omega \rightarrow P = \frac{V^2}{R} \rightarrow PR = V^2 \rightarrow V = \sqrt{PR}$   
 20 Volts, RMS = 28.3 V peak  
 $I = \frac{V}{R} \Rightarrow 2.5A, \text{RMS}, 3.54A \text{ peak}$

Use 60 volt powersupply.


Voltage gain =  $\frac{28.3}{.001} = 28,300$  (89 dB)

use 4 voltage gain stages (12.97) (13) each

Assume  $Z_{in} > 10K$  (not spec'd)

## Output stage

②

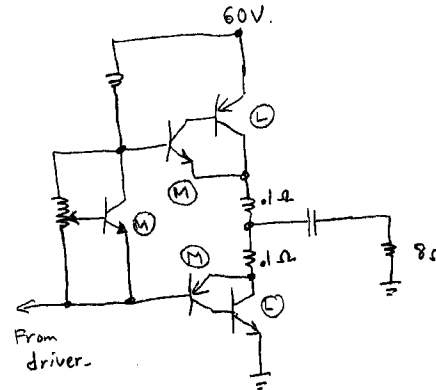

Composite/darlington output stage -

$\beta = 2500$

Need base drive current

$\frac{3.54A}{2500} = 1.41 \text{ ma}$

Power at half output:

$\frac{V^2}{R} = \frac{(30V)^2}{8} = 112.5 \text{ Watts} \approx 120 \text{ Watts}$

50% duty cycle  $\rightarrow \approx 60 \text{ Watts}$

This is above the rating of the "large" transistor.


We could use 2 in parallel, but often they will use one because it rarely operates that hot.

Power in driver:

$\frac{(30)^2}{50 \times 8} = 2.25 \text{ Watts}$ , 50% duty cycle  $\rightarrow 1.125 \text{ Watts}$

No problem for "medium" transistor.

Driver

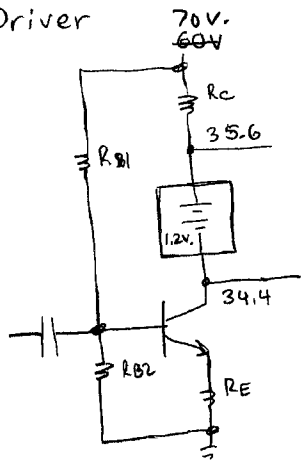


Need higher than 60 volts <sup>③</sup>

Due to voltage drop in Rc and RE.

Increase it to 70.

Set gain = 13.

Determine Rc

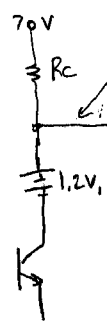

$$V_Q = 35.6$$

$$V_{Peak} = V_Q + V_{arr_{Peak}} = 35.6 + 28.3 = 63.9$$

call it 64

$$V_{Rc} = 70 - 64 = 6$$

$$R_c = \frac{V}{I} = \frac{6}{1.41 \text{ ma}} = 4.25 \text{ K}$$

use 3.3K

This means  $I_{CQ} = \frac{70 - 35}{3.3 \text{ K}} = \frac{35}{3.3 \text{ K}} = 10.6 \text{ ma}$

Power =  $(35)(10.6 \text{ ma}) = 371 \text{ mw}$

Rc must be rated at least .37 watt  
use 1/2 or 1 watt.

Transistor dissipation OK.

Driver p.2

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{135}{.0106} = 12.7 \text{ K} \quad \text{④}$$

$$\frac{r_{\pi}}{\beta} = \frac{.026}{I_E} = \frac{.026}{.0108} = 2.4 \Omega$$

Effective  $R_{LOAD} = 8 * 2500 = 20 \text{ K}$

Effective  $R_c = 20 \text{ K} \parallel 12.7 \text{ K} \parallel 3.3 \text{ K} = 2316$

For gain = 13  $R_{E_{Effective}} = 178.15$

Actual  $R_E = 178.15 - 2.4 = 175.75$

use 180  $\Omega$

$V_E = (0.0108)(220) = 1.94 \text{ V}$

$V_B = V_E + .7 = 2.6 \text{ V}$

$I_B = \frac{10.6 \text{ ma}}{50} = .21 \text{ ma}$

Choose bias network current = 2 ma

$R_{B2} = \frac{2.6}{2 \text{ ma}} = 1.3 \text{ K} \leftarrow \text{Too low.}$

try 1 ma


$R_{B2} = \frac{2.6}{1 \text{ ma}} = 2.6 \text{ K}$  (a little better)  
use 2.7K

$\frac{R_{B1}}{R_{B2}} = \frac{X}{2.7 \text{ K}} = \frac{67}{3} \quad X = (2.7 \text{ K}) \frac{67}{3} = 67 \text{ K}$

Add parallel resistor for  $I_B$

$R = \frac{V}{I_B} = \frac{67}{.21 \text{ ma}} = 319 \text{ K}$

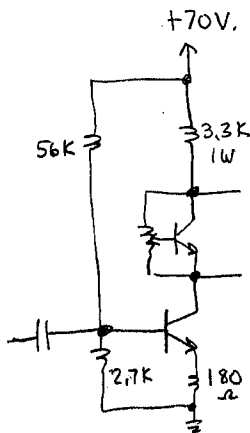$R = 67 \text{ K} \parallel 319 \text{ K} = 55.2 \text{ K}$  use 56K



Pre-driver


⑤

Need: gain = 13

$$R_{LOAD} = 2.7K \parallel (180)(50) \parallel 50K = 2K$$

$$\text{Output voltage swing} = \frac{28.3 \times 2}{13} = 4.35 \text{ p-p. (2.2V peak)}$$

Use emitter follower to drive 2K.

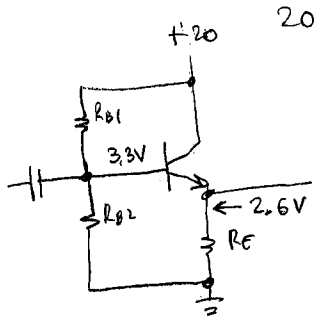

Direct couple to next stage, eliminating its bias resistors.

$$V_E = 2.6V$$

$$V_B = V_E + 0.7 = 3.3V.$$

→ sees 2K

$$Z_{in} = (2K)(50) = 100K$$

$I_E$  - must supply  $(3.3 + 2.2)V$  into 2K

$$\frac{5.5V}{2K} = 2.75 \text{ ma}$$

Make  $R_E$  2.7K (from the next stage bias network)

$$I_E = \frac{2.6V}{2.7K} \approx 1 \text{ ma}$$

$$I_B = \frac{1}{50} = .02 \text{ ma}$$


Choose Bias resistor current .2ma

$$R_{B2} = \frac{3.3V}{.2 \text{ ma}} = 16.5K \text{ use } 16K$$

$$R_{B1} = \frac{20 - 3.3}{.2 \text{ ma}} = \frac{16.7}{.2 \text{ ma}} = 75.9K \text{ use } 75K$$

Circuit so far:


⑥

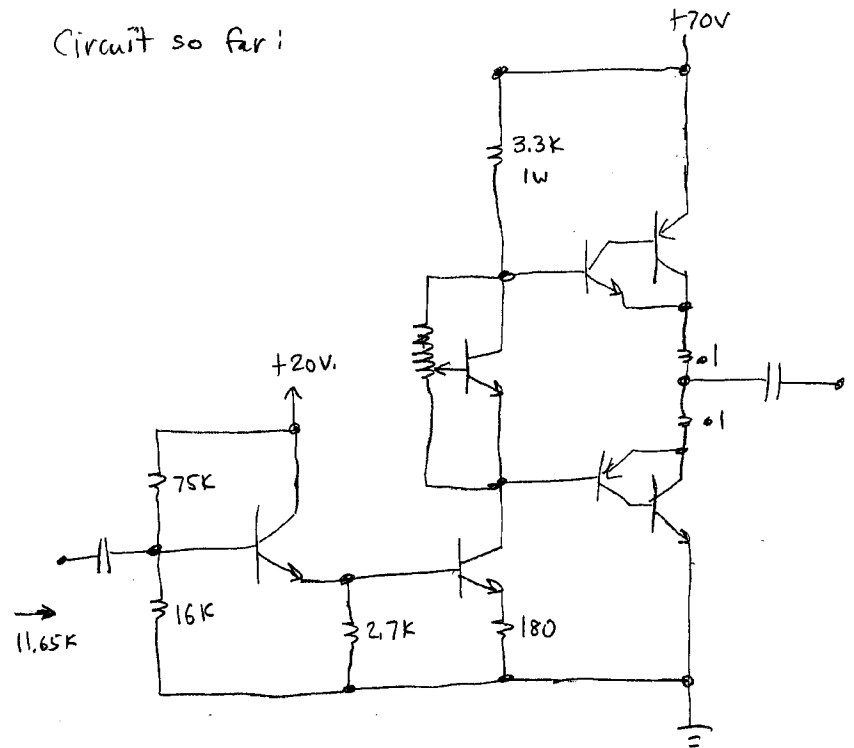

Preamp:

Use 3 identical stages,  $A_v = 13$  each

$$Z_{in} = 10K \quad R_L = 10K$$

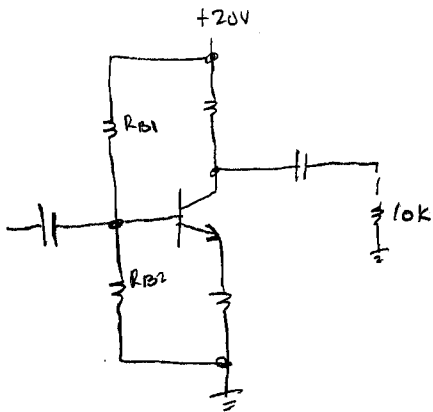

Choose  $R_C = 10K$   $V_C = 11V$  (for  $V_{CE} \approx 10$ )

$$\text{So } \dots V_{RC} = 9 \quad I_C = .9 \text{ ma}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{109}{.9 \text{ ma}} = 121K$$

$$\frac{r_{II}}{\beta} = \frac{.026}{I_E} = \frac{.026}{.9 \text{ ma}} = \frac{26 \text{ mV}}{.9 \text{ ma}} = 29 \Omega$$

$$\text{Effective collector load} = 10K \parallel 10K \parallel 121K = 4.8K$$

$$\text{Want effective } R_E = \frac{4.8K}{13} = 369$$

$$\text{Actual } R_E = 369 - 29 = 340 \Omega \text{ — use } 330 \Omega$$

$$Z_{in} = (330)(50) = 16.5K$$

⑦

Preamp p.2

Bias resistors --

for  $Z_{in} = 10K$ , want the parallel value to be

$$R_D = \frac{1}{\frac{1}{10K} + \frac{1}{16.5K}} = 25K$$


For  $V_C = 11V$ .

$$V_E = (.9 \text{ ma})(330 \Omega) = 297 \text{ mV}$$

$$V_B = 1V$$

make  $R_{B2} = 27K$
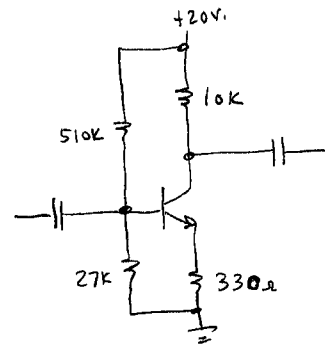
$$R_{B1} = (19)(27K) = 513K \quad \text{use } 510K$$



Put volume control between first + second stages.

⑧

