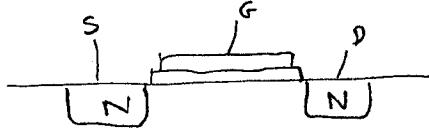



MOSFETs - a little deeper (Chapter 4)

Recall ---

N-channel MOSFET (4.1.)




No conduction D-S
with $V_{DS} = 0$

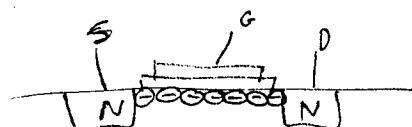



$$V_S \approx V_D$$

Looks like
a variable resistor.

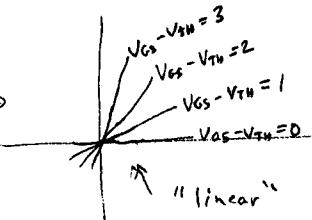Positive voltage on
gate causes formation
of channel —
Now current can flow.



As V_{DS} is increased ---

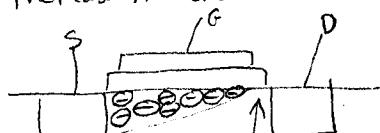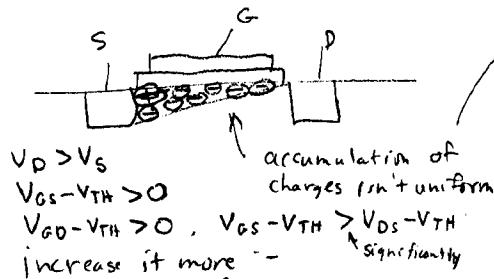

$V_{GS} - V_{TH} > 0$ ← This part
conducts
 $V_{GD} - V_{TH} < 0$ ← "pinched off"
pinch off region
→ "Saturation" region

1B

Formulas --

$$I_D = \begin{cases} 0 & V_{GS} - V_{TH} < 0 \\ K(2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2) & V_{GS} - V_{TH} > 0, V_{DS} < V_{GS} - V_{TH} \\ K(V_{GS} - V_{TH})^2 & V_{GS} - V_{TH} > 0, V_{DS} > V_{GS} - V_{TH} \end{cases}$$

↑

$$K = \frac{1}{2} K' \frac{W}{L} \frac{\text{Amps}}{\text{Volts}^2}$$

(As written in Horley, Guru, etc--)

1B
2

Usually K' is specified -- "process transconductance parameter"

$$I_D = \begin{cases} 0 & V_{GS} - V_{TH} < 0 \\ K' \frac{W}{L} ((V_{GS} - V_{TH})V_{DS} - \frac{1}{2} V_{DS}^2) & V_{GS} - V_{TH} > 0, V_{DS} < V_{GS} - V_{TH} \\ \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 & V_{GS} - V_{TH} > 0, V_{DS} > V_{GS} - V_{TH} \end{cases}$$






W = width of gate

L = length of gate

- usually around 1 μm (micron).


usually $W > L$
sometimes $W \gg L$

Top View

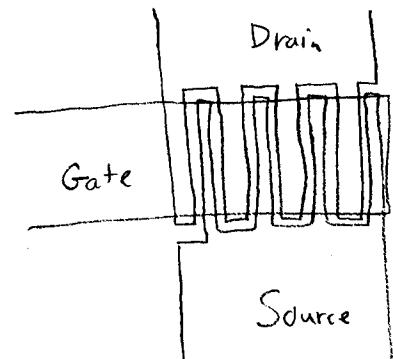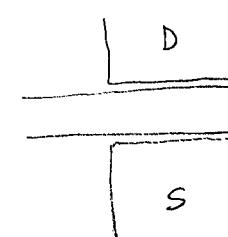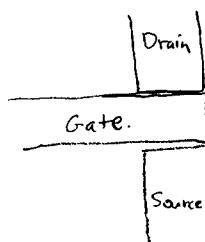

Determining K' ..

$$K' = M_n C_{ox}$$

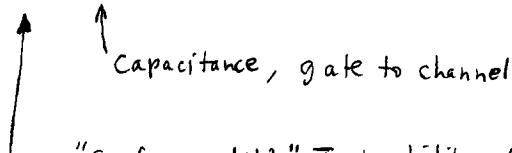

"Surface mobility," = mobility of carriers in the channel -

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \leftarrow \begin{array}{l} \text{permittivity of the insulator} \\ = 3.45 \times 10^{-11} \frac{\text{Farad}}{\text{meter}} \text{ for SiO}_2 \end{array}$$

Thickness of the insulator

→ so K depends on: Thickness of insulator
Width
Length.

M_n is sometimes called M_0 .

Spice name V_O or v_o - units = $\frac{\text{cm}^2}{\text{volt}\cdot\text{sec}}$

Letter O, number zero

Typical value = $600 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} = 600 \times 10^{-4} \frac{\text{m}^2}{\text{volt}\cdot\text{sec}}$

Example: $M_n = 600$
 $t_{ox} = 10^{-8}$ meter ($.01 \mu\text{m}$)


What is K' ?

Units:
Farad = $\frac{\text{coulomb}}{\text{volt}}$
Amps = $\frac{\text{coulombs}}{\text{sec.}}$
 $\frac{\text{F}}{\text{volt sec.}} = \frac{\text{coul.}}{\text{volt sec.}} = \frac{\text{coul.}}{\text{volt sec.} \cdot \text{car.}} = \frac{\text{coul.}}{\text{volt sec.}^2} = \frac{\text{amps}}{\text{volt sec.}^2}$

$$\begin{aligned} K' &= M_n C_{ox} = \\ &= (600 \times 10^{-4} \frac{\text{m}^2}{\text{volt}\cdot\text{sec}}) (3.45 \times 10^{-3} \frac{\text{F}}{\text{m}^2}) \\ &= 2.07 \times 10^{-4} \frac{\text{F}}{\text{volt sec}} = \frac{\text{amps}}{\text{volt sec}^2} \end{aligned}$$

(IB
3)

Example:

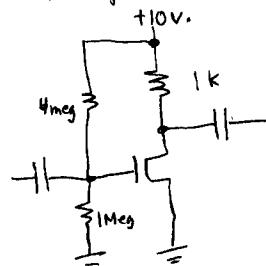

$$M_n = 600 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} = 6 \times 10^{-2} \frac{\text{m}^2}{\text{V}\cdot\text{s}}$$

$$t_{ox} = 0.01 \mu\text{m} = 10^{-8} \text{m}$$

$$W = 1 \mu\text{m}$$

$$L = 10 \mu\text{m}$$

$$V_{TH} = 0$$

(IB
4)

$$K' = 2.07 \times 10^{-4} \approx 2 \times 10^{-4}$$

$$K' \frac{W}{L} = 2 \times 10^{-3}$$

$$V_{GS} = 0 \Rightarrow V_{GS} - V_{TH} = 2$$

$$\begin{aligned} I_D &= \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \left(\frac{1}{2}\right) (2 \times 10^{-3}) (2)^2 \\ &= 4 \times 10^{-3} \text{ Amps} \end{aligned}$$

$$\begin{aligned} \text{For } R_D = 1\text{K}, V_R = 4 &\Rightarrow V_D = V_{CC} - V_D \\ &= 10^{-4} \\ &= 6 \end{aligned}$$

$$\boxed{V_{DS} = 6}$$

$$\boxed{I_D = 4 \text{ mA}}$$


Gain = ? -

$$g_m = \frac{dI_{out}}{dV_{in}}$$

$$\begin{aligned} g_m &= 2 K (V_{GS} - V_{TH}) = 2 \sqrt{K I_D} \\ &= K' \frac{W}{L} (V_{GS} - V_{TH}) = \sqrt{2 K' \frac{W}{L} I_D} \\ &= (2 \times 10^{-3})(2) = \sqrt{2(2 \times 10^{-3})(4 \times 10^{-3})} \\ &= 4 \times 10^{-3} \end{aligned}$$

$$\frac{V_{out}}{V_{in}} = -g_m R_L = -(4 \times 10^{-3})(10^3) = -4$$

"Design" for gain = -10, $R_D = 1K$

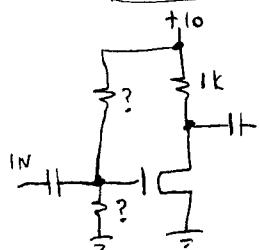

Same process as before:

$$\frac{V_{out}}{V_{in}} = -g_m R_L$$

$$-10 = -g_m (1000)$$

$$g_m = \frac{10}{1000} = .01 = 1 \times 10^{-2}$$

(1B)
5

To set bias ...


$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$5 \times 10^{-3} = \frac{1}{2} (10^{-2}) (V_{GS} - V_{TH})^2$$

$$\frac{5 \times 10^{-3}}{5 \times 10^{-2}} = (V_{GS} - V_{TH})^2$$

$$= 1 \text{ volt}$$

(1B)
6

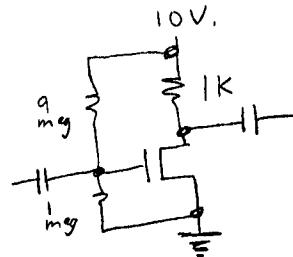

From before, $K' = 2 \times 10^{-4}$

Choose $V_{DS} = 5$ (half of supply)

This means $I_D = 5 \text{ mA} = 5 \times 10^{-3} \text{ Amps.}$

$$g_m = \sqrt{2 K' \frac{W}{L} I_{DQ}}$$

$$1 \times 10^{-2} = \sqrt{(2)(2 \times 10^{-4}) \frac{W}{L} (5 \times 10^{-3})}$$

$$1 \times 10^{-4} = (2)(2 \times 10^{-4}) \frac{W}{L} (5 \times 10^{-3})$$

$$\frac{1 \times 10^{-4}}{2 \times 10^{-6}} = \frac{W}{L}$$

$$50 = \frac{W}{L} \Rightarrow L = 1 \mu$$

$$W = 50 \mu$$


L - usually choose the minimum.
Sometimes increase to increase power capability.

$$K' \frac{W}{L} = (2 \times 10^{-4}) \frac{50}{1}$$


$$= 10^{-2}$$

"Channel length modulation"

Better equivalent circuit:

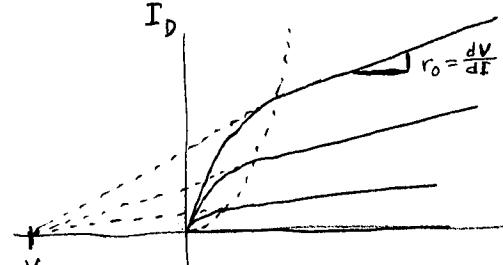

G_m

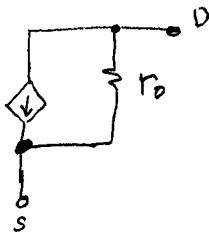

(IB)
7

$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

added term.

$$i_d = \underbrace{\frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2}_1 + \underbrace{\frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda}_2 V_{DS}$$

the current source

call the I_D (uppercase I)

r_o

$$\frac{1}{r_o} = \frac{i}{V_{DS}} = \lambda \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$


$$i_D = I_D (1 + \lambda V_{DS})$$

$$r_o = \frac{1}{\lambda I_D}$$

$\curvearrowleft I_D = \text{not counting channel length modulation.}$

(IB)
7

Example --

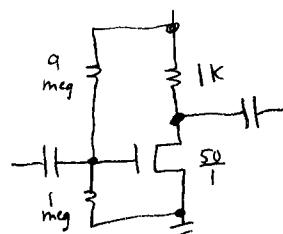

Suppose $V_A = 100$

$\lambda = 0.01$

What is the gain now?

$$I_D = 5 \text{ mA}$$


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.005)} = 20 \text{ k} \quad (2 \times 10^4)$$

$$\text{Effective } R_{LOAD} = 1\text{k} \parallel 20\text{k} = 952 \text{ }\Omega$$

$$\text{Gain} = -g_m R_L = -(1 \times 10^{-2})(952) = -9.52$$

Example ---

(substitute current source for R_D)

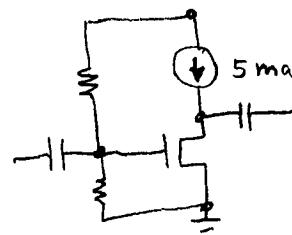

$$g_m = 1 \times 10^{-2} \text{ (as before)}$$

$$\text{gain} = -g_m R_L \leftarrow \text{what is } R_L?$$

$$R_L = r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.005)} = 20 \text{ k}$$


$$\text{gain} = -g_m R_L = -(1 \times 10^{-2})(2 \times 10^4) = -200$$

\Rightarrow We can get decent gain from FETs with no load!


Spice i $V_{TH} = "VTO"$
 letter O. $\lambda = "lambda"$

"Channel length modulation"

Better equivalent circuit:

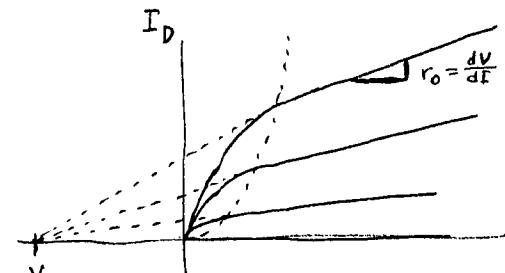

G_{DS}

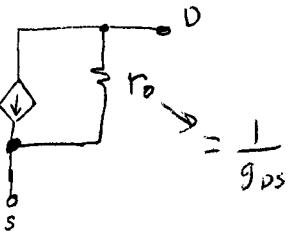

(IB)
7

$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

added term.

$$I_D = \underbrace{\frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2}_{\text{the current source}} + \underbrace{\frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda V_{DS}}_{r_0}$$

call this I_D (uppercase I)

$$\frac{1}{r_0} = \frac{I}{V_{DS}} = \lambda \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$


$$i_D = I_D (1 + \lambda V_{DS})$$

$$r_0 = \frac{1}{\lambda I_D}$$

I_D = not counting
channel length
modulation.

)

Example --

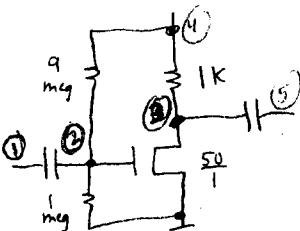

Suppose $V_A = 100$
 $\lambda = 0.01$

What is the gain now?

$$I_D = 5 \text{ mA}$$

$$r_0 = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.005)} = 20 \text{ k} \quad (2 \times 10^4)$$

(IB)
8

why?


$$\text{Effective } R_{LOAD} = 1 \text{ k} \parallel 20 \text{ k} = 952 \text{ }\Omega$$

$$\text{Gain} = -g_m R_L = -(1 \times 10^{-2})(952) = -9.52$$

9.97

Example ---

(substitute current source for R_D)

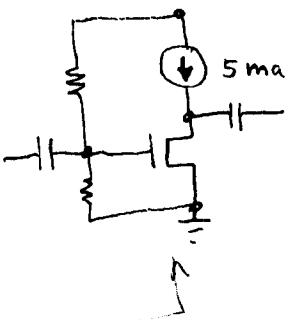

$$g_m = 1 \times 10^{-2} \text{ (as before)}$$

$$\text{gain} = -g_m R_L \leftarrow \text{what is } R_L?$$

$$R_L = r_0 = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.005)} = 20 \text{ k}$$

$$\text{gain} = -g_m R_L = -(1 \times 10^{-2})(2 \times 10^4) = -200.$$

212

\Rightarrow we can get decent gain from FETs
with no load!

bias ... $V_D = ?$ \leftarrow because of r_0

)