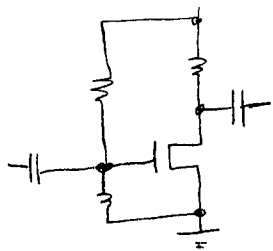



Biasing

Simple V_{GS} :



Very sensitive to process variations

"4-resistor"

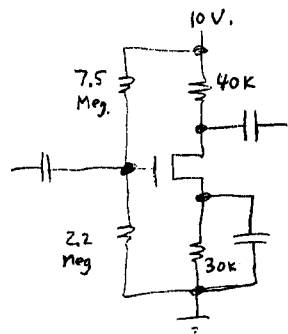

To analyze

Find gate voltage:

$$V_G = 2.27$$

Loop analysis

To design:

Pick voltage and current:

$$V_{DD} = 10$$

$$V_D = 6 \quad V_S = 3 \quad V_{GS} = 3$$

$$I_D = 0.1 \text{ mA}$$

$$\Rightarrow R_D = \frac{10-6}{10^{-4}} = 40 \text{ K}$$

$$R_S = \frac{3}{10^{-4}} = 30 \text{ K}$$

$$I_D = \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$10^{-4} = \frac{1}{2} (2 \times 10^{-4}) (10) (V_{GS} - V_{TH})^2$$

$$(V_{GS} - V_{TH})^2 = \frac{10^{-4}}{10 \times 10^{-4}} = \frac{1}{10}$$

$$V_{GS} - V_{TH} = 0.316$$

$$V_{GS} = 2.316 \text{ — use voltage divider}$$

(3C)
1


HW
4.3 all exercises
p.363: 36, 37, 38
p.364: 42, 43
p.365: 46, 47, 48
Look for shortcuts

4.4

4.5: all exercises

Drain-Gate Feedback

(3C)
2

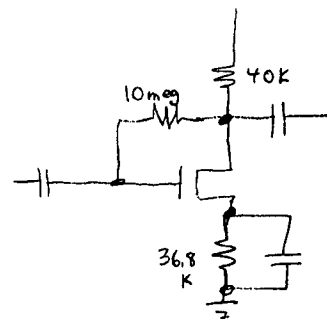

Low input resistance

To analyze:

To design:

$$V_{GS} = V_{DS}$$

Pick voltage and current:

$$V_{DD} = 10$$

$$V_D = 6$$

$$I_D = 0.1 \text{ mA}$$

$$k' = 2 \times 10^{-4}$$

$$V_{TH} = 2$$

$$\frac{W}{L} = 10$$

$$R_D = 40 \text{ K}$$

$$I_D = \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$10^{-4} = \frac{1}{2} (2 \times 10^{-4}) (10) (V_{GS} - V_{TH})^2$$


$$\frac{1}{10} = (V_{GS} - V_{TH})^2$$

$$V_{GS} = 2.316$$

$$\Rightarrow V_{DS} = 2.316 \quad V_S = V_D - V_{DS} = 6 - 2.316 = 3.68$$

$$R_S = \frac{V_S}{I} = \frac{3.68}{0.1 \text{ mA}} = 36.8 \text{ K}$$

Current source

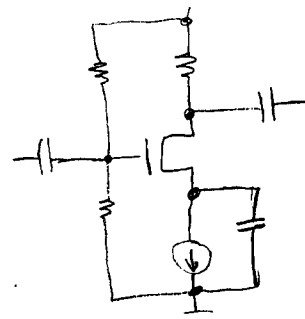

For current source —

use current mirror

Easy design —


Very consistent.

Getting rid of those resistors and capacitors

30 (7)

or... current mirrors
differential amps
etc.

Remember this?

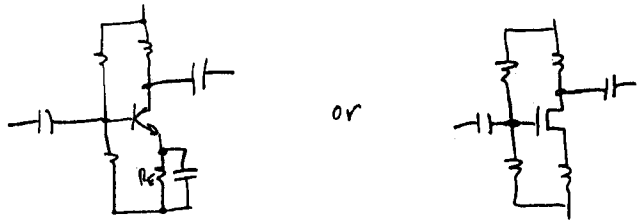


How to eliminate the emitter resistor and capacitor?

Answer: use more transistors.

Try this:

(inverting amp.)

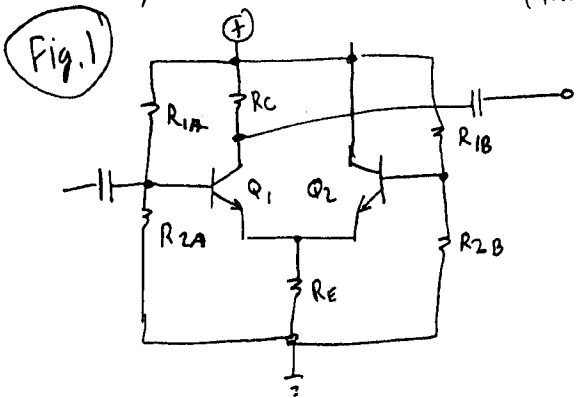

Q_1 and Q_2 are identical transistors.
(same V_{BE} , β , etc.)

$$R_{1A} = R_{1B}$$


$$R_{2A} = R_{2B}$$

so Q_1, Q_2 have identical bias.

Q_2 is an emitter follower on the DC bias, so it eliminates the need for the capacitor.

Now, try this one:

31 (2)

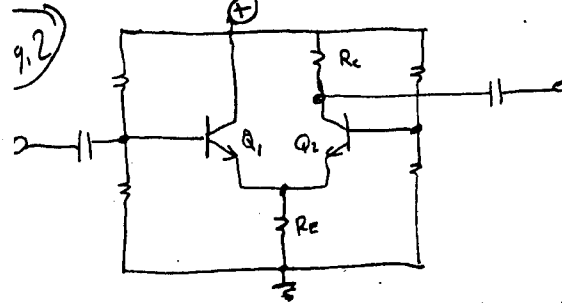

This is the same except that the output is taken off Q_2 instead of Q_1 .

Q_1 is an emitter follower.

Q_2 is a common base amplifier.


Low input impedance
High output impedance
Current gain = 1
Voltage gain = high.

This (Fig 2) has characteristics the same as Fig. 1, except that it is non-inverting.

$$\text{Fig 2 Gain} = \frac{R_C'}{\left(\frac{2V_{BE}}{\beta}\right)} \rightarrow \text{Fig 1 Gain} = \frac{-R_C'}{\left(\frac{2V_{BE}}{\beta}\right)} \quad \text{Effective load.}$$

Usual application --


use + and - supply, so $V_B = 0$:

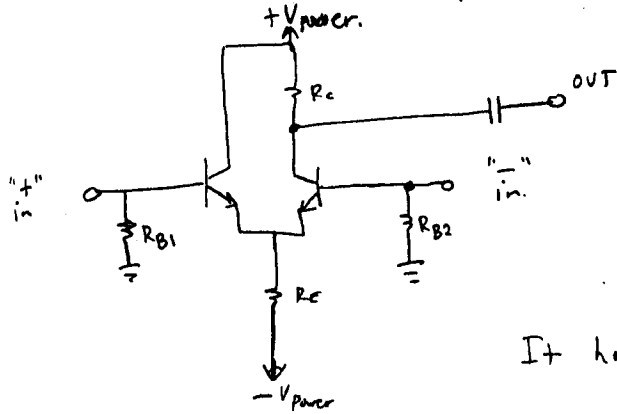

This is a "differential" amplifier.

It has 2 inputs, 1 output.

Now, add another stage.

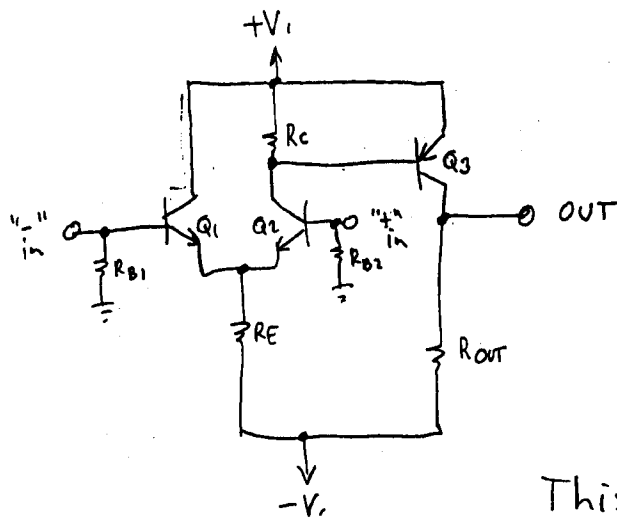

This additional stage inverts phase, so switch + and - inputs.

It also restores the DC level, proper bias puts OUT at 0 V.DC.

This is a simple op-amp.

High gain! No capacitors!

Other nice properties --

- Q_1 and Q_2 track each other in V_{BE} with temperature.

→ easy to bias
not temperature sensitive.

For best balance, Q_1 and Q_2 should match. -

Exact V_{BE} , β is not critical

but matching affects output offset.

For best results, use adjacent transistors from the same wafer.

→ Easy on an IC.


→ Can buy matched pairs.

Gain is very high.

(So is distortion.)

Use negative feedback to lower gain and distortion.


Better op-amp with emitter follower:

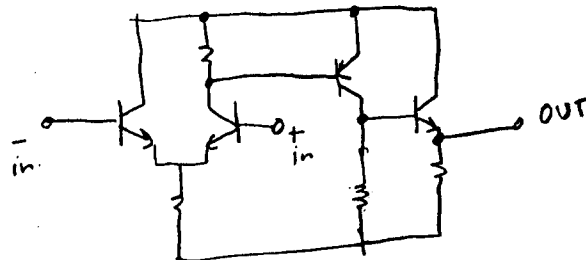

Improving the op-amp

30
5

Current mirrors.

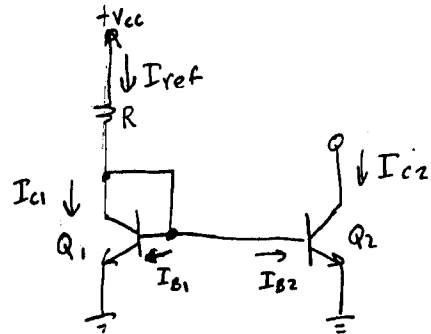

Q_1 and Q_2 are the same.

$$I_{C2} = I_{ref}$$

Use R to set current.

Suppose -- $V_{CC} = 10$
 $R = 10K$

Since $V_{BE} = .6$,
 $V_R = 9.4$
so $I_{ref} = .94 \text{ ma}$.


$V_{BE_{Q1}} = V_{BE_{Q2}} \longrightarrow$ Implies $I_{C2} = .94 \text{ ma}$ also.

Can get other currents by making Q_1, Q_2 different.

Let Q_2 be like Q_1 except 10 times the area --- equivalent to 10 of them in parallel.

Now, $I_{C2} = 9.4 \text{ ma}$.

Also:

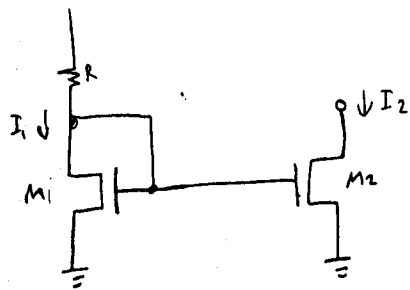


if M_1 and M_2 are identical, $I_1 = I_2$.


I_2 can be scaled by adjusting size.

Op amp with current mirrors:

30
6

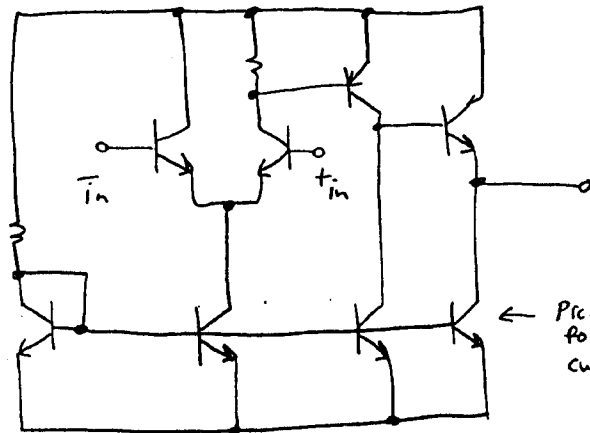

Similar with FET's

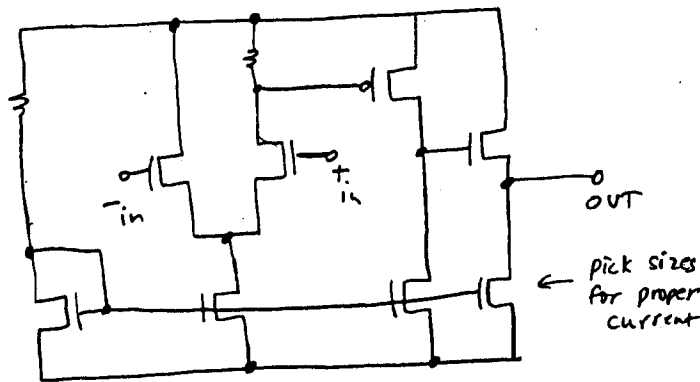

Getting rid of the collector resistor -
Use a current mirror there, too.

3C
7

