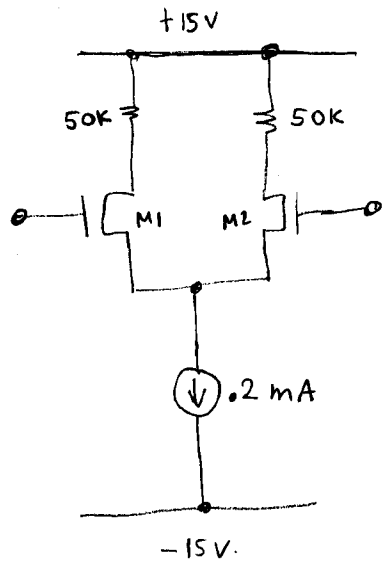


MOSFET differential amp (Chapter 7-1).

(4B)
1



$$K' = 2 \times 10^{-4}$$

$$V_{TH} = 2$$

$$\frac{W}{L} = 10$$

Find operating point:

$$I_D = 1 \text{ mA} = 10^{-3}$$

$$= \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} (2 \times 10^{-4}) (10) (V_{GS} - V_{TH})^2$$

$$10^{-3} = 10^{-3} (V_{GS} - V_{TH})^2$$

$$V_{DD} - V_D = I_D R_D$$


$$= (10^{-3}) (5 \times 10^4)$$

$$V_{DD} - V_D = 5$$

$$V_D = +10$$



Differential gain

(4B)
2

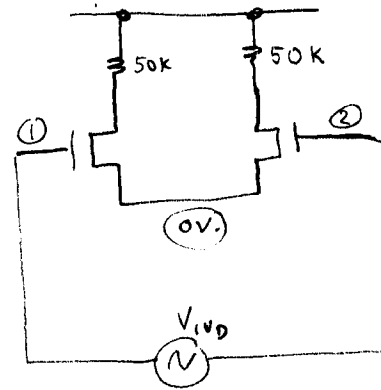

Think about ...

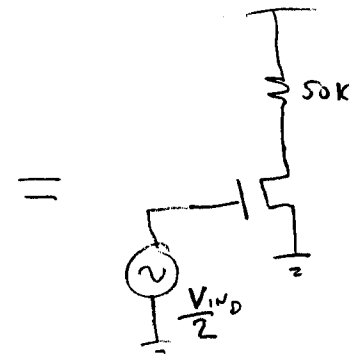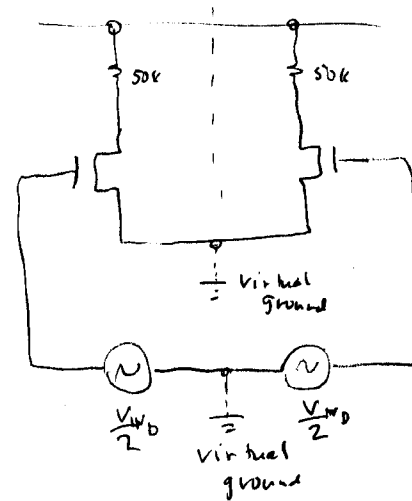Node ① goes up, Node ② goes down
by the same amount




$$A = \frac{g_m R_L}{2}$$

split to half circuits -
analyze each half

Common mode "gain"


(4B)
3

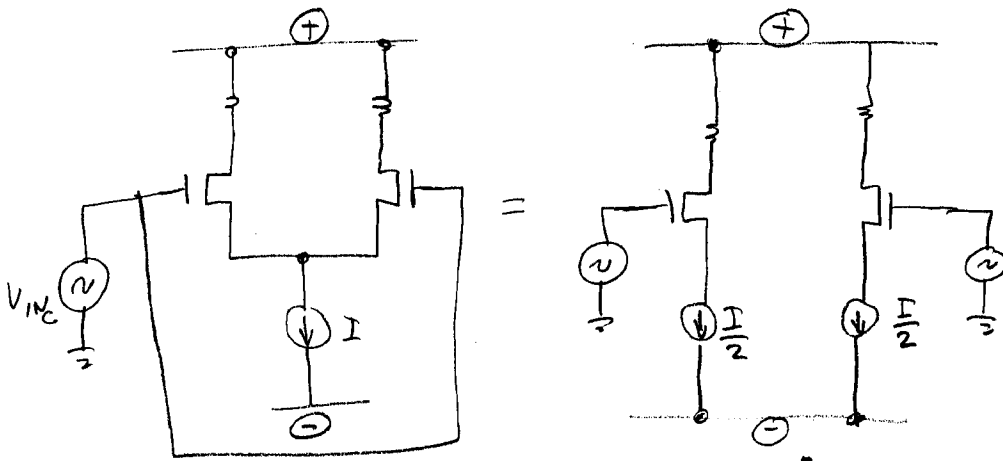

split to half-circuits
Analyze each half.


Drive one side...

(4B)
4

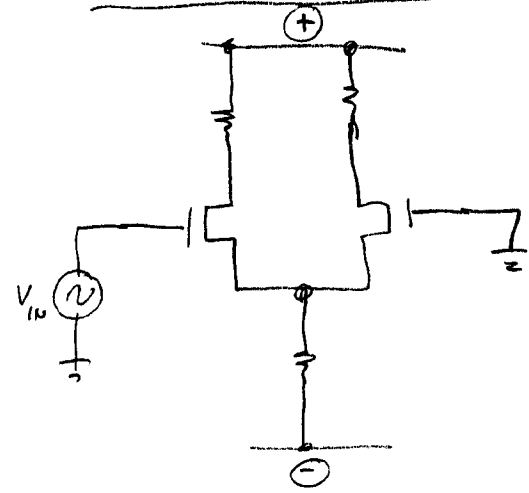

Apply superposition —
it consists of both differential mode
and common mode.

Differential

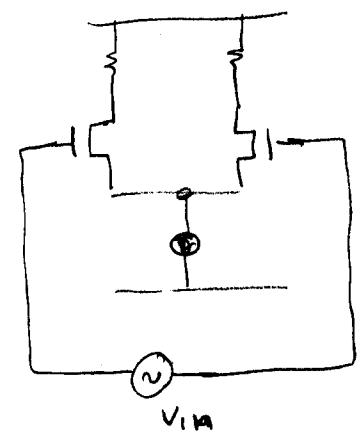

Common mode

