

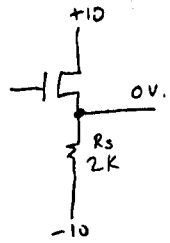


Last stage

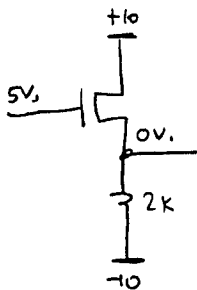
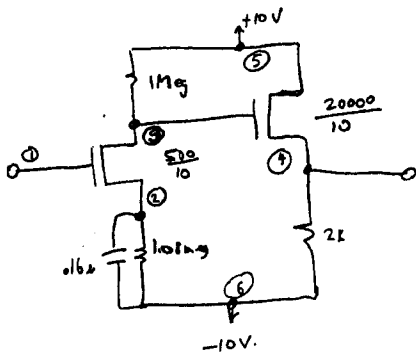
$$I_{DQ} = \frac{V}{R_s} = \frac{10}{2k} = 5\text{ma}$$



$$R_{out} = 50\Omega$$

$$= \frac{1}{g_m + \frac{1}{2k}}$$

$$g_m + \frac{1}{2k} = \frac{1}{50}$$

$$g_m = \frac{1}{50} - \frac{1}{2k} = \frac{1}{51.28} = .0195 \approx .02$$

$$g_m = \sqrt{2K_p \frac{W}{L} I_{DQ}}$$

$$.02 = \sqrt{(2)(20\mu) \frac{W}{L} (5\text{ma})}$$

$$.02 = \sqrt{200 \times 10^{-9} \frac{W}{L}}$$

$$400 \times 10^{-6} = 200 \times 10^{-9} \frac{W}{L}$$

$$\frac{400 \times 10^{-6}}{200 \times 10^{-9}} = \frac{W}{L} = 2000$$

$$\boxed{L = 10\mu}$$

$$\boxed{W = 20,000\mu}$$

$$2k = K_p \frac{W}{L} = (20\mu)(2000)$$

$$= .04$$

$$K = .02$$

$$I_D = K(V_{GS})^2$$

$$.005 = .02(V_{GS})^2$$

$$\frac{.005}{.02} = (V_{GS})^2 = .25$$

$$\boxed{V_{GS} = .5}$$


Choose FET:

$$\boxed{V_{TH} = 4.5 \Rightarrow V_{GS} = 5.0}$$

$$V_{TH} = -2 \Rightarrow V_{GS} = -1.5$$

TEST 1

First stage

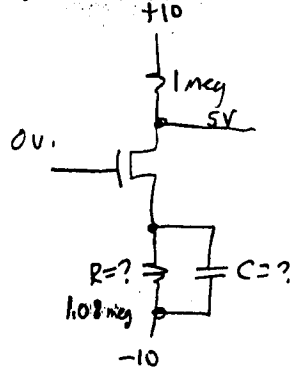

$$\text{Gain} = 100 \Rightarrow 40\text{ dB}$$

$$= -g_m R_L \quad R_L = 1\text{meg}$$

$$g_m = \frac{100}{1e6} = 10^{-4}$$

$$= \sqrt{2K_p \frac{W}{L} I_{DQ}}$$

$$I_{DQ} = \frac{5V}{1\text{meg}} = 5\mu\text{A}$$

$$10^{-4} = \sqrt{(2)(20 \times 10^{-6}) \frac{W}{L} (5 \times 10^{-6})}$$

$$10^{-4} = \sqrt{(2 \times 10^{-10}) \frac{W}{L}}$$

$$10^{-8} = 2 \times 10^{-10} \frac{W}{L}$$

$$\frac{10^{-8}}{1.8 \times 10^{-10}} = \frac{W}{L} = 50$$

$$\boxed{L = 10\mu}$$

$$\boxed{W = 500\mu}$$

If $V_G = 0$, $V_{GS} = 4.6$

then $V_S = -4.6$

$$V_{RS} = 10 - 4.6 = 5.4$$

$$I = 5\mu\text{A} \text{ (from } I_D)$$

$$R = \frac{V}{I} = \frac{5.4V}{5\mu\text{A}} = 1.08\text{meg}$$

$$C: R_{S \text{ effective}} = \frac{1\text{meg}}{100} = 10k$$

$$f = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi f R}$$

$$C = \frac{1}{2\pi (100)(10k)} = 1.59 \times 10^{-7}$$

$$\boxed{C = .16\mu\text{f}}$$

TEST 2

$$2k = K_p \frac{W}{L} = (20\mu)(50)$$

$$= .001$$

$$K = .0005$$

$$I_D = K(V_{GS})^2$$

$$5\mu\text{A} = 50 \frac{\mu\text{A}}{\text{V}^2} (V_{GS})^2$$

$$\frac{5}{500} = V_{GS}^2$$

$$V_{GS} = .1$$

Choose FET:

$$\boxed{V_{TH} = 4.5 \Rightarrow V_{GS} = 4.6}$$

$$V_{TH} = -2 \Rightarrow V_{GS} = -1.9$$