

Stage 2 - design for 40 dB gain.

$$\text{Gain} = -g_m R_L \Rightarrow \frac{1}{g_m} = \frac{R_L}{\text{gain}} = \frac{10k}{100} = 100$$

$$g_m = 0.01$$

$$g_m = \sqrt{2K' \frac{W}{L} I_{DQ}}$$

$$0.01 = \sqrt{2(5 \times 10^{-6}) \left(\frac{W}{L}\right) (1.5 \times 10^{-3})}$$

$$10^{-4} = 2(5 \times 10^{-6}) \left(\frac{W}{L}\right) (1.5 \times 10^{-3})$$

$$\frac{W}{L} = 6667$$

$$L = 1 \mu\text{m} \\ W = 6666 \mu\text{m}$$

$$\text{check: } \sqrt{2(5 \times 10^{-6})(6667)(1.5 \times 10^{-3})} = 0.01 \checkmark$$

Bias: $V_{GS} = ?$


$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$1.5 \times 10^{-3} = \frac{1}{2} (5 \times 10^{-6}) (6667) (V_{GS} - V_{TH})^2$$

$$(V_{GS} - V_{TH})^2 = 9 \times 10^{-2}$$

$$V_{GS} - V_{TH} = 0.3 \Rightarrow V_{GS} = 1.3$$

$$V_G = 15 - 1.3 = 13.7$$

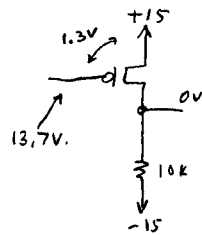

①

Stage 1: design for 40 dB gain

$$I_D = 5 \mu\text{A} \quad V_{RD} = 1.3$$

$$R = \frac{V}{I} = \frac{1.3}{5 \times 10^{-6}} = 260k$$

$$\text{gain} = g_m R_L \quad g_m = \frac{\text{gain}}{R_L} = \frac{100}{260k}$$

$$g_m = 3.85 \times 10^{-4} = \frac{1}{2600}$$

$$g_m = \sqrt{2K' \frac{W}{L} I_{DQ}}$$

$$3.85 \times 10^{-4} = \sqrt{2(20 \times 10^{-6}) \left(\frac{W}{L}\right) (5 \times 10^{-6})}$$

$$1.48 \times 10^{-5} = 2(20 \times 10^{-6}) \left(\frac{W}{L}\right) (5 \times 10^{-6})$$

$$\frac{W}{L} = 740$$

$$L = 1 \mu\text{m} \\ W = 740 \mu\text{m}$$

$$\text{check: } \sqrt{2(20 \times 10^{-6})(74000)(5 \times 10^{-6})} = 3.85 \times 10^{-4} \checkmark$$

$$\text{Bias: } I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{TH})^2$$


$$5 \times 10^{-6} = \frac{1}{2} (20 \times 10^{-6}) (740) (V_{GS} - V_{TH})^2$$

$$(V_{GS} - V_{TH})^2 = 6.76 \times 10^{-4}$$


$$V_{GS} - V_{TH} = 0.026$$

$$V_{GS} = 1.026 \text{ V} \dots$$
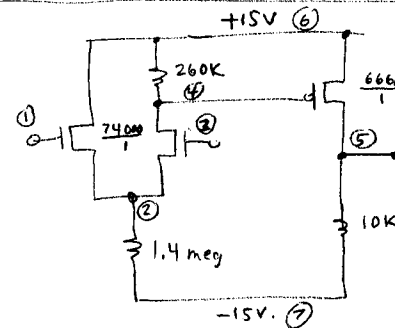
$$R_S = \frac{14V}{10 \mu\text{A}} = 1.4 \text{ meg.}$$



②

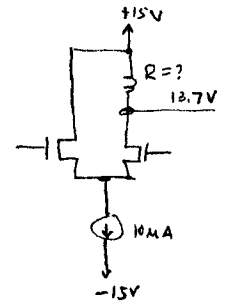

Gnuicap 2005.05.15 RCS 25.20
 The Gnu Circuit Analysis Package
 Never trust any version less than 1.0
 Copyright 1982-2002, Albert Davis
 Gnuicap comes with ABSOLUTELY NO WARRANTY
 This is free software, and you are welcome
 to redistribute it under certain conditions
 according to the GNU General Public License.
 See the file "COPYING" for details.
 gnuicap> <p4.ckt echo

"project 4" simple op-amp
 m1 6 1 2 7 nnn l=1u w=740u
 m2 4 3 2 7 nnn l=1u w=740u
 m3 5 4 6 6 ppp l=1u w=6666u
 rs 2 7 1.4meg
 rd 6 4 260k
 rout 5 7 10k
 rb1 1 0 1meg
 rb2 3 0 1meg
 vin 3 1 gen
 vdd 6 0 dc 15
 vss 7 0 dc -15

.model nnn nmos level=1 kp=20u vto=1 cgdo=2e-10 cgso=2e-10 tox=50e-9
 .model ppp pmos level=1 kp=5u vto=-1 cgdo=2e-10 cgso=2e-10 tox=50e-9
 .print op v(nodes)
 .op

#	v(1)	v(2)	v(3)	v(4)	v(5)	v(6)	v(7)
300.15	0.	-1.026	0.	13.702	-0.23979	15.	-15.

.print ac v(nodes)

.ac 1k
 #Freq v(1) v(2) v(3) v(4) v(5) v(6) v(7)
 1.K 0.50549 0.02264 0.49548 48.739 4.8345K 4.8345u 4.834
 5u

.ac 1 1g dec
 #Freq v(1) v(2) v(3) v(4) v(5) v(6) v(7)
 1. 0.5 23.233u 0.5 49.966 4.9562K 4.9562u 4.956
 2u
 10. 0.5 232.11u 0.5 49.966 4.9562K 4.9562u 4.956
 2u
 100. 0.50006 0.0023204 0.49995 49.953 4.955K 4.955u 4.955

u
 1.K 0.50549 0.02264 0.49548 48.739 4.8345K 4.8345u 4.834
 5u
 10.K 0.58753 0.093993 0.41534 20.235 2.0072K 2.0072u 2.007
 2u
 100.K 0.60229 0.10226 0.39775 2.211 219.31 219.31n 219.3

1n
 1.Meg 0.56128 0.075462 0.44315 0.22215 21.959 21.958n 21.95
 8n
 10.Meg 0.5099 0.014304 0.49032 0.028886 2.1966 2.1963n 2.196
 5n
 100.Meg 0.50762 0.0092518 0.49244 0.01855 0.21889 218.88p 218.8
 9p
 1.G 0.4938 0.0083927 0.50626 0.016787 0.026016 26.161p 26.05
 4p

gnuicap> print ac v(4) vp(4)

gnuicap> ac

#Freq	v(4)	vp(4)
1.	49.966	179.99
10.	49.966	179.87

100.	49.953	178.71
1.K	48.739	167.28
10.K	20.235	113.94
100.K	2.211	92.99
1.Meg	0.22215	94.767
10.Meg	0.028886	127.04
100.Meg	0.01855	144.4
1.G	0.016787	41.993

gnuicap> b

>rgg 1 0 1

>

gnuicap> op

#	v(1)	v(2)	v(3)	v(4)	v(5)	v(6)	v(7)
300.15	0.	-1.026	0.	13.702	-0.23979	15.	-15.

gnuicap> ac

#Freq	v(4)	vp(4)
1.	50.012	179.99
10.	50.012	179.87
100.	49.999	178.71
1.K	48.785	167.28
10.K	20.257	113.94
100.K	2.2135	92.973
1.Meg	0.22233	94.607
10.Meg	0.028925	125.63
100.Meg	0.02001	131.94
1.G	0.031221	30.869

gnuicap> print ac + vp(1) vp(3)

gnuicap> ac

#Freq	v(4)	vp(4)	vp(1)	vp(3)
1.	50.012	179.99	-180.	-2.7181n
10.	50.012	179.87	-179.97	-27.181n
100.	49.999	178.71	-179.73	-271.68n
1.K	48.785	167.28	-177.44	-2.589u
10.K	20.257	113.94	-175.82	-4.9136u
100.K	2.2135	92.973	-175.07	-5.9561u
1.Meg	0.22233	94.607	-141.79	-54.396u
10.Meg	0.028925	125.63	-97.336	-543.41u
100.Meg	0.02001	131.94	-91.542	-0.0054094
1.G	0.031221	30.869	-91.135	-0.051855

gnuicap> 1

M1 (6 1 2 7) nnn l= 1.u w= 740.u
 M2 (4 3 2 7) nnn l= 1.u w= 740.u
 M3 (5 4 6 6) ppp l= 1.u w= 0.006666
 Rs (2 7) 1.4Meg
 Rd (6 4) 260.K
 Rout (5 7) 10.K
 Rb1 (1 0) 1.Meg
 Rb2 (3 0) 1.Meg
 Vin (3 1) GENERATOR
 Vdd (6 0) DC 15.
 Vss (7 0) DC -15.

.model nnn nmos (level=1 tnom= 27. fc= 0.5 pb= 0.8 cj= 0. mj= 0.5 cjsw= 0.
 mjsw= 0.5 is= 10.f rsh= 0. cgso= 200.p cgdo= 200.p cgbo= 0. vto= 1. gamma=
 0. phi= 0.6 tox= 50.n ld= 0. uo= 600. tpg=1 kp= 20.u)
 +>(* cox= 690.6288u)
 .model ppp pmos (level=1 tnom= 27. fc= 0.5 pb= 0.8 cj= 0. mj= 0.5 cjsw= 0.
 mjsw= 0.5 is= 10.f rsh= 0. cgso= 200.p cgdo= 200.p cgbo= 0. vto=-1. gamma=
 0. phi= 0.6 tox= 50.n ld= 0. uo= 600. tpg=1 kp= 5.u)
 +>(* cox= 690.6288u)

```
.print op v(nodes)
.op
.print ac v(nodes)
.ac 1k
.ac 1 lg dec
Rgg ( 1 0 ) 1.
gnucap> del rgg
```

```
gnucap> print ac v(5) vp(5)
```

```
gnucap> ac
```

#Freq	v(5)	vp(5)
1.	10.127f	180.
10.	1.0127p	180.
100.	101.27p	179.97
1.K	10.126n	179.73
10.K	1.0115u	177.32
100.K	91.791u	154.9
1.Meg	0.0021447	100.41
10.Meg	0.020571	68.419
100.Meg	0.051191	13.373
1.G	0.052572	1.3611

```
gnucap> op
```

#	v(1)	v(2)	v(3)	v(4)	v(5)	v(6)	v(7)
300.15	0.	-1.026	0.	13.702	-0.23979	15.	-15.

```
gnucap> ac
```

#Freq	v(5)	vp(5)
1.	4.9562K	-0.012936
10.	4.9562K	-0.12936
100.	4.955K	-1.2934
1.K	4.8345K	-12.723
10.K	2.0072K	-66.113
100.K	219.31	-87.495
1.Meg	21.959	-90.07
10.Meg	2.1966	-93.396
100.Meg	0.21889	-123.61
1.G	0.026016	92.496

```
gnucap> EOF on stdin
```

